

FIGURE 8.1 Datapath Example

the a
cells
ment
logic
desig
struc

cess

8.2

Add
mul
num
add
mer
is re
ing

and
can
pro
can
P te

8.2

Pro
to


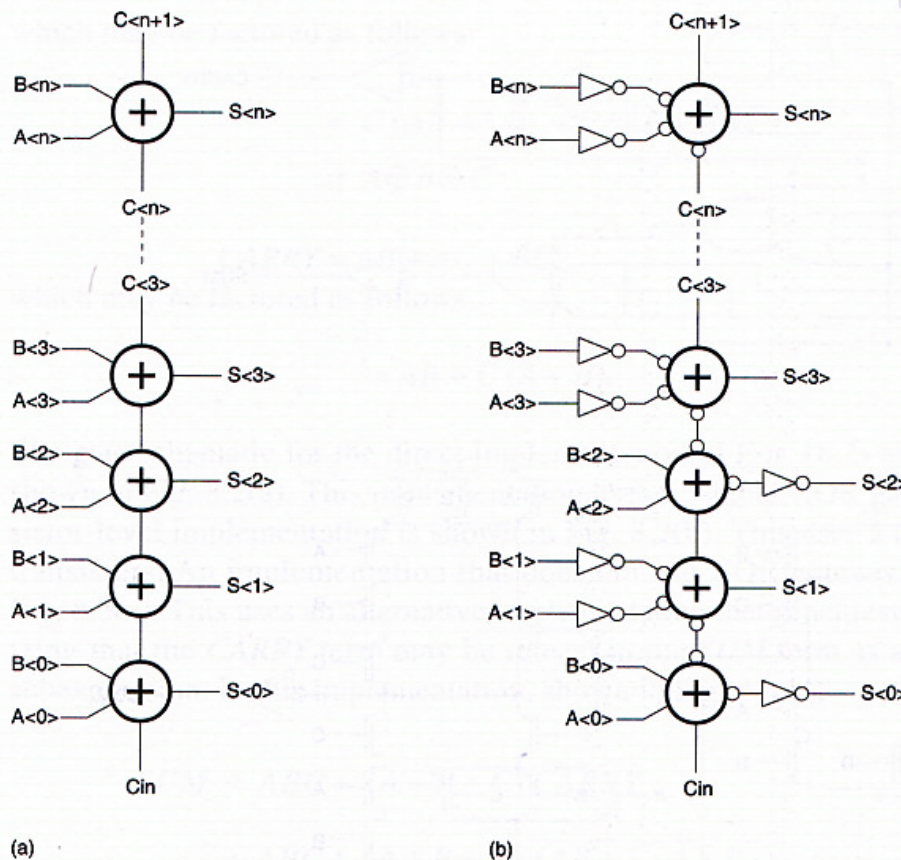


Figure 8.4 Parallel adder implementations

B<3>
B<2>
B<1>
B<0>

(a)

tra
lay

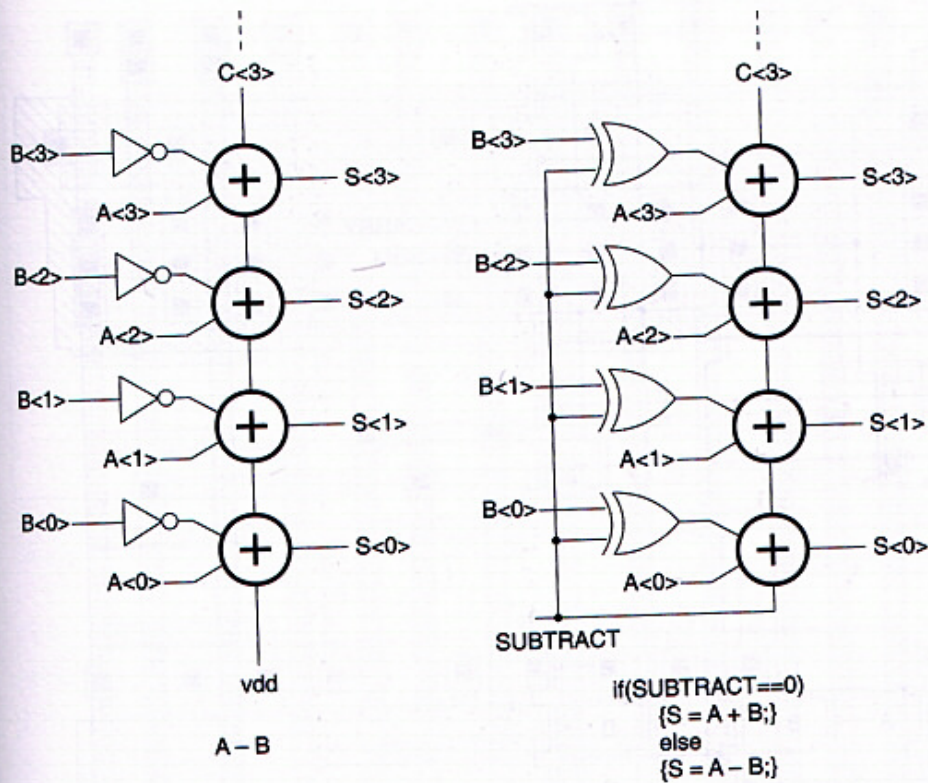

(a)

(b)

FIGURE 8.5 Arithmetic operators: (a) subtractor; (b) adder/subtractor

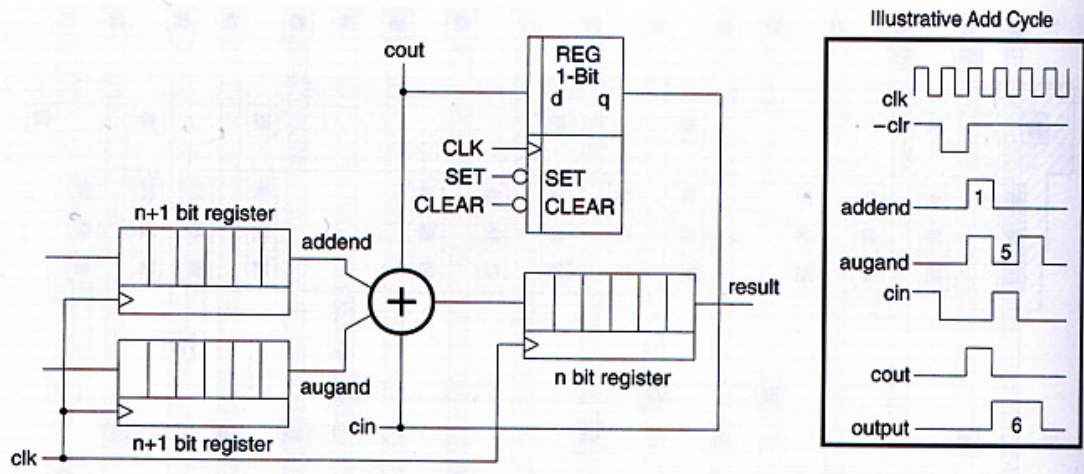


Figure 8.8 Bit-serial adder implementation

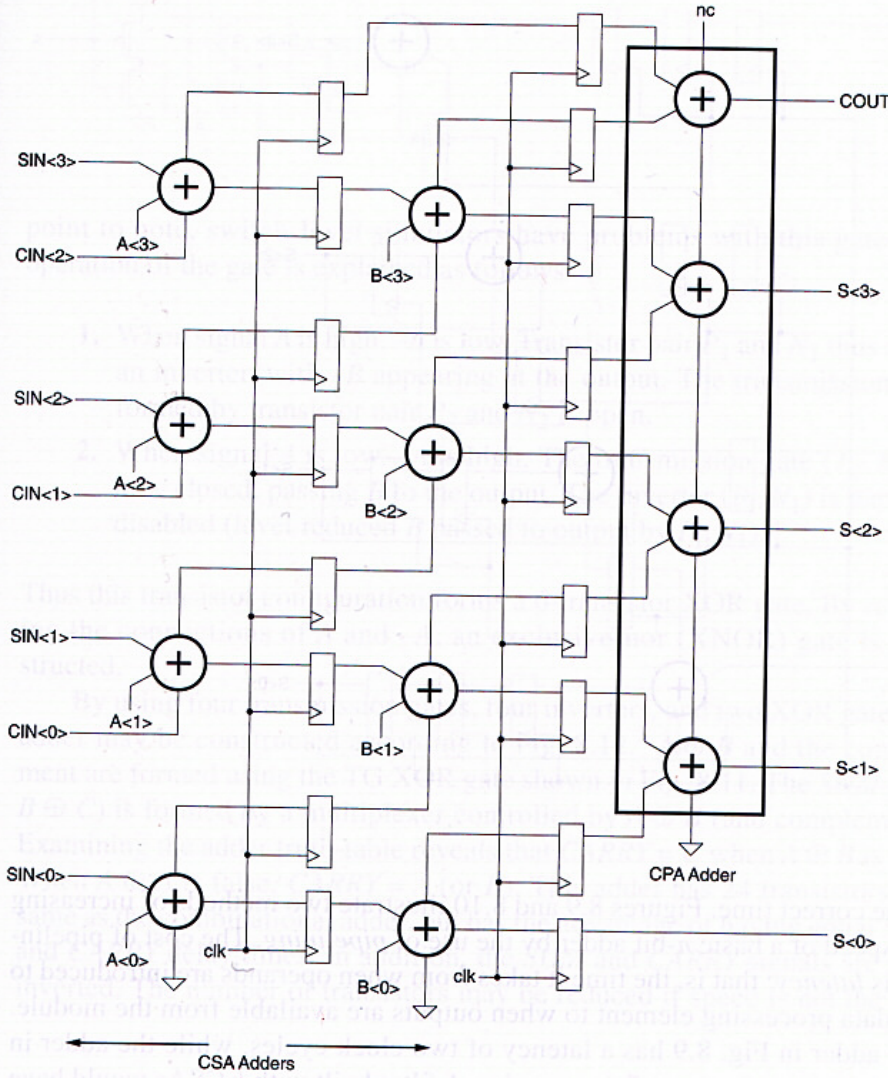


FIGURE 8.9 Carry-save adder (CSA) example

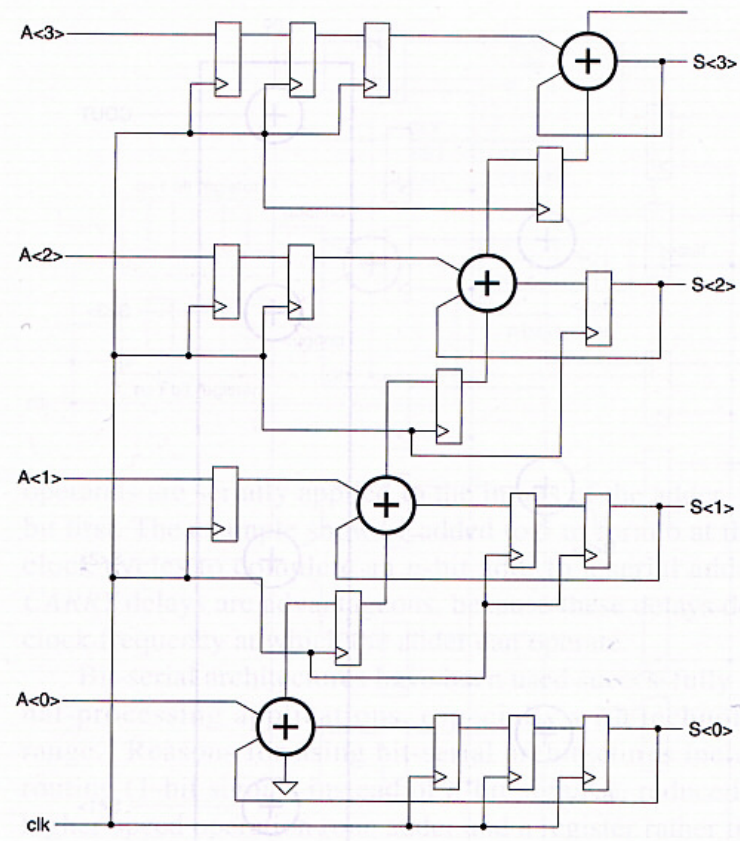


Figure 8.10 Pipelined carry-propagate (CPA) example

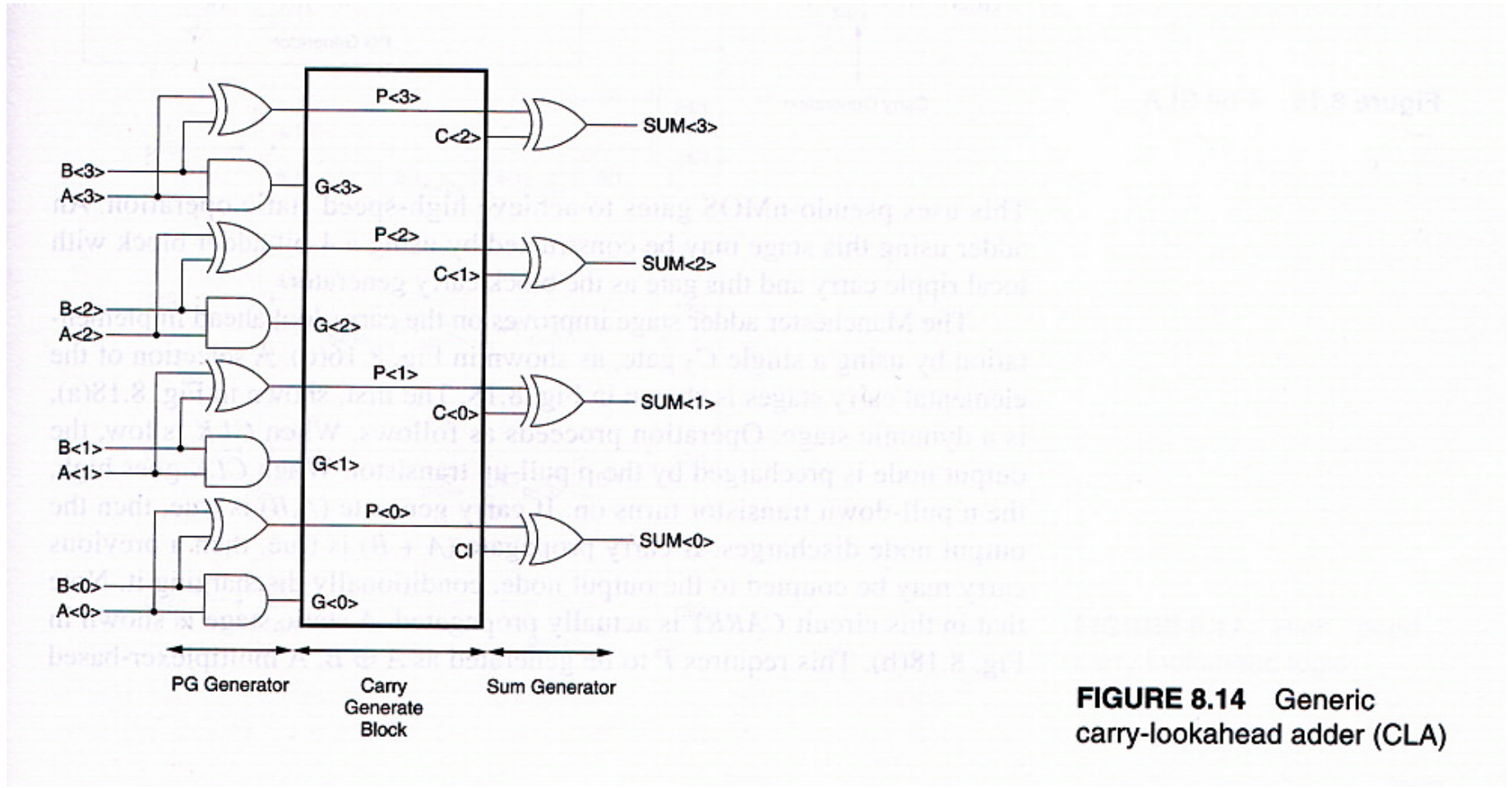


FIGURE 8.14 Generic carry-lookahead adder (CLA)

TABLE 8.2 4-bit Multiplier Partial Products

				X3	X2	X1	X0	Multiplicand
				Y3	Y2	Y1	Y0	Multiplier
				X3Y0	X2Y0	X1Y0	X0Y0	
			X3Y1	X2Y1	X1Y1	X0Y1		
		X3Y2	X2Y2	X1Y2	X0Y2			
X3Y3	X2Y3	X1Y3	X0Y3					
P7	P6	P5	P4	P3	P2	P1	P0	Product

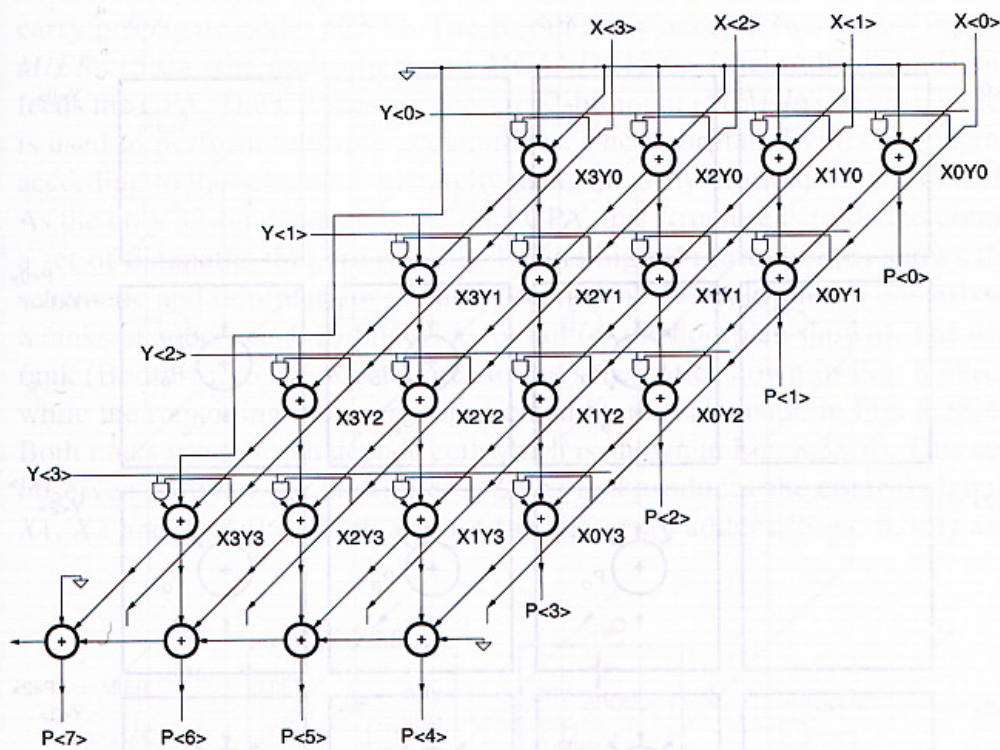


FIGURE 8.36 A 4×4 array multiplier

are mn sum-
 tes. For 4-bit
 2.
 dders, and n^2
 multiplier is
 shows a cell
 is propagated

 
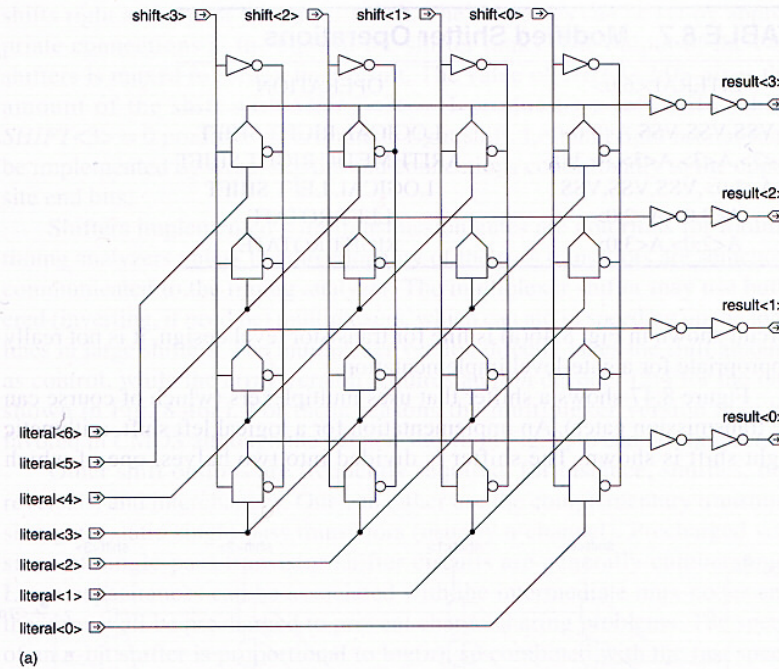


FIGURE 8.46 Array shifter using transmission gates: (a) circuit; (b) cell layout

TABLE 8.6 Shifter Operations

SHIFT	RESULT
1	LITERAL<3:0>
2	LITERAL<4:1>
4	LITERAL<5:2>
8	LITERAL<6:3>

 
 


FIGURE 8.48 Memory-chip architecture

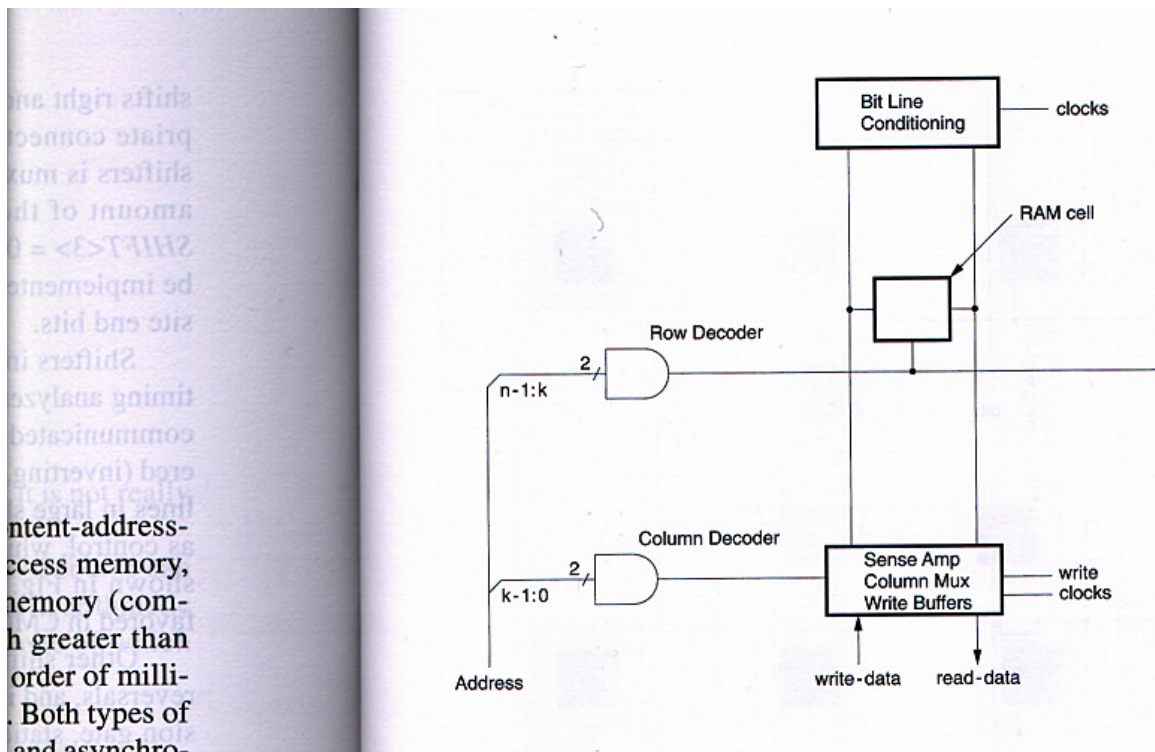


FIGURE 8.49 Generic RAM circuit

 
 


Figure 8.50 Static RAM cell circuits

 


FIGURE 8.51 Mask layout for 6-transistor static RAM

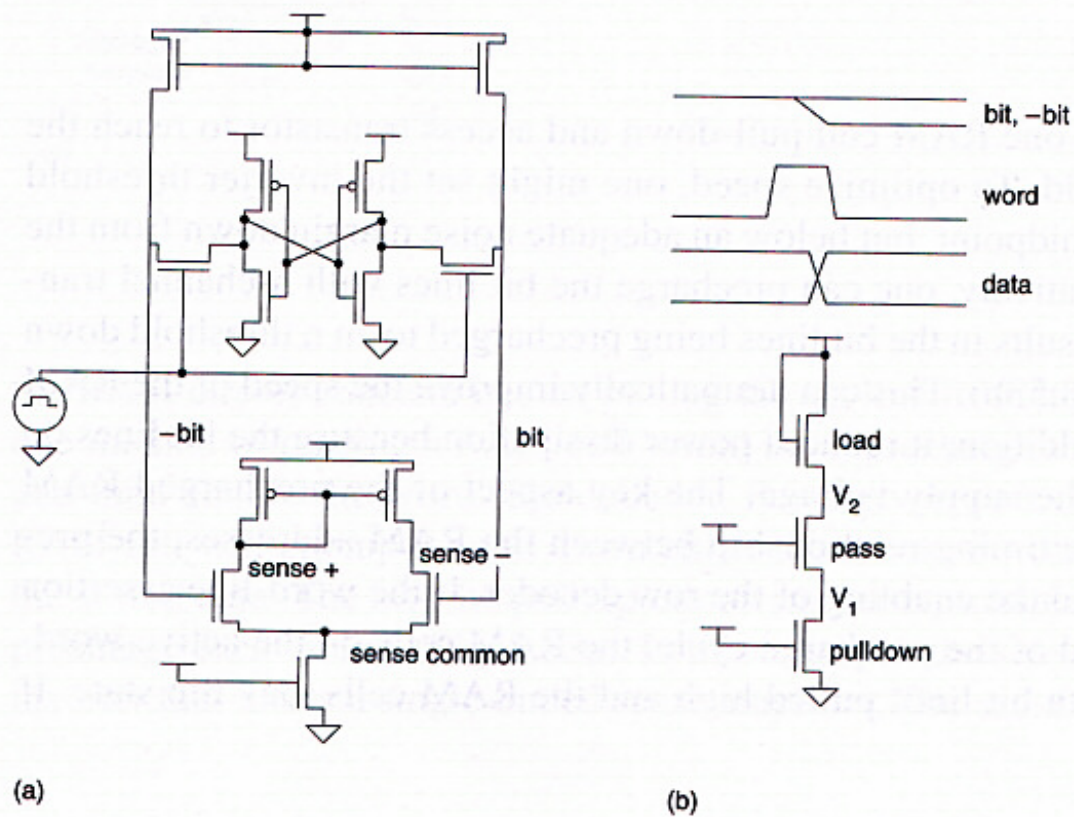


Figure 8.54 RAM read operation model


 
 


FIGURE 8.57 Static RAM—write circuits: (a) n-channel pass transistors; (b) circuit model during write; (c) complementary transmission gate version

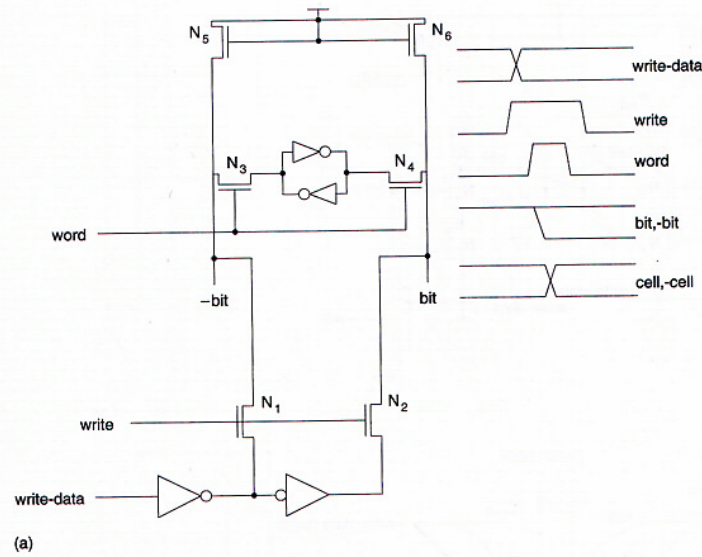

If the delay in Fig. 8.64 could be used where routed to a sense the decoder has write operation is being actively s. However, the nt values before AM, this speed y sizing transis- / decode signal. 8.3.1.6 RA The circuit p and write ports. ng pass transis-

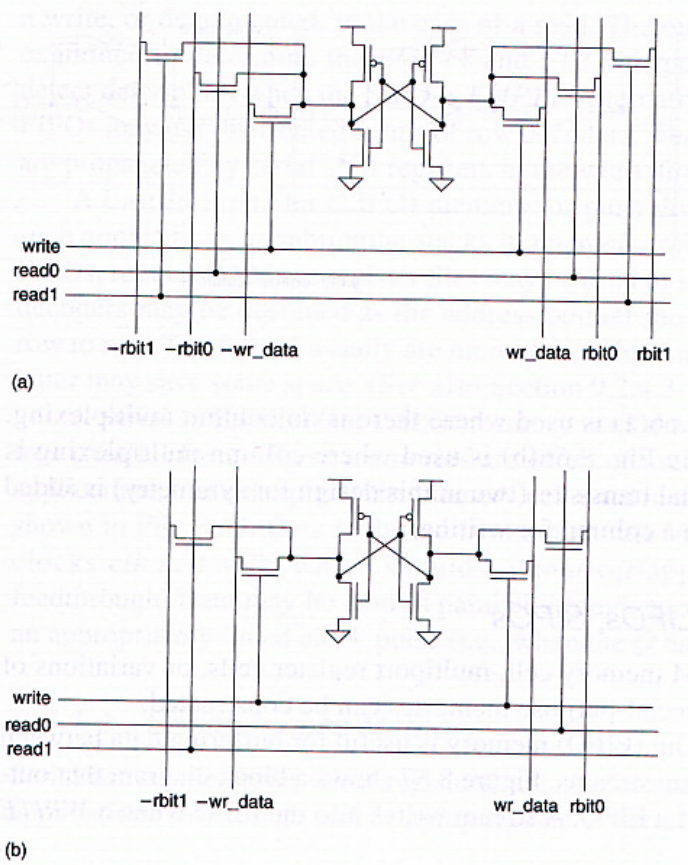


FIGURE 8.65 Multiported (2R-1W) RAM cell: (a) fully differential; (b) single-ended read

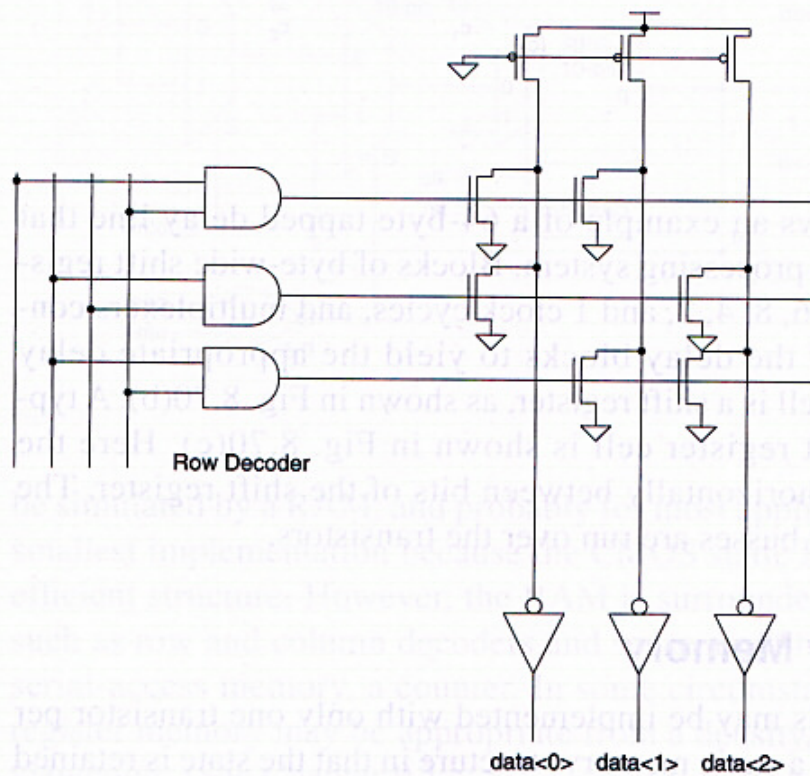


Figure 8.71 Basic ROM architecture

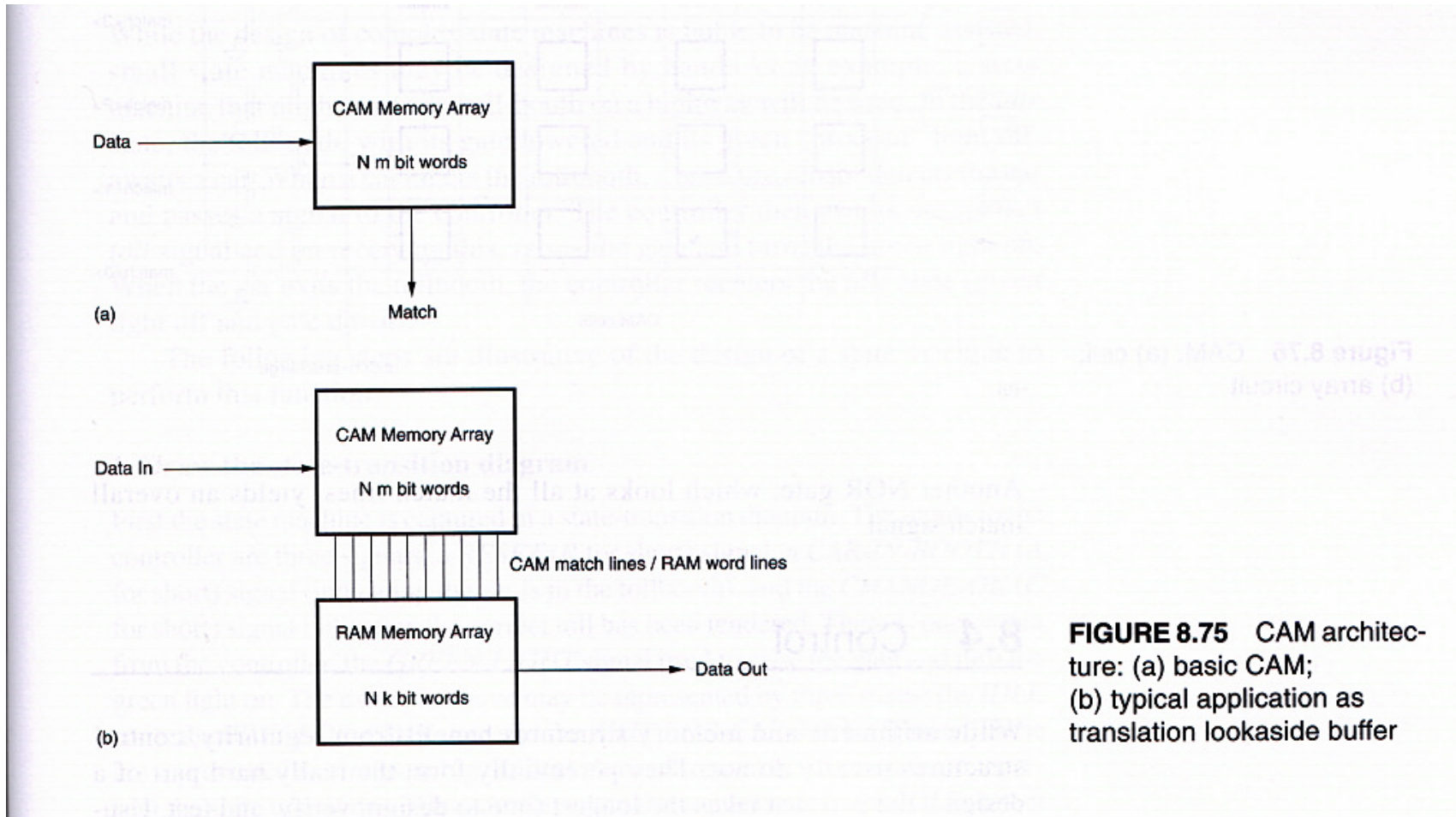


FIGURE 8.75 CAM architecture: (a) basic CAM; (b) typical application as translation lookaside buffer