

“A Verilog Overview”

by

Orlando J. Hernandez, Ph.D.

Electrical & Computer Engineering
School of Engineering
THE COLLEGE OF NEW JERSEY

Presentation Overview

- Introduction to Verilog – Part I
- Introduction to Verilog – Part II
 - AND, OR, HALF ADDER, FULL ADDER
- Introduction to Verilog – Part III
 - ALU Design
- Control and Data Path Organization
 - Finite State Machines, Digital Filter
- Q&A Sessions

INTRODUCTION TO Verilog





PART I

Design Automation

- Need To Keep With Rapid Changes, Electronic Products Have To Be Designed Extremely Quickly
- Electronic **D**esign **A**utomation (**EDA**)
 - Design Entry
 - Simulation
 - Synthesis
 - Design Validation & Test

Design Automation. Cont...

- Design Entry
 - Schematic Capture

    

Design Automation. Cont...

- Design Entry - Textual Form:
 - Verilog
 - VHDL (**V**HSIC **H**ardware **D**escription Language)
 - VHSIC (**V**ery **H**igh **S**peed **I**ntegrated Circuits)

Design Automation. Cont...

- Design Entry - Textual Form:

```
module and_2 (X, Y, Z);  
    input X, Y;  
    output Z;  
  
    assign Z = X & Y;  
endmodule
```

Introduction To Verilog

- Verilog Is an Industry Standard Language to Describe Hardware From the Abstract to Concrete Level.

BRIEF HISTORY OF Verilog

- Began as a proprietary HDL promoted by Cadence Design Systems.
- Cadence transferred control of Verilog to a consortium of companies and universities known as Open Verilog International (OVI).
- Verilog is an IEEE Standard (IEEE Standard 1364-1995).
- Verilog continues to be extended and upgraded (IEEE Standard 1364-2000, System Verilog).

MOTIVATION


- Need a Method to Quickly Design, Implement, Test and Document Increasingly Complex Digital Systems.
- Schematic and Boolean Equations Inadequate for Million-Gate ICs.
- Design Portability

What is Verilog?

- A Design entry language
- A Simulation modeling language.
- A Verification language.
- A Standard language.
- As simple or complex as required.


How is Verilog Used?

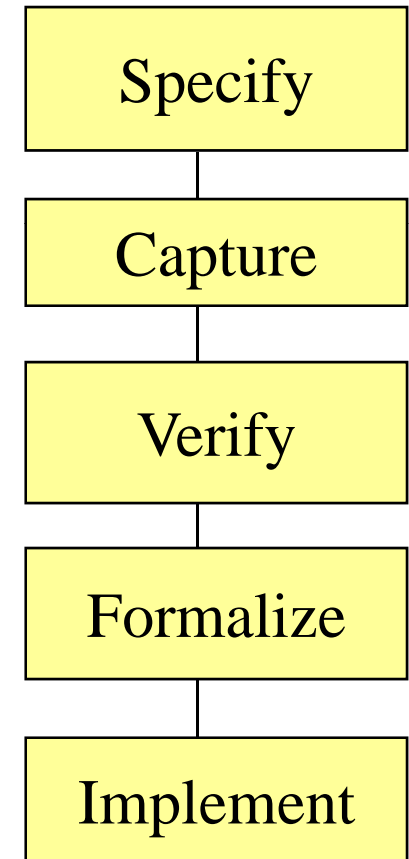- For Design Specification (“Specify”)
- For Design Entry (“Capture”)
- For Design Simulation (“Verify”)
- For Design Documentation (“Formalize”)
- As an Alternate to Schematics



Design Process (e. g. for FPGAs)

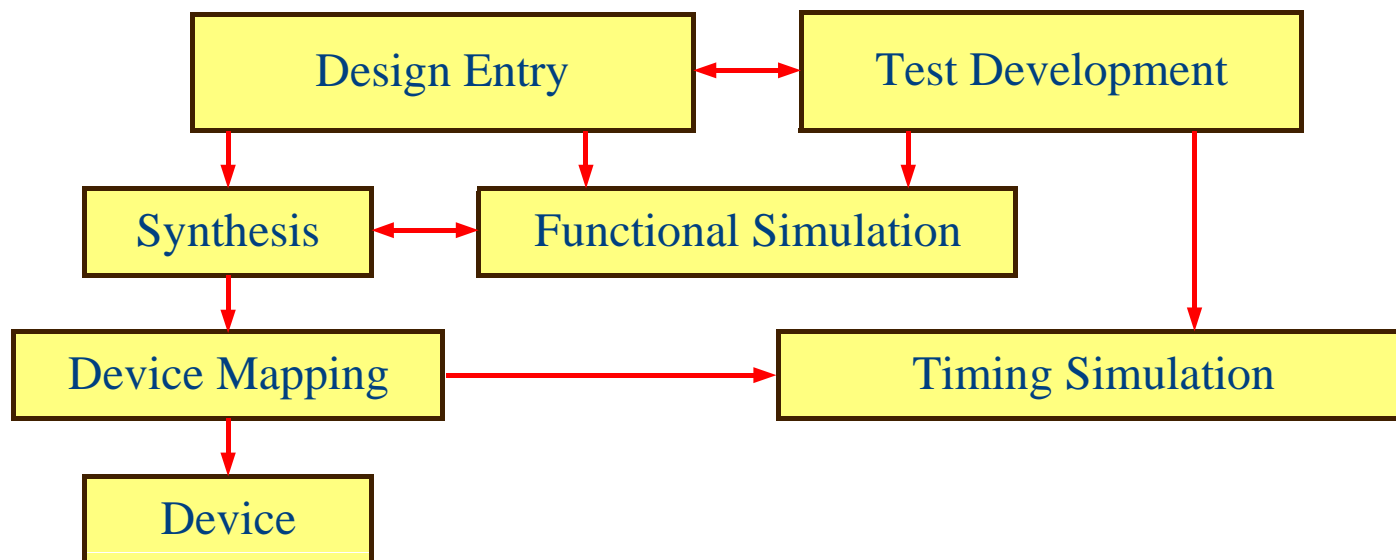- Verilog Can Be Used for Both Design and Test Development



When Should Verilog Be Used?

- Verilog is highly beneficial to use as a structured, top down approach to design.
- Verilog makes it easy to build, use, and reuse libraries of circuit elements.
- Verilog can greatly improve your chances of moving into more advanced tools and design flows.

Advantages of Verilog

- The Ability to Code the Behavior and to Synthesize an Actual Circuit.
- Power and Flexibility
- Device (specific FPGA) Independent Design
- Technology (specific silicon process) Independent Design

Advantages of Verilog Cont...

- Portability Among Tools and Devices
- Fast Switch Level Simulations
- Quick Time to Market and Low Cost
- Industry Standard

Getting Started with Verilog

- Its Easy To Get Started With Verilog, But It Can Be Difficult To Master It.
- To Begin With, A Subset of The Language Can Be Learned To Write Useful Models.
- Later, More Complex Features Can Be Learned To Implement Complex Circuits, Libraries, And APIs.

A First look at Verilog


- Lets start with a simple Combinational circuit: an 8-bit Comparator.

An 8 Bit Comparator

- Comparator Specifications:
 - Two 8-bit inputs
 - 1-bit Output
 - Output is 1 if the inputs match or 0 if they differ.

An 8 Bit Comparator

Comparator

 

	0	1	2	3	4	5	6	7
A	1	0	1	1	0	0	1	1
B	1	0	1	1	0	0	1	1

Comparator Verilog Source Code

```
// Eight-bit Comparator
module compare (A, B, EQ)
    input [7:0] A, B;
    output EQ;

    assign EQ = (A == B);
endmodule
```

- Define the inputs and outputs - the ports of the circuit
- Define the function of the circuit

What is a module

- Every Verilog design description has at least one module construct.
- A large design has many modules and are connected to form the complete circuit.
- The module port declarations describe the circuit as it appears from “outside”- from perspective of its input and output interfaces.

What is a module?

```
module compare (A, B, EQ)
  input [7:0] A, B;
  output EQ;
  :
  :
```

- The module and port declarations includes a name, compare, and port direction statements defining all the inputs and outputs of the module.
- The Rest of the module Describes the Actual Function.

What is a module?

```
    :  
    :  
    assign EQ = (A == B);  
endmodule
```

- Before the keyword **endmodule** is found the actual functional description of the comparator.

Data Types

- Verilog's high level data types allow data to be represented in much the same way as in high-level programming languages.
- A data type is an abstract representation of stored data.

Data Types

- These data types might represent individual wires in a circuit, or a collection of wires.

Data Types

- Basic Data Types
 - Nets
 - **wire, wand, tri, wor**
 - Continuously driven
 - Gets new value when driver changes
 - LHS of continuous assignment

```
tri [15:0] data;  
    // unconditional  
assign data[15:0] = data_in;  
    // conditional  
assign data[15:0] = enable ? data_in : 16'bz;
```
 - Registers
 - Reg
 - Represents storage
 - Always stores last assigned value
 - LHS of an assignment in a procedural block

```
reg signal;  
@(posedge clock) signal = 1'b1;  
    // positive edge  
@(reset) signal = 1'b0; // event (both edges)
```

Some Data Types

Data Type	Values	Examples
Bit	'1' , '0' , 'x' , 'z'	Q = 1'b1;
Array of bits	"101001"	Data[5:0] = 6'b101001;
Boolean	Use Bit	EQ = 1'b1; // True
Integer	-2, -1, 0, 1, 2, 3	C = c+2;
Real	1.0, -1.0E5	V1 - V2/5.3;
Time	'timescale 1ns/1ps	#6 Q = 1'b1;
Register	Single or array of bits	
Character	Use 8-bit register	
String	Use register of length 8 x the # of characters	

Design Units

- Design units are a concept that provide advanced configuration management capabilities.
- Design units are modules of Verilog that can be compiled separately and stored in a library.

Library Design unit

- A Library is a collection of commonly used modules to be used globally among different design units.
- Library is identified with compiler/simulator command line switches.

Levels of Abstraction (Styles)

- Verilog supports many possible styles of design description.
- These styles differ primarily in how closely they relate to the underlying hardware.

Levels of Abstraction (Styles)

- Levels of Abstraction refers to how far your design description is from an actual hardware realization.
- The three main levels of abstraction are:
 - Behavior
 - Dataflow
 - Structure



Levels of Abstraction (Styles)

Behavior

Dataflow

Structure



Performance Specification

Test Benches

Sequential Description

State Machines

Register Transfers

Selected Assignments

Arithmetic Operation

Boolean Equations

Hierarchy

Physical Information

Behavioral Modeling

- The Highest Level of Abstraction Supported in Verilog.
- The Behavior Approach Describes the Actual Behavior of Signals Inside the Component.

Verilog Timing Issues

- The Concept of Time Is the Critical Distinction Between Behavioral Descriptions and Low Level Descriptions.
- The Concept to Time May Be Expressed Precisely, With Actual Delays Between Related Events



An Example of Behavioral Modeling: A half adder



half_adder

- Half Adder
- Inputs a, b : 1 bit each.
- Output Sum, Carry : 1 bit each.

 


Figure 1-1 Half adder circuit

Verilog Code for half_adder

```
// Half Adder
module half_adder (a, b, sum, carry);
  input a, b;
  output sum, carry;

  reg sum, carry;

  always @ (a or b) begin
    sum = a ^ b;
    carry = a & b;
  end
endmodule
```

INTRODUCTION TO Verilog

PART II

Dataflow Modeling

- The dataflow level of abstraction is often called **Register Transfer Language (RTL)**.
- Some behavioral modeling can also be called **RTL**.
- The dataflow level of abstraction describes how information is passed between registers in the circuit.


Concurrent and Sequential Verilog

- Verilog Allows Both Concurrent and Sequential Statements to Be Entered.
- The Difference Between Concurrent and Sequential Statements Must Be Known for Effective Use of the Language.

Concurrent Verilog

- All Statements in the Concurrent Area Are Executed at the Same Time.
- There Is No Significance to the Order in Which Concurrent Statements Occur.

Concurrent Verilog

 


Example of Concurrent Verilog

Full Adder



Full Adder circuit

 

Verilog code for Full Adder

```
// Full Adder Using Signal Assignment Instructions
module full_adder (a, b, c_in, sum, c_out);
    input a, b, c_in;
    output sum, c_out;

    wire s1, s2, s3;

    assign s1 = a ^ b;
    assign s2 = s1 & c_in;
    assign s3 = a & b;
    assign sum = s1 ^ c_in;
    assign c_out = s2 | s3;
endmodule
```

Verilog code for Full Adder

- The **assign** expressions are all concurrent signal assignment statements. All the statements are executed at the same time.

```
assign s1 = a ^ b;
```

```
assign s2 = s1 & c_in;
```

```
assign s3 = a & b;
```

```
assign sum = s1 ^ c_in;
```

```
assign c_out = s2 | s3;
```

Verilog code for Full Adder

- The simulator evaluates all the **assign** expressions, and then applies the results to the signals.
- Once the simulator has applied the results it waits for one of the signal to change and it reevaluates all the expressions again.

Verilog code for Full Adder

- This cycle will continue until the simulation is completed.
- This is called “event driven simulation”.
- It is more computationally efficient than time driven simulation.


Wires

- In the full_adder Verilog code we came across “wire”.
- So what are “wires”?
 - Wires Are Used to Carry Data From Place to Place in a Verilog Design Description.
 - Wires in Verilog Are Similar to Wires in a Schematic.
 - Wires are internal to a module.

Sequential Verilog

- Sequential Statements Are Executed One After the Other in the Order That They Appear.
- Example of Sequential Statement: Always.

Sequential Verilog

 

Always Construct

- The Always construct is the primary means to describe sequential operations.
- Always starts with the keyword *always*, then *begin*, and ends with the keyword *end*.
- The whole *always* construct itself is treated as a concurrent statement.

Always Statement

- The *always* construct consists of three parts
 - Sensitivity List
 - Declaration Part
 - Statement Part

Syntax of Always Statement

```
module module_name ( ... ports ... );  
    :  
    always @ (sensitivity_list)  
        begin : block_name  
            local_declaration;  
            .....  
            sequential statement;  
            sequential statement;  
            .....  
        end  
endmodule
```

Always Example

```
module nand2 (a, b, c);  
  input a, b;  
  output c;  
  
  reg c;  
  
  always @ (a or b)  
    begin : nand2_always_block  
      reg temp;  
      temp = ~(a & b);  
      if (temp == 1'b1) #5 c = temp;  
      else if (temp == 1'b0) #6 c = temp;  
    end  
endmodule
```


Example Description

- The **always** sensitivity list enumerates exactly which signals causes the block to execute.

```
always @ (a or b)
```

Example Description

- The declarative part is used to declare local variables or constants that can be used in the block.

```
reg temp;
```

Example Description

- Variables are temporary storage areas similar to variables in software programming languages.

```
reg temp;
```

Use of Sequential Statements

- Sequential Statements Exist Inside the Always Statements As Well As in Sub Programs.
- The Sequential Statements Are:
 - if case forever repeat
 - while for wait fork/join

if Statements

- The IF statement starts with the keyword *if* and ends with the keyword *end*.

```
if (x < 10) begin  
    a = b;  
end
```

if Statements

- There are also two optional clauses

- else if clause
- else clause

```
if (day == Sunday) begin  
    weekend = true;  
end  
else if (day == Saturday) begin  
    weekend = true;  
end  
else begin  
    weekday = true;  
end
```

if Statements

- The **if** statement can have multiple **else if** statement parts but only one **else** statement part.

Case Statement

- The Case statement is used whenever a single expression value can be used to select between a number of actions.
- A Case statement consists of the keyword ***case*** followed by an operator expression, and ended with an ***endcase*** keyword.

Case Statement

- The expression will either return a value that matches one of the *choices* in a statement part or match a *default* clause.

Case Statement Example

```
reg [1:0] bit_vec;  
.....  
case bit_vec  
  2'b00 :  
    return = 0;  
  2'b01 :  
    return = 1;  
  2'b10 :  
    return = 2;  
  2'b11 :  
    return = 3;  
endcase
```

Loop Statements

- The loop statement is used whenever an operation needs to be repeated.
- Loop statements are implemented in three ways
 - *repeat* condition loop statement
 - *while* condition loop statement
 - *for* condition loop statement

Loop Statements (*repeat*)

- The *repeat* condition Loop statement will loop as many times as the condition expression.

```
repeat (flag) begin  
    day = get_next_day (day);  
end
```

Loop Statements (*while*)

- The *while* condition Loop statement will loop as long as the condition expression is TRUE.

```
while (day == weekday) begin  
    day = get_next_day (day);  
end
```

Loop Statements (*for loop*)

```
for (i = 1; i <= 10; i = i + 1) begin  
    i_squared[i] = i*i;  
end
```

- This loop will execute 10 times whenever execution begins and its function is to calculate squares from 1 to 10 and insert them into i_squared memory.

Wait Statement

- The *wait* statement allows to suspend the sequential execution based on a conditional expression.
- *wait* until an expression is true.

wait (conditional expression)

Wait Statement

- The *wait* conditional expression clause will suspend execution of the process until the expression returns a true value.

```

initial
  begin
    wait (!oe)
    o = q;
  end
  
```


Structural Verilog

- Structural-level design methods can be useful for managing the complexity of a large design description.
- Structure level of abstraction is used to combine multiple components to form a larger circuit.

Structural Verilog


- Structural Verilog Descriptions Are Quite Similar in Format to Schematic Netlists.
- Larger Circuits Can Be Constructed From Smaller Building Blocks.

Example of Structural Verilog


Let us consider an ALU with

- An OR gate
- An XOR gate
- A Half Adder
- A Full Adder
- A Multiplexer

Example of Structural Verilog

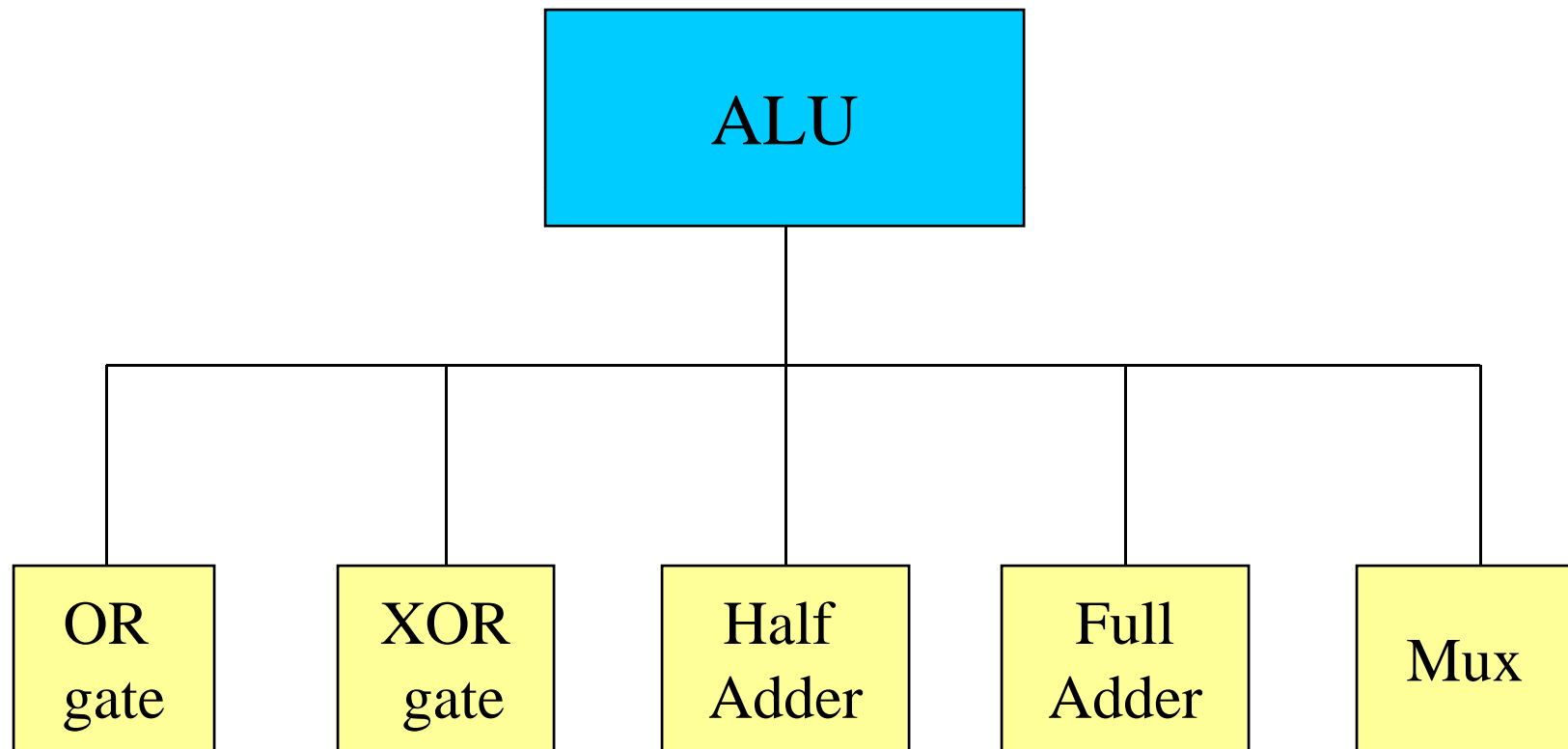


ALU – Block Diagram

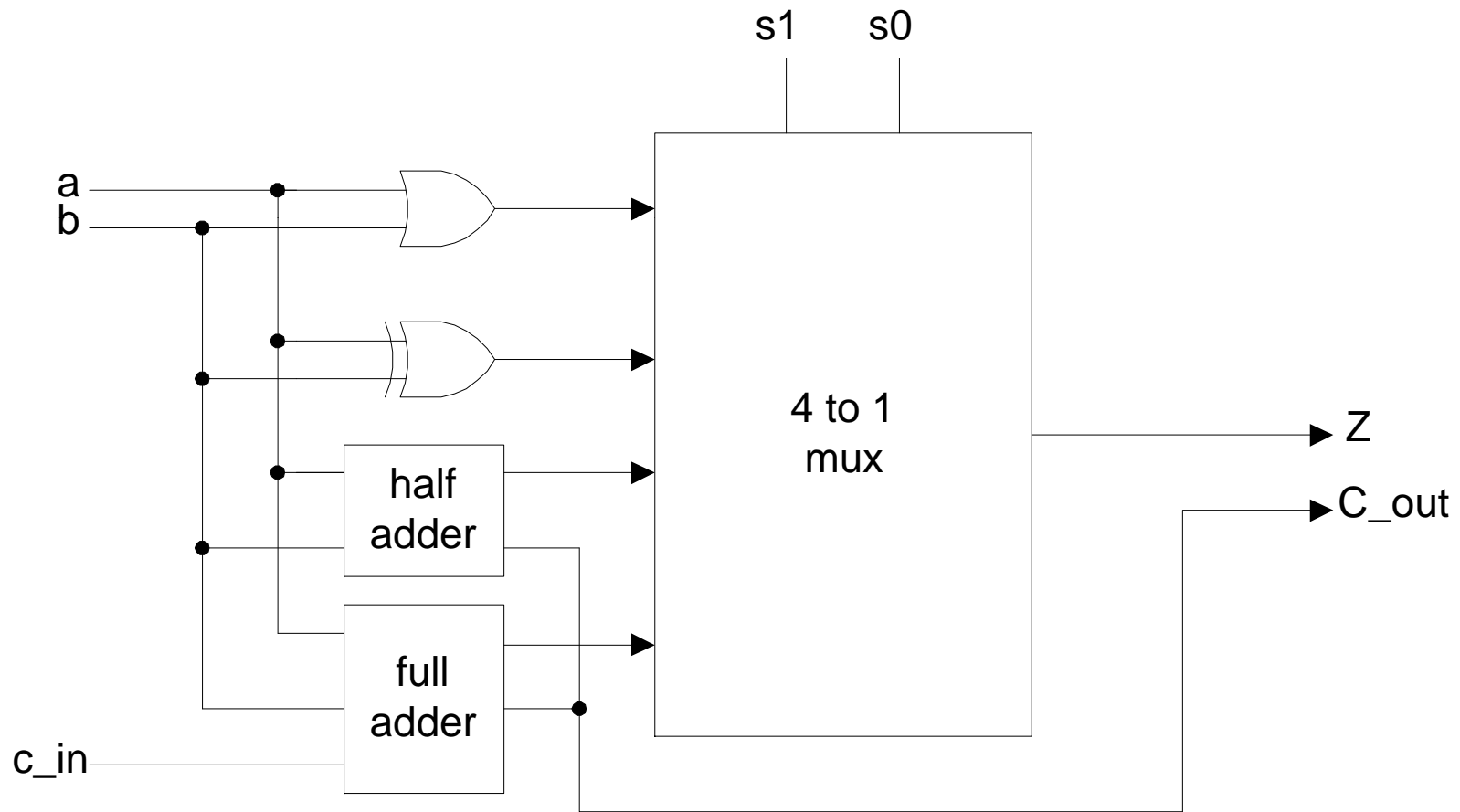

ALU – Function Table

S1	S0	Z	C_out
0	0	a or b	0
0	1	a xor b	0
1	0	ha_sum	ha_c_out
1	1	fa_sum	fa_c_out

 

Electrical & Computer Engineering
 School of Engineering
 THE COLLEGE OF NEW JERSEY

Verilog code for OR gate

```
module t_or (a, b, ored);  
  input a, b;  
  output ored;  
  
  assign ored = a | b;  
endmodule
```

Verilog code for XOR

```
module t_xor (a, b, xored);  
  input a, b;  
  output xored;  
  
  assign xored = a ^ b;  
endmodule
```


Verilog Code for half_adder

// Half Adder

```

module half_adder (a, b, sum, c_out);
  input a, b;           // declaring I/O ports
  output sum, c_out;

  assign sum = a ^ b;
  assign c_out = a & b;
endmodule

```


 


Figure 1-1 Half adder circuit

Full Adder circuit

 

Verilog code for full_adder

```
// Full Adder
module full_adder (a, b, c_in, sum, c_out);
    input a, b, c_in;
    output sum, c_out;

    wire s1, s2, s3;

    assign s1 = a ^ b;
    assign s2 = c_in & s1;
    assign s3 = a & b;
    assign sum = a ^ b;
    assign c_out = s2 | s3;
endmodule
```

```
// Using Signal Assignment Instructions
```

Main Code for ALU

```
module alu (a, b, c_in, s0, s1, z, c_out);  
  input a, b, c_in, s0, s1;  
  output z, c_out;  
  
  reg z, c_out;  
  
  wire ored, xored, ha_sum, ha_c_out, fa_sum, fa_c_out;  
  
  t_or a1 (.a(a), .b(b), .ored(ored));  
  t_xor x1 (.a(a), .b(b), .xored(xored));  
  half_adder h1 (.a(a), .b(b), .sum(ha_sum),  
               .c_out(ha_c_out));  
  full_adder f1 (.a(a), .b(b), .c_in(c_in), .sum(fa_sum),  
               .c_out(fa_c_out));
```

Main Code for ALU Cont....

```

always @ (a or b or c_in or s0 or s1) begin
    if (s1 == 1'b0 && s0 == 1'b0) begin
        z = ored;
        c_out = 1'b0;
    end
    if (s1 == 1'b0 && s0 == 1'b1) begin
        z = xored;
        c_out = 1'b0;
    end
    if (s1 == 1'b1 && s0 == 1'b0) begin
        z = ha_sum;
        c_out = ha_c_out;
    end
    if (s1 == 1'b1 && s0 == 1'b1) begin
        z = fa_sum;
        c_out = fa_c_out;
    end
end
end
endmodule


```

CONTROL AND DATA PATH ORGANIZATION

Control and Data Path Organization

- Most complex digital circuits can be broken up into two parts:
 - Control
 - Data Path

Control and Data Path Organization

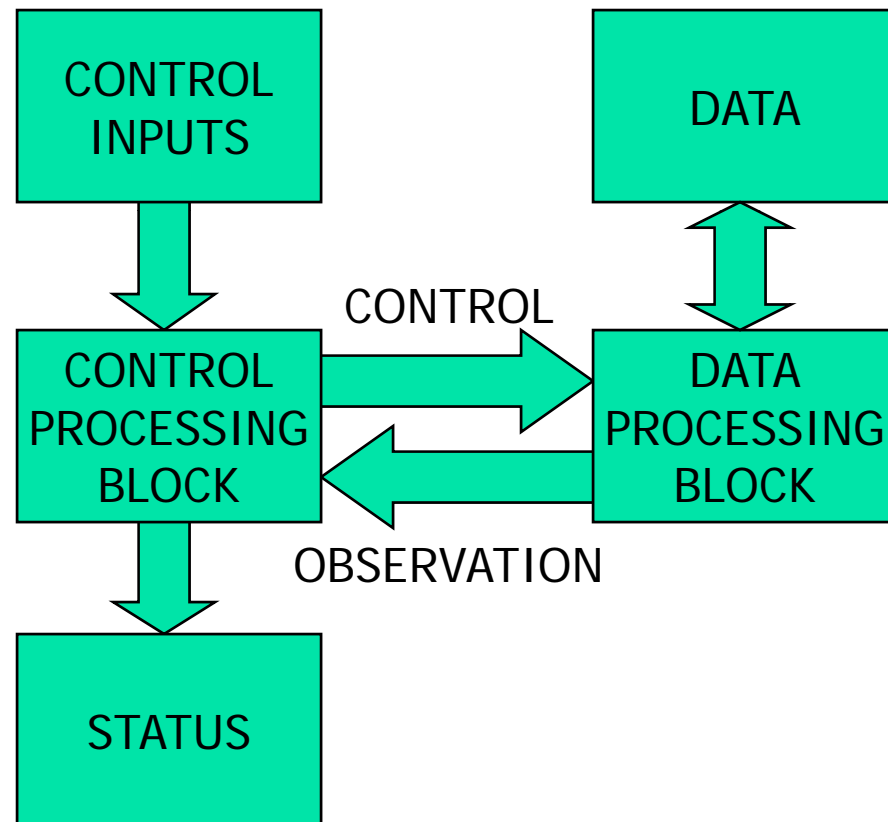


Finite State Machines

- Two Classes of Finite State Machines (FSMs):
 - Moore Machines
 - Mealy Machines


Moore Finite State Machines

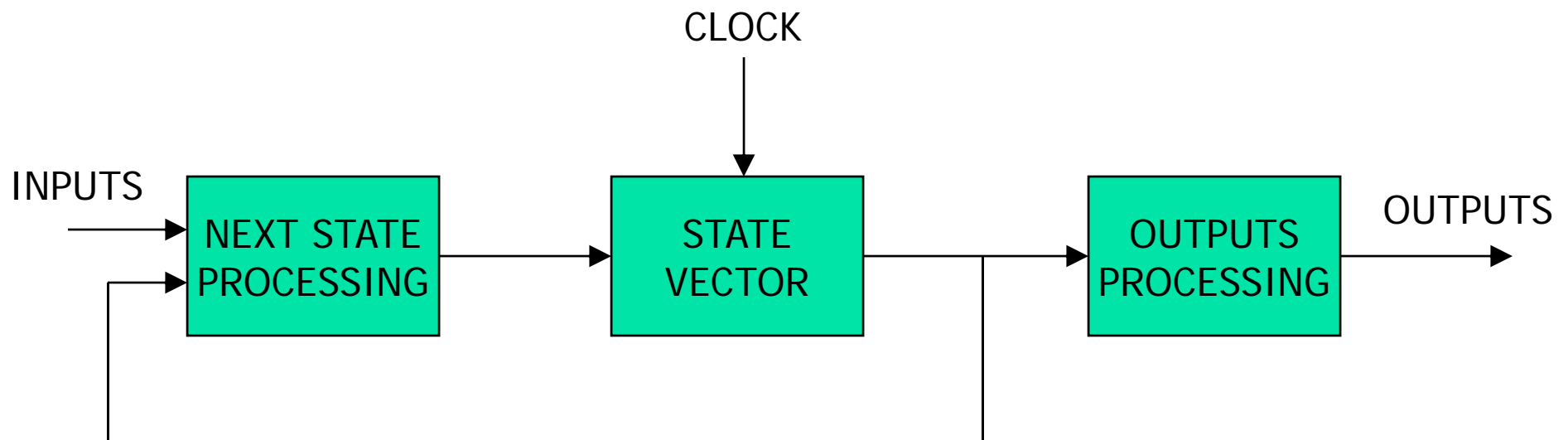- **Outputs depend only on the state**
- State and Outputs Processing are combinational elements
- State Vector is Sequential Elements




Mealy Finite State Machines

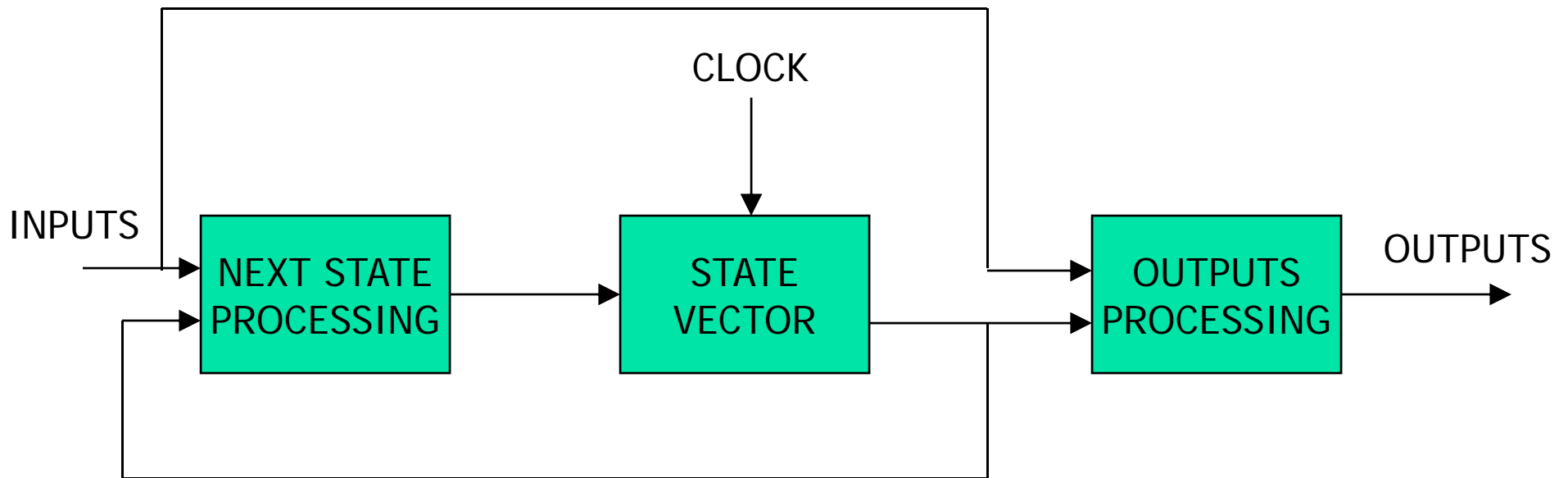- Outputs depend on the state and the inputs




Verilog IMPLEMENTATION EXAMPLES – A Decimation Filter for a Sigma-Delta Analog to Digital Converter

2-Ch Σ - Δ Analog to Digital Converter

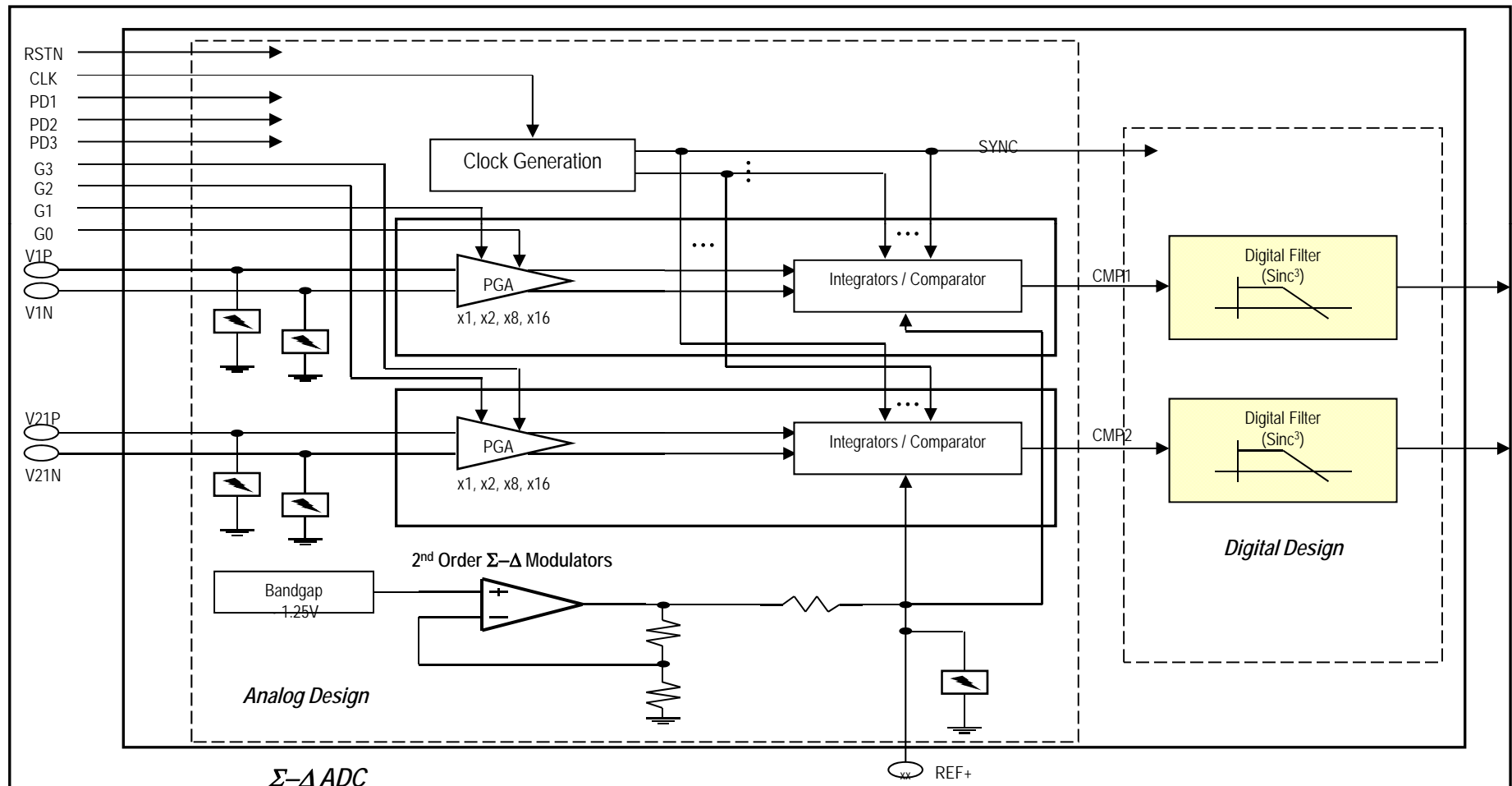


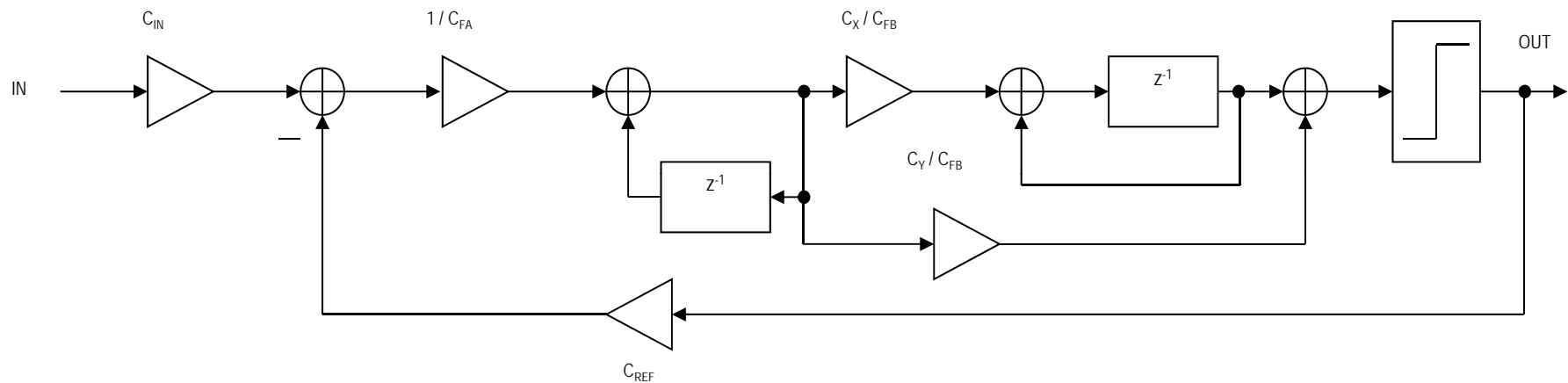2nd Order Σ - Δ Modulator (block/algorithmic)




- This can be modeled in Behavioral Verilog

2nd Order Σ - Δ Modulator (circuit)

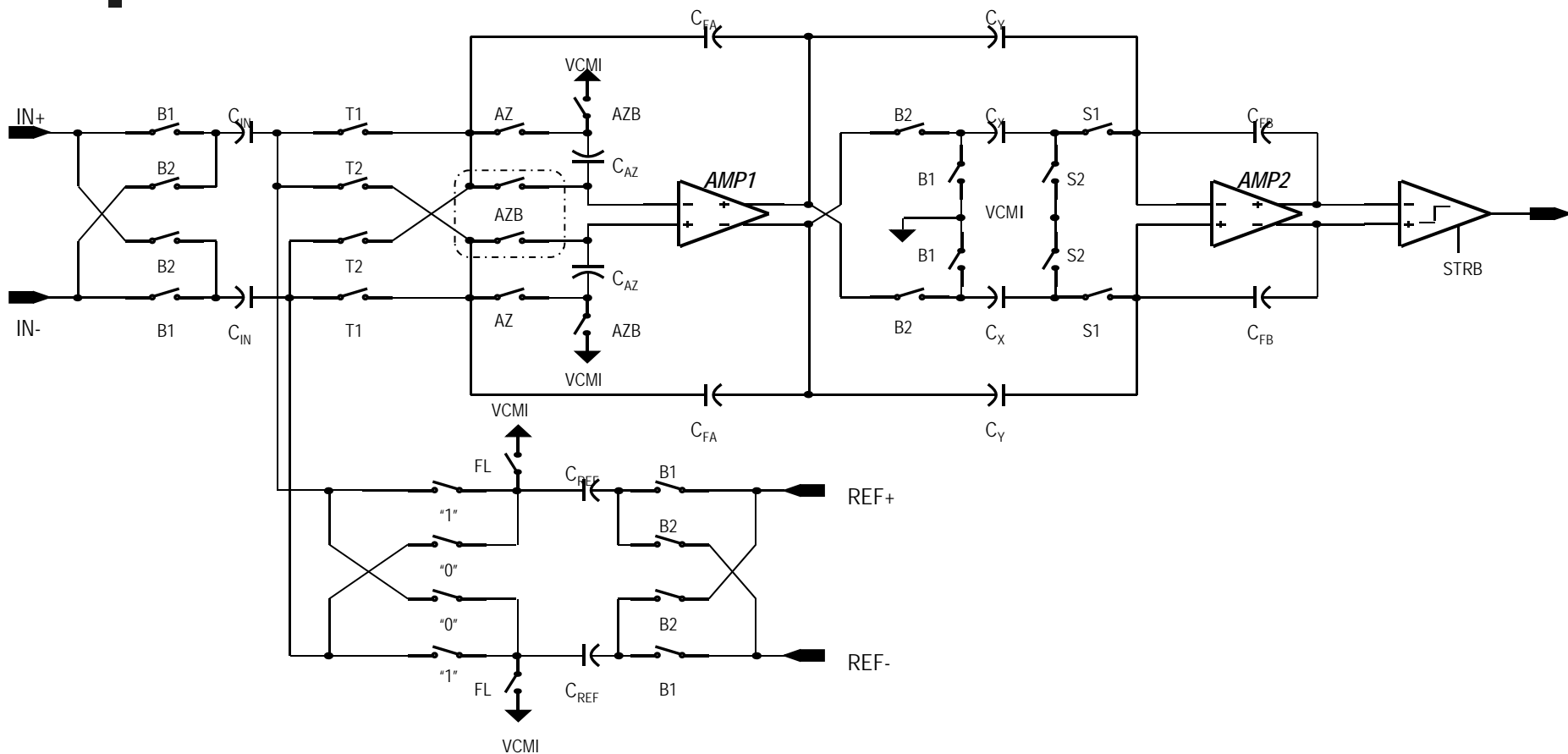

- This can also be modeled in Behavioral Verilog

Decimation Digital Filter

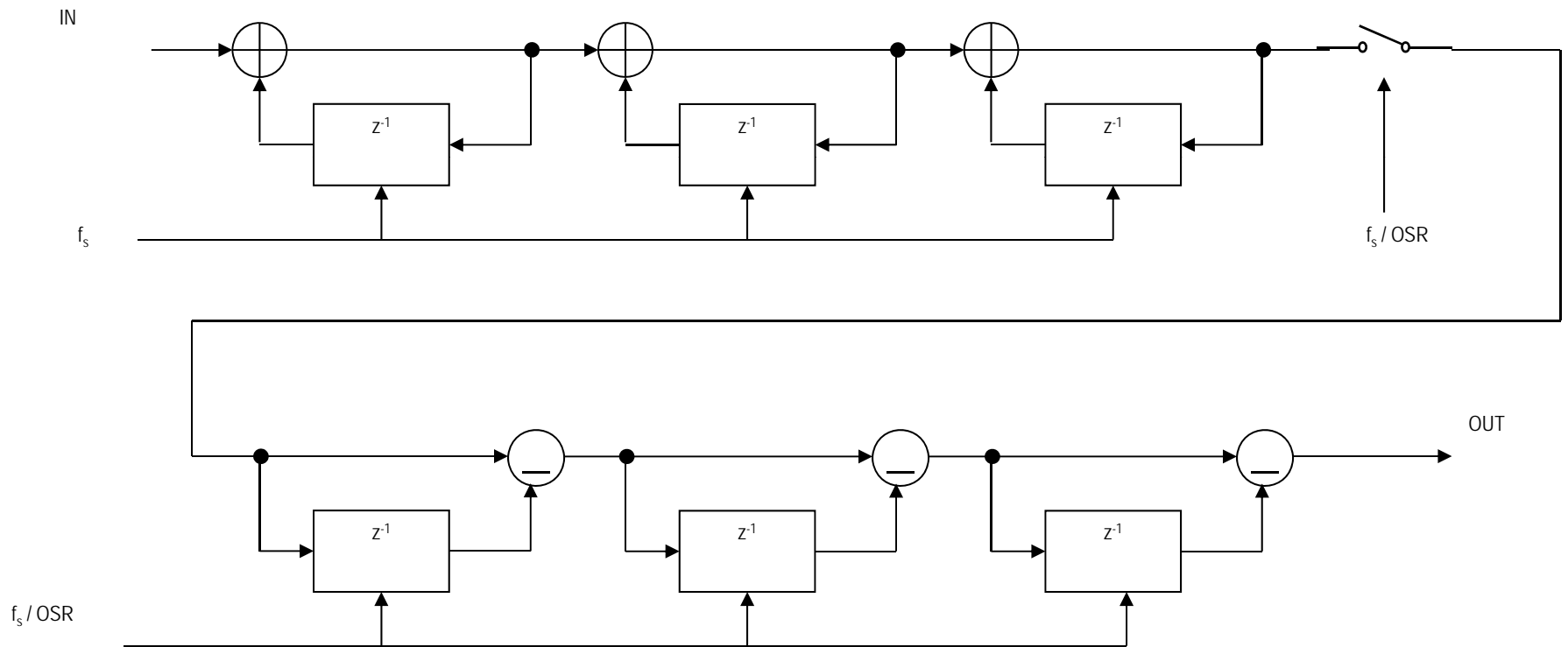

Decimation Digital Filter

- Cubic sinc
- Bits of noise free accuracy for delta-sigma ADC's:
 - $\text{BITS} = 3 * \text{LOG}(\text{OSR}) / \text{LOG}(2) + 2$
 - Assume $\text{OSR}=32$, then $\text{BITS}=17$, and set $\text{BITS}=16$

Decimation Digital Filter

- First Filter Equations
 - $H_1(z) = Y_1(z)/X(z) = 1/(1 - 3z^{-1} + 3z^{-2} - z^{-3})$
 - $y_1(n) = x(n) + 3y_1(n-1) - 3y_1(n-2) + y_1(n-3)$
- Second Filter Equations
 - $H_2(z) = Y(z)/X_1(z) = 1 - 3z^{-1} + 3z^{-2} - z^{-3}$
 - $y(n) = x_1(n) - 3x_1(n-1) + 3x_1(n-2) - x_1(n-3)$
- Decimation (Retiming)
 - $x_1(n) = y_1(n/\text{OSR})$
 - $x_1(n) = y_1(n/32)$

What do we need for our design?

- $y_1(n) = x(n) + 3 y_1(n-1) - 3 y_1(n-2) + y_1(n-3)$
- $y(n) = x_1(n) - 3 x_1(n-1) + 3 x_1(n-2) - x_1(n-3)$
- $x_1(n) = y_1(n/32)$


■ Control

- On every $x(n)$
 - S02: Store $x(n)$ in accumulator, count $x(n) \bmod 32$
 - S03: Accumulate $2 y_1(n-1)$
 - S04: Accumulate $y_1(n-1)$
 - S05: Accumulate 1's complement of $2 y_1(n-2)$
 - S06: Accumulate 1's complement of $y_1(n-2)$
 - S07: Accumulate 2
 - S08: Accumulate $y_1(n-3)$
 - S09: Update y registers
- On every $x_1(n)$ (every 32nd $y_1(n)$)
 - S10: Accumulate 1's complement of $2 x_1(n-1)$
 - S11: Accumulate 1's complement of $x_1(n-1)$
 - S12: Accumulate $2 x_1(n-2)$
 - S13: Accumulate $x_1(n-2)$
 - S14: Accumulate 1's complement of $x_1(n-3)$
 - S15: Accumulate 3, output result
 - S16: Store $y_1(n-1)$ in accumulator
 - S17: Update x registers

■ Data Path

- 16 bits
- Adder-Accumulator
- 1's complement
- Shift left by one ($\times 2$)
- Store $y_1(n-1)$, $y_1(n-2)$, $y_1(n-3)$
- Store $x_1(n-1)$, $x_1(n-2)$, $x_1(n-3)$
- Constants: 2 & 3

Decimation Digital Filter Architecture

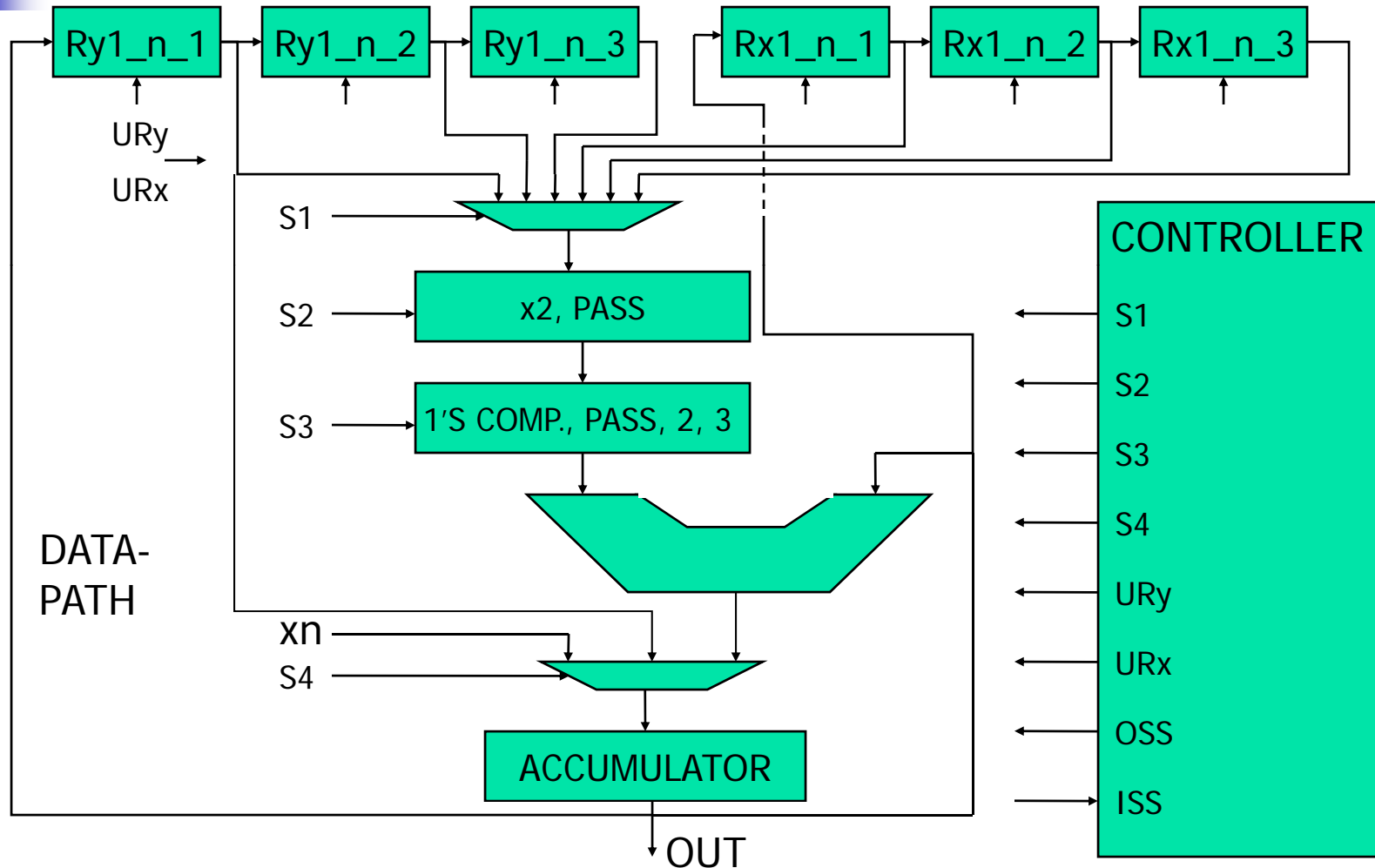

Verilog code for Data_Path

```
// Data_Path
module Data_Path (CLK, reset, xn, URy, URx,
                  S2, S3, S4, S1,
                  OUTPUT);

input CLK, reset, xn, URy, URx, S2;
input [1:0] S3, S4;
input [2:0] S1;
output [15:0] OUTPUT;
```

Verilog code for Data_Path

```

reg [15:0] Ry1_n_1, Ry1_n_2, Ry1_n_3;
reg [15:0] Rx1_n_1, Rx1_n_2, Rx1_n_3;
reg [15:0] ACCUMULATOR;

parameter my_zero = 16'b0000000000000000;

reg [15:0] T1, T2, T3, T4, T5;
reg my_msb;

assign OUTPUT = ACCUMULATOR;

always @ (posedge CLK or reset) begin
  if (reset == 1'b1) begin
    Ry1_n_1 = my_zero; Ry1_n_2 = my_zero; Ry1_n_3 = my_zero;
    Rx1_n_1 = my_zero; Rx1_n_2 = my_zero; Rx1_n_3 = my_zero;
    ACCUMULATOR = my_zero;
  else if (CLK == 1'b1) begin
    if (URy == 1'b1) begin
      Ry1_n_3 = Ry1_n_2; Ry1_n_2 = Ry1_n_1;
      Ry1_n_1 = ACCUMULATOR;
    end
    if (URx == 1'b1) begin
      Rx1_n_3 = Rx1_n_2; Rx1_n_2 = Rx1_n_1;
      Rx1_n_1 = ACCUMULATOR;
    end
    case (S1)
      3'b000 : T1 = Ry1_n_1;
      3'b001 : T1 = Ry1_n_2;
      3'b010 : T1 = Ry1_n_3;
      3'b011 : T1 = Rx1_n_1;
      3'b100 : T1 = Rx1_n_2;
      3'b101 : T1 = Rx1_n_3;
    endcase
    endcase
    case (S2)
      1'b0 :
        my_msb = T1[15];
        T2 = T1 << 1;
        T3 = T2 & 16'b0111111111111111;
        T4 = T3 | {my_msb, 15'b0000000000000000};
      1'b1 : T4 = T1;
    endcase
    endcase
    case (S3)
      2'b00 : T5 = ~T4;
      2'b01 : T5 = T4;
      2'b10 : T5 = 16'b0000000000000010;
      2'b11 : T5 = 16'b0000000000000011;
    endcase
    endcase
    case (S4)
      2'b00 : ACCUMULATOR = {15'b0000000000000000, xn};
      2'b01 : ACCUMULATOR = Ry1_n_1;
      2'b10 : ACCUMULATOR = ACCUMULATOR + T5;
    endcase
  end
end
endmodule

```

Verilog code for Controller

// Controller

```
module Controller (CLK, reset, ISS, URy, URx,  
                  S2, OSS, S3, S4, S1);
```

```
input CLK, reset, ISS;
```

```
output URy, URx, S2, OSS;
```

```
output [1:0] S3, S4;
```

```
output [2:0] S1;
```

Verilog code for Controller

```
parameter S00 = 5'h00, S01 = 5'h01, S02 = 5'h02, S03 = 5'h03,
S04 = 5'h04, S05 = 5'h05, S06 = 5'h06, S07 = 5'h07, S08 = 5'h08,
S09 = 5'h09, S10 = 5'h0A, S11 = 5'h0B, S12 = 5'h0C, S13 = 5'h0D,
S14 = 5'h0E, S15 = 5'h0F, S16 = 5'h10, S17 = 5'h11;
```

```
reg URy, URx, S2, OSS;
reg [1:0] S3, S4;
reg [2:0] S1;
```

```
reg [4:0] PRState, NXState;
```

```
reg [4:0] Counter;
```

```
always @ (PRState) begin
  if (PRState == S09) URy = 1'b1;
  else URy = 1'b0;
  if (PRState == S17) URx = 1'b1;
  else URx = 1'b0;
  if (PRState == S05 || PRState == S06) S1 = 3'b001;
  else if (PRState == S08) S1 = 3'b010;
  else if (PRState == S10 || PRState == S11) S1 = 3'b011;
  else if (PRState == S12 || PRState == S13) S1 = 3'b100;
  else if (PRState == S14) S1 = 3'b101;
  else S1 = 3'b000;
```

```
  if (PRState == S03 || PRState == S05 ||
      PRState == S10 || PRState == S12) S2 = 1'b0;
  else S2 = 1'b1;
  if (PRState == S05 || PRState == S06 ||
      PRState == S10 || PRState == S11 ||
      PRState == S14) S3 = 2'b00;
  else if (PRState == S07) S3 = 2'b10;
  else if (PRState == S15) S3 = 2'b11;
  else S3 = 2'b01;
  if (PRState == S02) S4 = 2'b00;
  else if (PRState == S16) S4 = 2'b01;
  else S4 = 2'b10;
  if (PRState == S15) OSS = 1'b1;
  else OSS = 1'b0;
end
```


Verilog code for Controller

```

always @ (posedge CLK or reset) begin
  if (reset == 1'b1) begin
    PRState = S00;
    Counter = 5'b00000;
  end
  else begin
    PRState = NXState;
    if (Counter == 5'b11111) Counter = 5'b00000;
    else Counter = Counter + 5'b00001;
  end
end
always @ (PRState or ISS) begin
  case (PRState)
    S00 : if (ISS == 1'b1) NXState = S02;
    S01 : if (ISS == 1'b1) NXState = S02;
    S02 : NXState = S03;
    S03 : NXState = S04;
    S04 : NXState = S05;
    S05 : NXState = S06;
    S06 : NXState = S07;
    S07 : NXState = S08;
    S08 : NXState = S09;
    S09 : if (Counter == 5'b00000) NXState = S10;
           else NXState = S01;
    S10 : NXState = S11;
    S11 : NXState = S12;
    S12 : NXState = S13;
    S13 : NXState = S14;
    S14 : NXState = S15;
    S15 : NXState = S16;
    S16 : NXState = S17;
    S17 : NXState = S01;
  endcase
end
endmodule

```

Main Code for FILTER

```
module FILTER (reset, CLK, ISS, xn,  
               OSS, OUTPUT);
```

```
input reset, CLK, ISS, xn;
```

```
output OSS;
```

```
output [15:0] OUTPUT;
```

Main Code for FILTER Cont...

```
wire URy, URx, S2;
```

```
wire [1:0] S3, S4;
```

```
wire [2:0] S1;
```


```
Controller c (.CLK(CLK), .reset(reset),  
             .ISS(ISS), .URy(URy), .URx(URx), .S2(S2),  
             .OSS(OSS), .S3(S3), .S4(S4), .S1(S1));
```

```
Data_Path dp (.CLK(CLK), .reset(reset),  
             .xn(xn), .URy(URy), .URx(URx), .S2(S2),  
             .S3(S3), .S4(S4), .S1(S1), .OUTPUT(OUTPUT));
```


```
endmodule
```

Conclusions


From Gates to Large IP

 

Conclusions

 

Thanks.....

 

hernande@tcnj.edu

<http://www.tcnj.edu/~hernande/>