



“RAPID SYSTEM PROTOTYPING OF ELECTRONIC SYSTEMS:

A VHDL OVERVIEW”

By

Luis E. Navarrete, MSEE

Orlando J. Hernandez, Ph.D.

**Tecnologías de la Información: Telecomunicaciones, Aplicaciones en Procesamiento
Digital de Señales y Diseño Digital con VHDL**

UNIVERSIDAD DEL NORTE

May 21 - 23, 2003

Presentation Overview


- Modern Electronic Design Overview
 - Digital Logic Technologies
 - Programmable Logic Devices - FPGAs
- Introduction to VHDL – Part I
- Introduction to VHDL – Part II
 - AND, OR, HALF ADDER, FULL ADDER
- Introduction to VHDL – Part III
 - ALU Design
- Control and Data Path Organization
 - Finite State Machines, Digital Filter
- Introduction to MAX+PLUS II
- Implementations and Examples on the ALTERA UP1 Board
- Q&A Sessions

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Modern Electronic Design


- Electronic Circuit Design

- Analog Design

 

Analog

- Digital Design

 


Digital

- Analog & Digital  Mixed Signal Design

- Software and Hardware Engineers Plays an Increasing Important Role in Embedded Systems

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Digital Logic Technologies

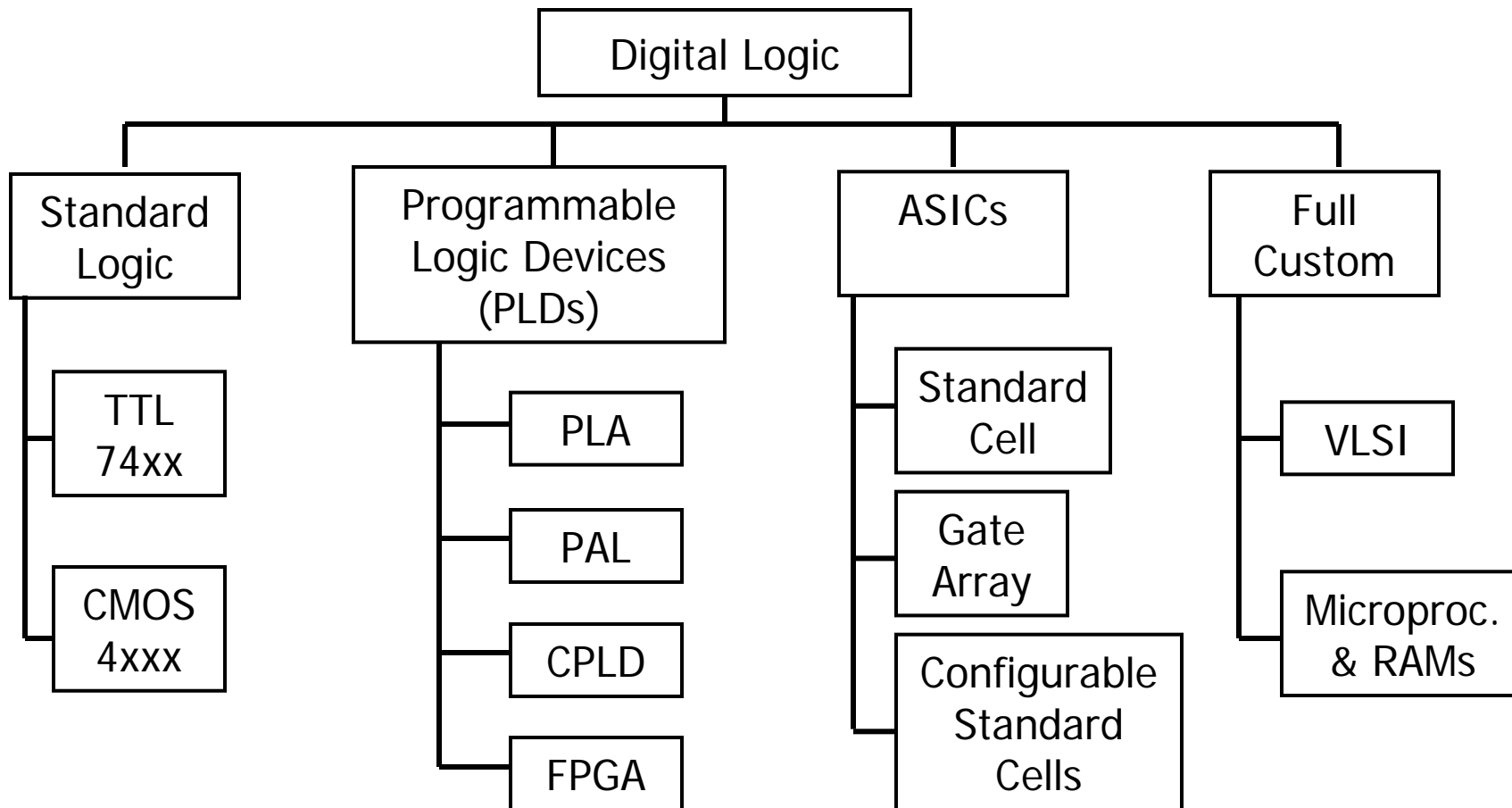

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Digital Logic Technologies

Programmable Logic Devices PLD:

- Chips that contains relatively large amounts of logic circuitry with a structure that is not fixed. Introduced in the 1970's. Several types of PLD's have been available:
 - Programmable Logic Array (PLA)
 - Programmable Array Logic (PAL)
 - Complex Programmable Logic Devices (CPLDs)
 - Field Programmable Gate Arrays (FPGAs)

Digital Logic Technologies


Programmable Logic Array PLA:

- Based on the idea that logic functions can be realized in sum-of-products form.
- A PLA comprises a programmable collection of AND gates that feeds a set of OR gates, configured to realize any sum-of-product functions of the PLA Inputs

Digital Logic Technologies

Programmable Logic Array PLA:

- PLA, Schematic:

 

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE

Digital Logic Technologies

Programmable Array Logic PAL:

- In a PLA both the AND and the OR planes are programmable.
- Historically the programmable switches presents two difficulties for the manufacturers, they are hard to fabricate and reduced speed-performance.

Digital Logic Technologies


Programmable Array Logic PAL:

- These Drawbacks led to the development of a device where only the AND Plane is programmable while the OR plane remains fixed. These devices were called the PALs.

Digital Logic Technologies

Programmable Array Logic PAL:

- PAL, Schematic:

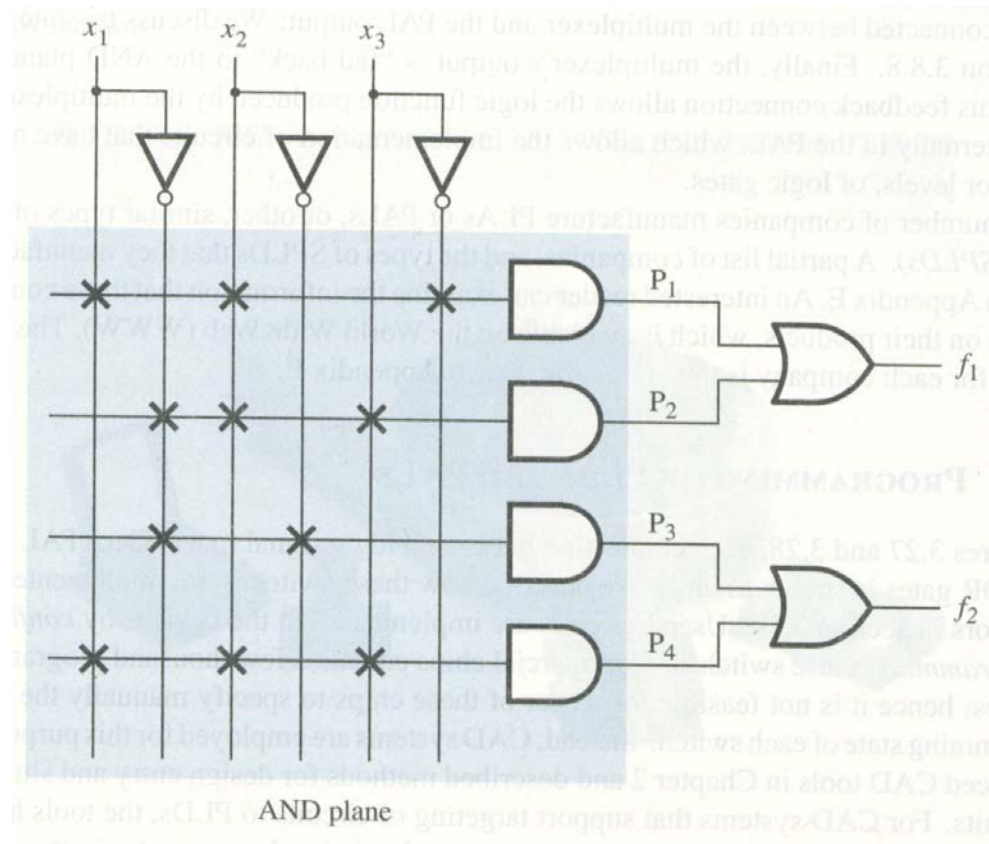

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE

Digital Logic Technologies

Complex Programmable Logic Devices CPLDs:

- CPLDs were created as a substitute for the PLAs and PALs which are useful for implementing a wide variety of small digital circuits.
- This small digital circuits will be limited to a relatively small amount of inputs and outputs.

Digital Logic Technologies


Complex Programmable Logic Devices CPLDs:

- For implementing more complex circuits, either multiple PLAs or PALs can be used or a CPLD.
- A CPLD comprises multiple circuit blocks on a chip, with internal wiring resources to connect the circuit blocks. Each circuit block is similar to a PLA or a PAL.

Digital Logic Technologies

Complex Programmable Logic Devices CPLDs:

- CPLDs, Schematics:

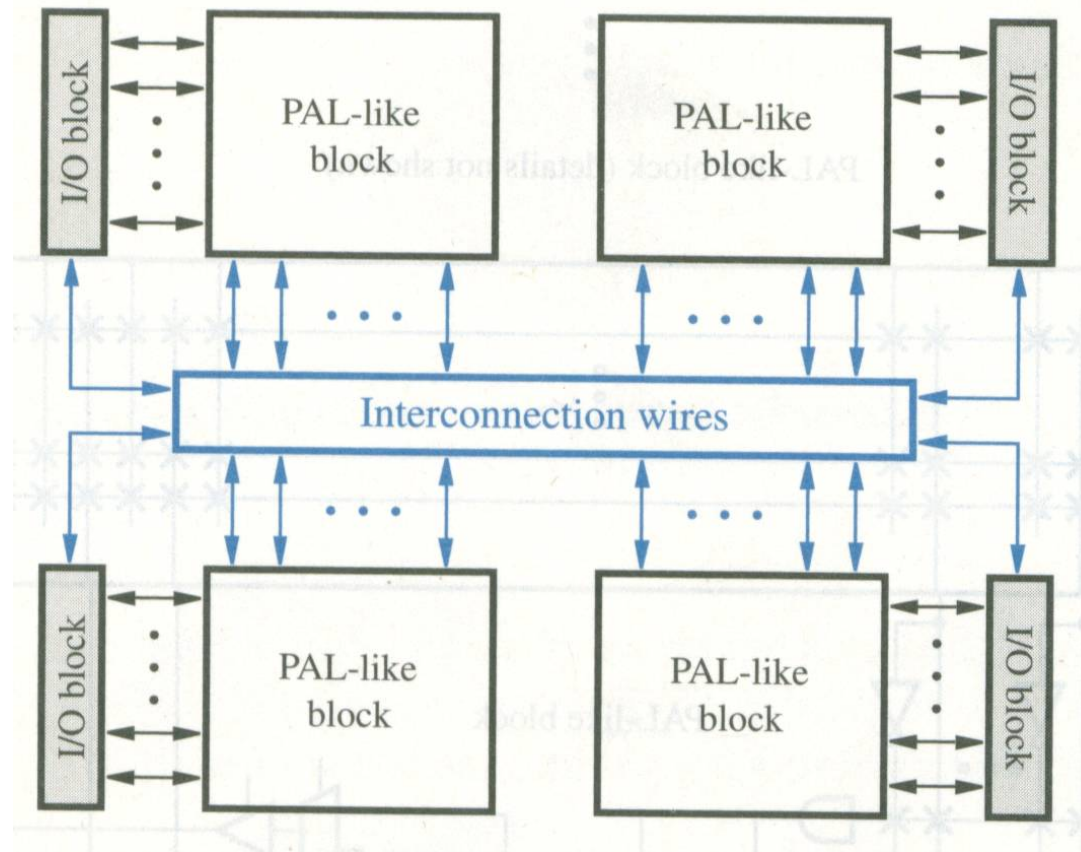

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE

May 21 - 23, 2003

13

Digital Logic Technologies

Field Programmable Gate Arrays FPGAs:

- Is a programmable logic device that supports implementation of relatively large logic circuits (Much more than 20,000 gates).
- FPGAs, does not contains AND or OR planes as the CPLDs. Instead, FPGAs provide logic blocks for implementation of the required functions.

Digital Logic Technologies


Field Programmable Gate Arrays FPGAs:

- They contain tree main types of resources:
 - Logic Blocks
 - I/O blocks for connecting to the package pins
 - and interconnection wires and switches
- More sophisticated state of the art FPGAs also contain:
 - Complex I/Os
 - Memories
 - Analog
 - Custom laid out processors

Digital Logic Technologies

Field Programmable Gate Arrays FPGAs:

- FPGAs, Schematics:

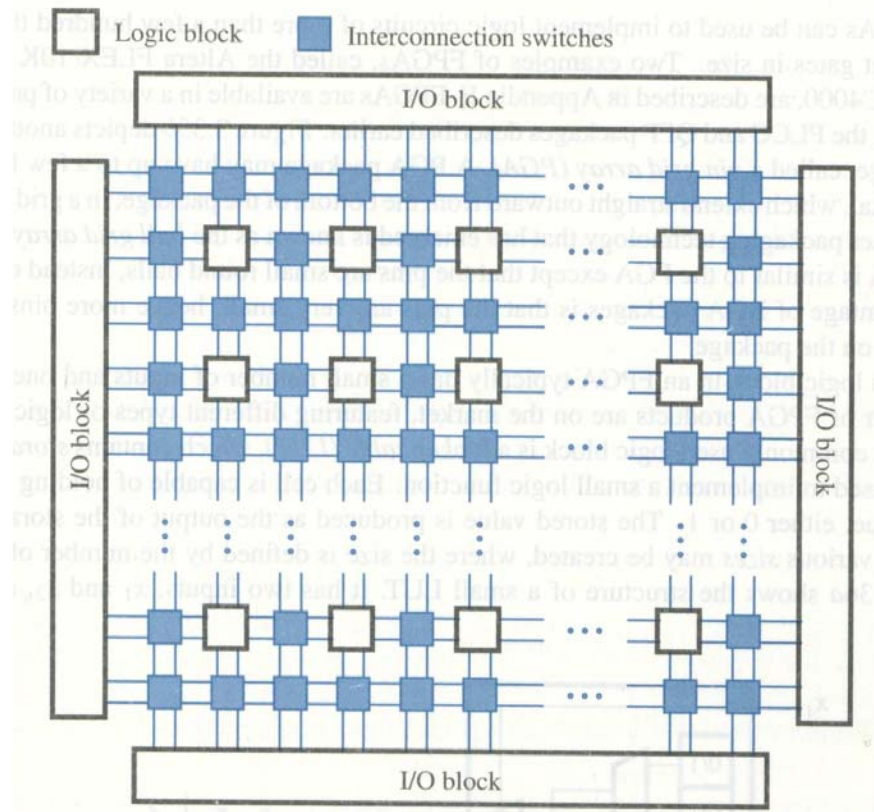

Digital Logic Technologies

Application Specific Integrated Circuit, ASICs:

- Chips that are design using state of the art VLSI technologies and that are tailored to some specific needs (or applications).
- In the 1980's Application Specific Integrated Circuits (ASIC) designs were focused to meet time-to-market and customers specific requirements.

Digital Logic Technologies

Application Specific Integrated Circuit, ASICs:

- There are several integrated circuits design options:
 - Standard Cell Design
 - Gate Array(are among the main ones).
- Emerging technologies are combining the density and cost efficiency of standard cells with the flexibility and quick design times of gate arrays: configurable standard cells

Digital Logic Technologies

Standard Cell Design:

- Is a design methodology where a library of macros (cells), which are predefined and pre-laid-out, is provided by a vendor.
- The user designs his/her circuit with these cells (logic function blocks) resulting in a schematic defining the interconnects among selected cells.

Digital Logic Technologies

Standard Cell Design:


- Typical libraries are created with low gate level primitives such as: AND, OR, NAND, NOR, XOR, Inverters, flip-flops, registers and other similar components.

Digital Logic Technologies

Gate Array Design:

- The Gate Array design uses a custom interconnection pattern of an array of uncommitted logic gates. These are called Gate Arrays.
- Wafers of chips containing the uncommitted logic gate arrays can be pre-fabricated up to the point of the final metallization steps which creates the logic personalization.

Digital Logic Technology Tradeoffs

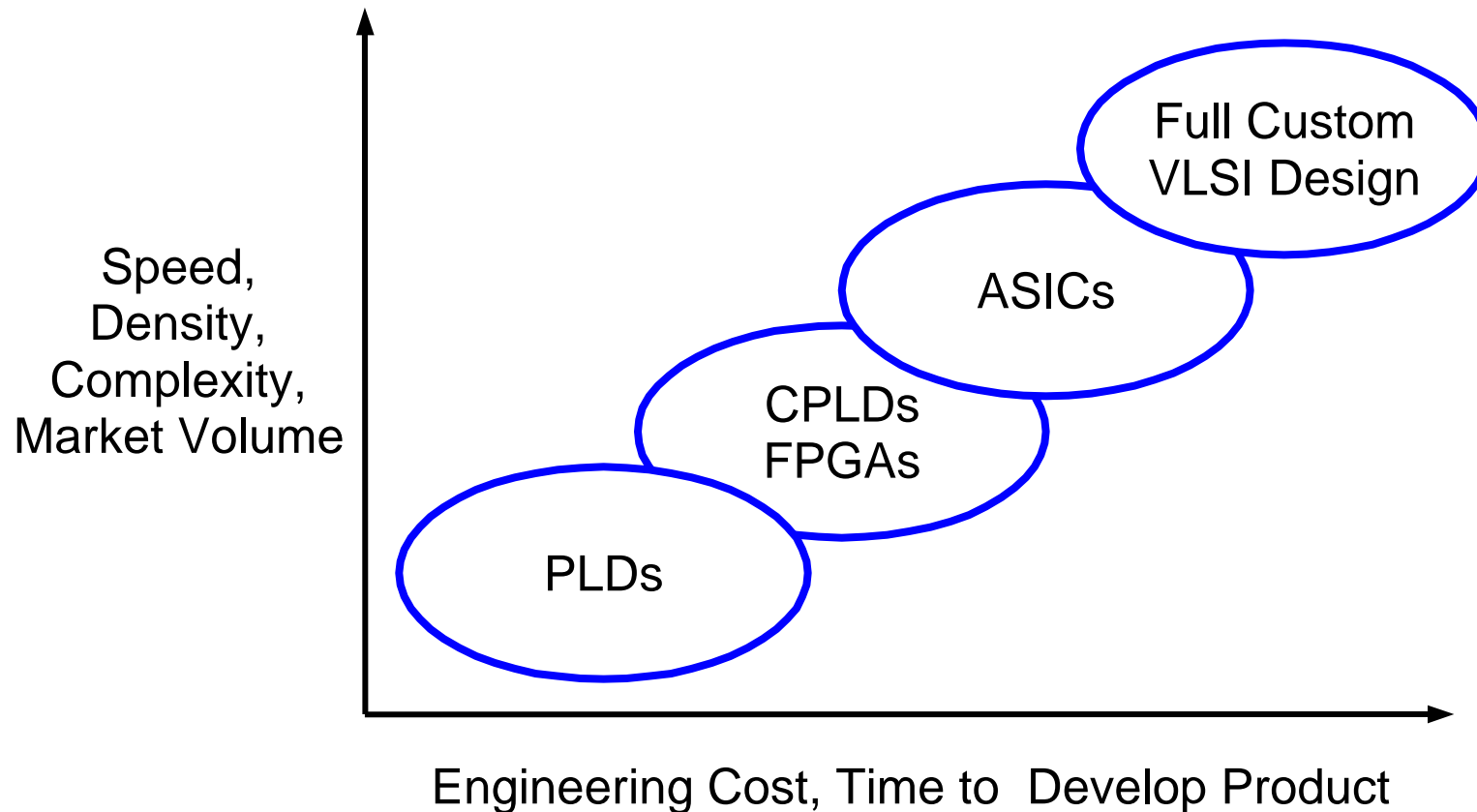


Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Field Programmable Logic Arrays, FPGAs


- FPGAs are Integrated Circuits Whose Internal Functional Operation is Defined by the User
- **RAPID SYSTEM PROTOTYPING OF ELECTRONIC SYSTEMS.**
- They can be Programmed using a Hardware description Language, VHDL

UP1 Development Board

www.altera.com

 

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

 

Session I





INTRODUCTION TO VHDL – PART I

Design Automation

- Need To Keep With Rapid Changes, Electronic Products Have To Be Designed Extremely Quickly
- Electronic Design Automation (EDA)
 - Design Entry
 - Simulation
 - Synthesis
 - Design Validation & Test

Design Automation. Cont...

- Design Entry
 - Schematic Capture

    

Design Automation. Cont...

- Design Entry - Textual Form:
 - **VHDL** (**V**HSIC **H**ardware **D**escription Language)
 - **VHSIC** (**V**ery **H**igh **S**peed **I**ntegrated Circuits)

Design Automation. Cont...

- Design Entry - Textual Form:

```
entity and_2 is
    port (X, Y:in BIT; Z:out BIT);
end entity and_2;
```

```
architecture DATAFLOW of and_2 is
begin
    Z <= X and Y;
end architecture DATAFLOW;
```

Introduction To VHDL

- VHDL: **V**ery High Speed Integrated Circuit (VHSIC) **H**ardware **D**escription **L**anguage.
- VHDL Is an Industry Standard Language to Describe Hardware From the Abstract to Concrete Level.

BRIEF HISTORY OF VHDL

- VHDL is a Derivative of the VHSIC Program by US Dept. of Defense Along With IBM, Texas Instruments, and Intermetrics.
- In 1986 VHDL Became IEEE Standard and After Several Revisions. It Was Adopted As the IEEE 1076 Standard.

BRIEF HISTORY OF VHDL

- In 1999 the Analog and Mixed Signal Extensions Were Added to VHDL (VHDL-AMS)
- In 2000 the latest upgrade (Object Oriented added...)

MOTIVATION


- Need a Method to Quickly Design, Implement, Test and Document Increasingly Complex Digital Systems.
- Schematic and Boolean Equations Inadequate for Million-Gate ICs.
- Design Portability

What is VHDL?

- A Design entry language
- A Simulation modeling language.
- A Verification language.
- A Standard language.
- As simple or complex as required.


How is VHDL Used?

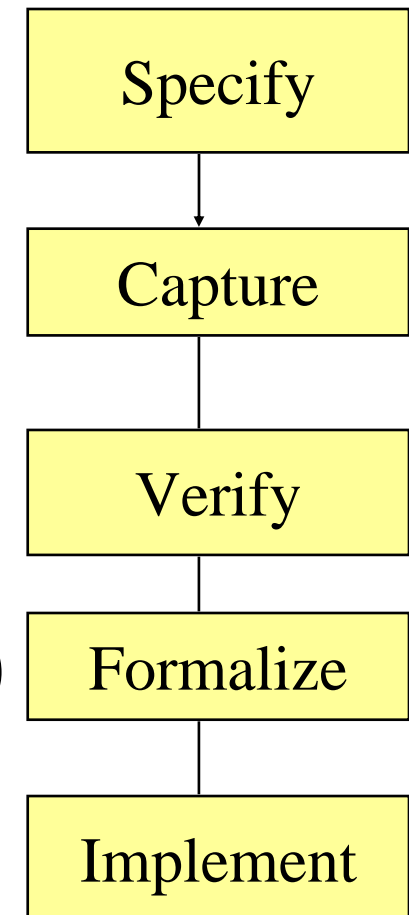- For Design Specification ("Specify")
- For Design Entry ("Capture")
- For Design Simulation ("Verify")
- For Design Documentation ("formalize")
- As an Alternate to Schematics



FPGA Design Process

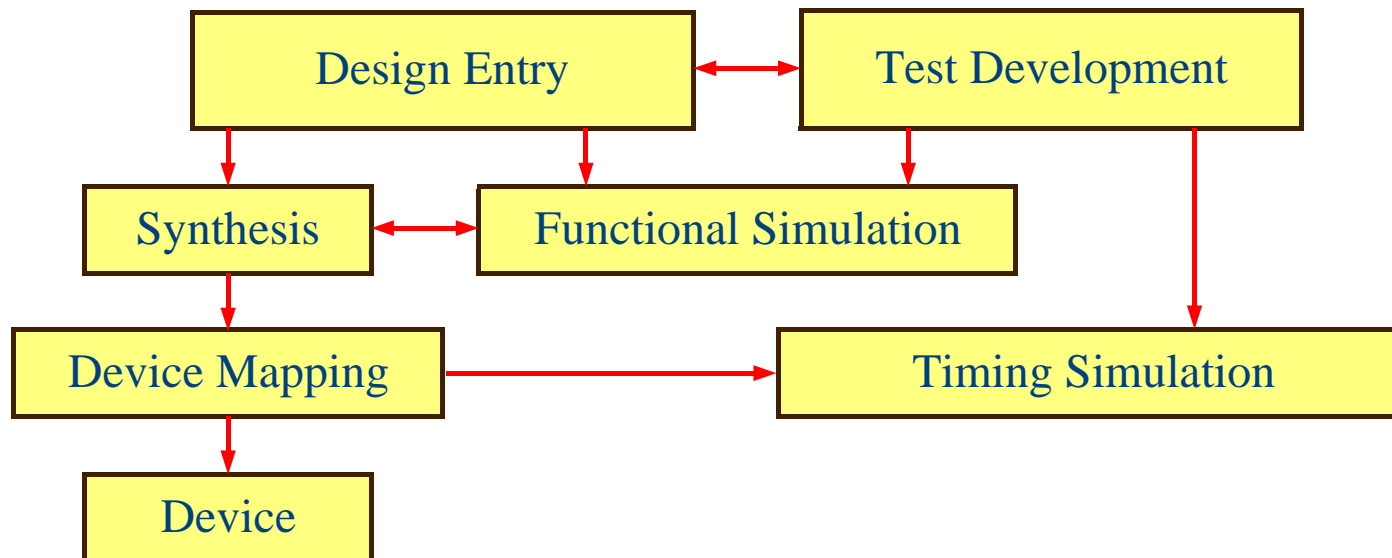- VHDL Can Be Used for Both Design and Test Development



When Should VHDL Be Used?

- VHDL is highly beneficial to use as a structured, top down approach to design.
- VHDL makes it easy to build, use, and reuse libraries of circuit elements.
- VHDL can greatly improve your chances of moving into more advanced tools and device targets.

Advantages of VHDL

- The Ability to Code the Behavior and to Synthesize an Actual Circuit.
- Power and Flexibility
- Device (specific FPGA) Independent Design

Advantages of VHDL Cont...

- Portability Among Tools and Devices
- Fast Switch Level Simulations
- Quick Time to Market and Low Cost
- Industry Standard

Getting Started with VHDL

- Its Easy To Get Started With VHDL, But Its Difficult To Master It.
- To Begin With, A Subset of The Language Can Be Learned To Write Useful Models.
- Later More Complex Features Can Be Learned To Implement Complex Circuits.

A First look at VHDL


- Lets start with a simple Combinational circuit: an 8-bit Comparator.

An 8 Bit Comparator

- Comparator Specifications:
 - Two 8-bit inputs
 - 1-bit Output
 - Output is 1 if the inputs match or 0 if they differ.

An 8 Bit Comparator

Comparator

 

	0	1	2	3	4	5	6	7
A	1	0	1	1	0	0	1	1
B	1	0	1	1	0	0	1	1

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE

Comparator VHDL Source Code

-- Eight-bit Comparator

entity compare **is**

port (A, B : **in** std_logic_vector (0 **to** 7);

EQ : **out** std_logic);

end compare;

architecture comp **of** compare **is**

begin

EQ <= '1' **when** (A=B) **else** '0';

end comp;

- **An entity declaration that defines the inputs and outputs - the ports of the circuit**
- **An architecture that defines the function of the circuit**

Entities and Architectures

- Every VHDL design description has at least one entity/architecture pair.
- A large design has many entity / architecture pairs and are connected to form the complete circuit.

What is an Entity?

- An entity declaration describes the circuit as it appears from “outside” - from perspective of its input and output interfaces.
- An entity declaration is analogous to a block symbol on a schematic.

What is an Entity?

```
entity compare is
```

```
    port (A, B : in std_logic_vector (0 to 7);
```

```
        EQ : out std_logic);
```

```
end compare;
```

- The entity declarations includes a name, compare, and a port statement defining all the inputs and outputs of the entity.

What is an Architecture?

- Architecture Describes the Actual Function - or Contents of the Entity to Which It Is Bound.
- Architecture Is Roughly Analogous to a Lower Level Schematic Referenced by the High Level Functional Block Symbol.

What is an Architecture?

```
architecture comp of compare is  
begin
```

```
EQ <= '1' when (A=B) else '0';  
end comp;
```

- The architecture declaration begins with a unique name, comp, followed by the name of the entity to which the architecture is bound, in this case compare.

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

What is an Architecture?

```
architecture comp of compare is  
begin
```

```
EQ <= '1' when (A=B) else '0';  
end comp;
```

- Between the keywords **begin** and **end** is found the actual functional description of the comparator.


Data Types

- VHDL's high level data types allow data to be represented in much the same way as in high-level programming languages.
- A data type is an abstract representation of stored data.

Data Types

- These data types might represent individual wires in a circuit, or a collection of wires.

Data Types

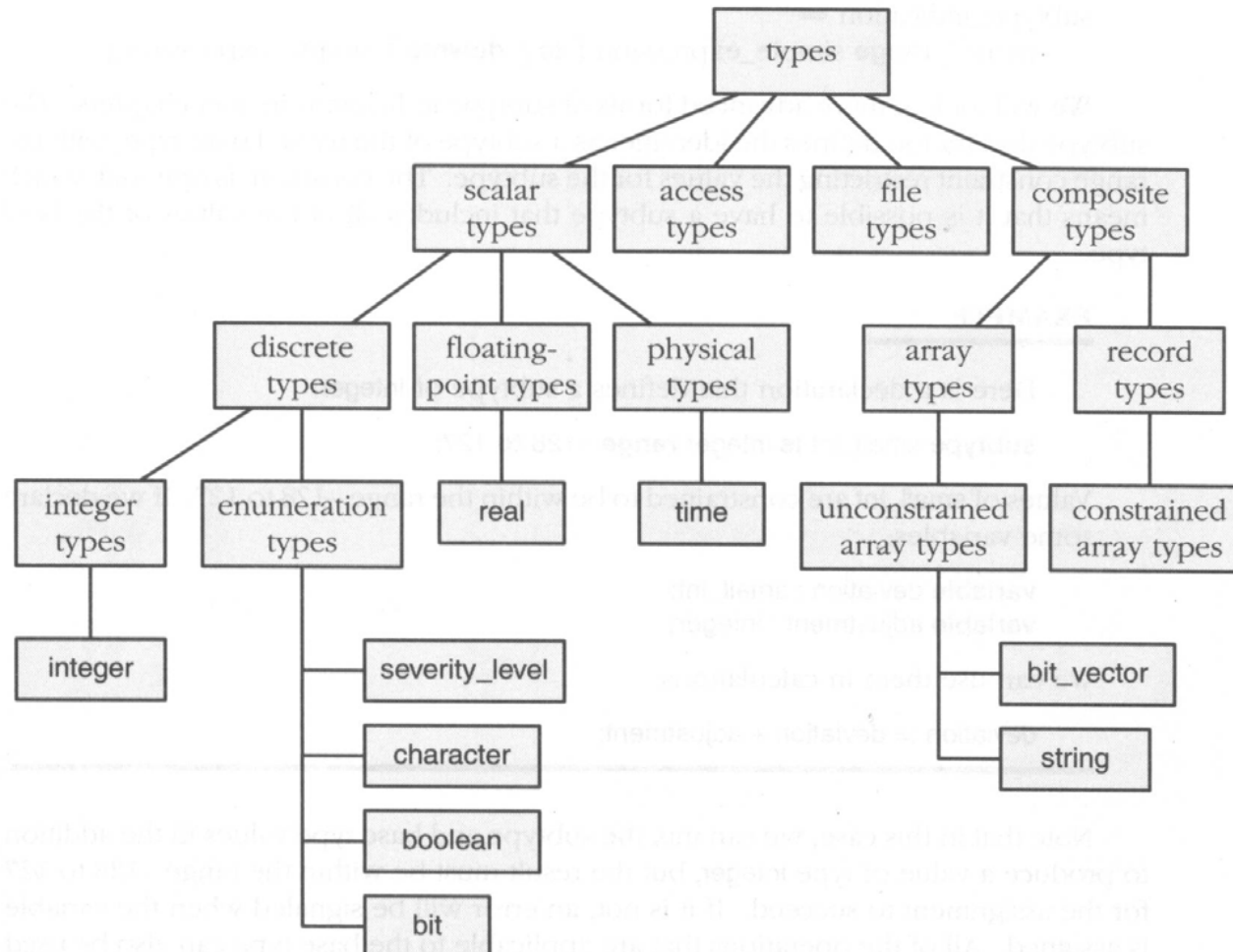


Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Data Types

Data Type	Values	Examples
Bit	'1', '0'	Q <= '1';
Bit_vector	(array of bits)	Data <= "101001"
Boolean	True, False	EQ <= True ;
Integer	-2, -1, 0, 1, 2, 3	C <= c+2;
Real	1.0, -1.0E5	V1 = V2/5.3;
Time	1ua, 100ps	Q <= '1' after 6 nS
Character	'a', 'b', '2', '\$'	Char <= 'X';
String	(Array of characters)	Msg <= "MEM";

Design Units

 - Design units are a concept unique to VHDL that provide advanced configuration management capabilities.
- Design units are segments of VHDL code that can be compiled separately and stored in a library.



Design Units

Design Units

**Configuration
(or default configuration)**

Package

Package Body

Entity

Architecture (s)

Package Design unit

- A Package is a collection of commonly used data types to be used globally among different design units.
- Package declaration is identified by the *package* keyword.

Package Design Unit

- Items defined within a package can be made visible to any other design unit in the complete VHDL design and they can be compiled into libraries for later re-use.
- A package can consist of two basic parts
 - A package declaration
 - A package body (optional)

Package Design unit

- Syntax of package

```
package my_package is  
    function my_global_function ( ..... )  
    return bit;  
end my_package;
```

Package Body

- The package body defines the actual behavior of the items specified in the package.
- The relationship between package and package body is somewhat similar to that of entity and its corresponding architecture.

VHDL Configurations

- VHDL allows you to create more than one alternate architecture for an entity.
- This feature helps in experimenting with different implementations of circuit description.
- Its also useful for simulation and for project team environments.


VHDL Configurations

- Configuration declarations are not generally used for synthesis, and may not be supported by the synthesis tools.
- Configuration declarations are always optional, even for complex circuits.

VHDL Configurations


- An example of configuration declaration
 
```
configuration t_build of rcomp is  
  for structure  
    for COMP1: compare use entity  
      work.compare (comp);  
    for ROT1: rotate use entity  
      work.rotate (rotate1);  
  end for;  
end t_build;
```



Design Description

More Typical Design Description

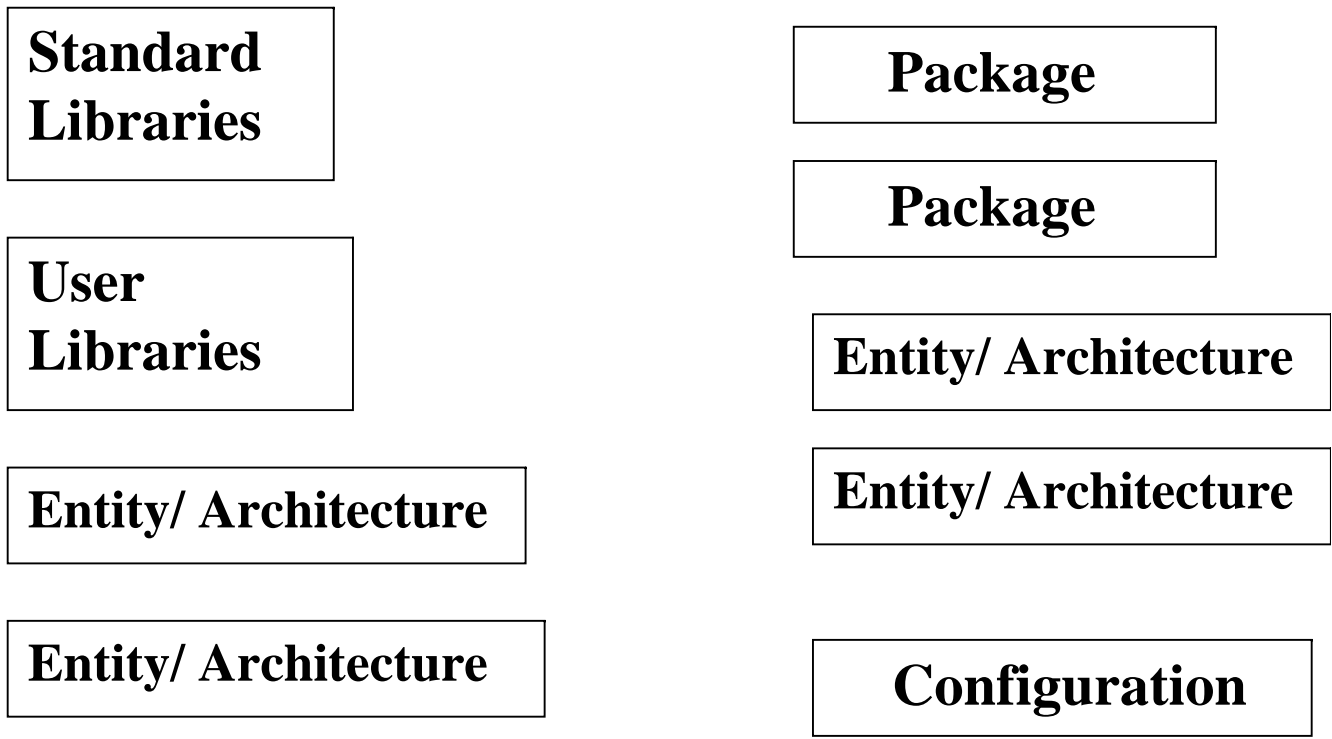

Levels of Abstraction (Styles)

- VHDL supports many possible styles of design description.
- These styles differ primarily in how closely they relate to the underlying hardware.

Levels of Abstraction (Styles)

- Levels of Abstraction refers to how far your design description is from an actual hardware realization.
- The three main levels of abstraction are:
 - Behavior
 - Dataflow (RTL)
 - Structure

Levels of Abstraction (Styles)

Behavior

Dataflow

Structure



Performance Specification
Test Benches
Sequential Description
State Machines
Register Transfers
Selected Assignments
Arithmetic Operation
Boolean Equations
Hierarchy
Physical Information

Behavioral Modeling

- The Highest Level of Abstraction Supported in VHDL .
- The Behavior Approach Describes the Actual Behavior of Signals Inside the Component.

VHDL Timing Issues

- The Concept of Time Is the Critical Distinction Between Behavioral Descriptions and Low Level Descriptions.
- The Concept to Time May Be Expressed Precisely, With Actual Delays Between Related Events

An Example of Behavioral Modeling: A half adder



half_adder

- Half_adder
- Inputs a, b : 1 bit each.
- Output Sum, Carry : 1 bit each.

 


Figure 1-1 Half adder circuit

VHDL Code for half_adder

-- Half Adder

library IEEE; --refer IEEE library.

use IEEE.std_logic_1164.**all**;

entity half_adder **is**

port (a, b : **in** std_logic; --declaring I/O ports
 sum, carry : **out** std_logic);

end half_adder;

half_adder code (cont...)

architecture behavior of
half_adder is

begin

sum <= (a xor b);

carry <= (a and b);

end behavior;

 


Figure 1-1 Half adder circuit



Max+Plus II

Development Software

- MAX+PLUS II is a Development software created by ALTERA
- This software supports schematic capture and text-based hardware description language (HDL) design entry, including Verilog® HDL, VHDL, and the Altera® Hardware Description Language (AHDLTM)



Max+Plus II

Development Software

- It also provides design programming, compilation, and verification support for all devices supported by the MAX+PLUS II BASELINE software including the EPM7128S, EPF10K20, and EPF10K70 devices



Max+Plus II

Development Software

- The MAX+PLUS II University software can be freely distributed to students for installation on their personal computers and provides instant access to online help.
- For more information, follow the University Program Link at www.altera.com




Max+Plus II

Development Software

- This Tool was created to help during the various implementation steps:
 - Design
 - Graphical Entry
 - VHDL Model
 - Compilation
 - Simulation
 - Verification
 - Synthesis

Max+Plus II


Main Window

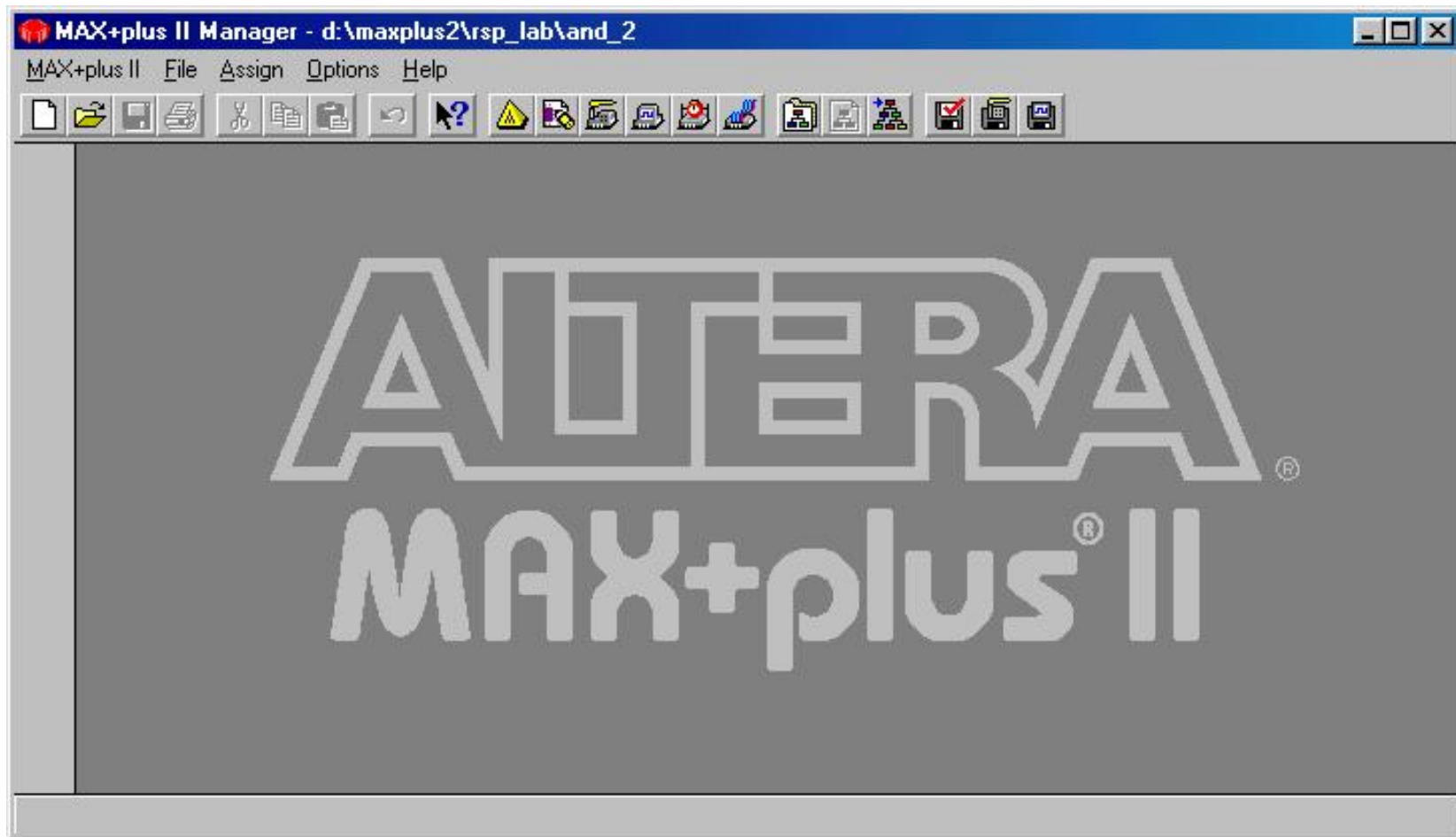

Max+Plus II

1st Part of The Process !!!!

Design

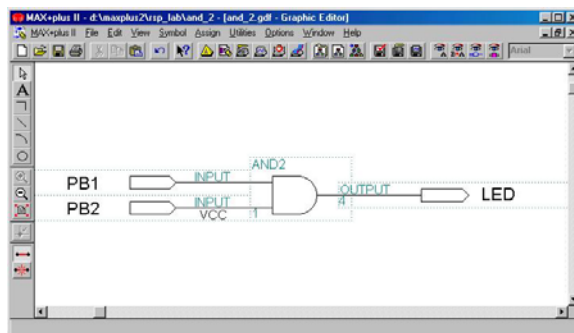


Graphical Entry

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
  
entity and_2 is  
  port (X, Y:in BIT; Z:out BIT);  
end entity and_2;  
  
architecture DATAFLOW of and_2 is  
  begin  
    Z <= NOT((NOT X) and (NOT Y));  
  end architecture DATAFLOW;
```

HDL Model

Compilation

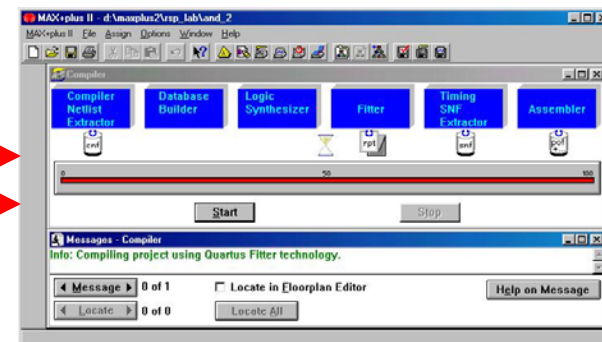


Compiler

Max+Plus II


2nd Part of The Process !!!!

Simulation

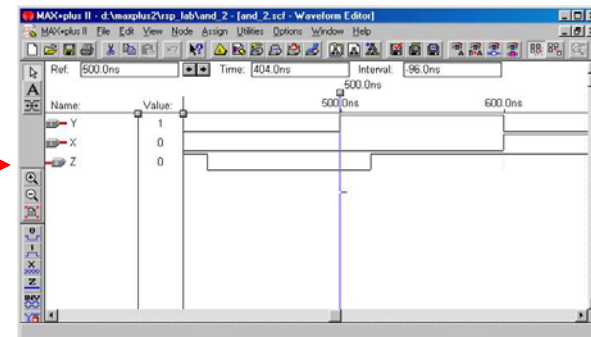


Timing Diagram

Compilation

 

Compiler

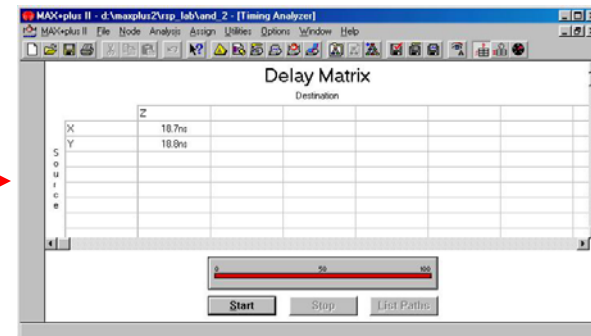


Timing Analysis


Max+Plus II

3rd Part of The Process !!!!

Verification

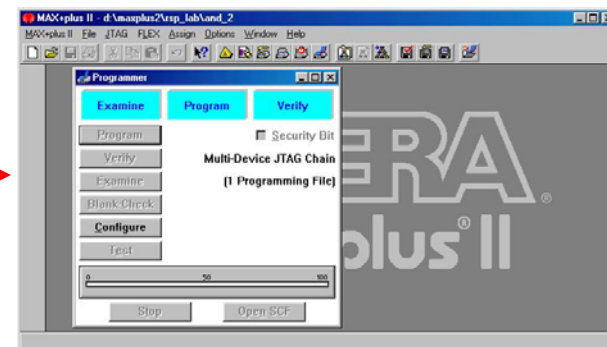


Programming

 

UP1 Board

Compilation

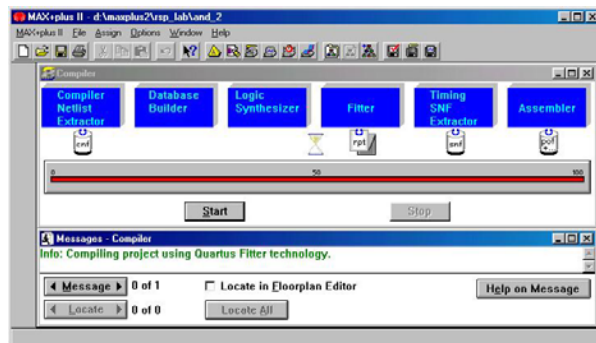

Compiler




Max+Plus II

Development Software

- MAX+PLUS II University software targets the UP1 and UP1X development boards.
- the FLEX10K and MAX7000S devices can be configured and programmed (respectively) to interact with the included hardware or with any other external design.

Max+Plus II Development Software

 

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE

May 21 - 23, 2003




Max+Plus II

Half-Adder

- We will use our previous Half-Adder model as an example of how to perform a VHDL code entry.

Max+Plus II

Half-Adder, Code Entry

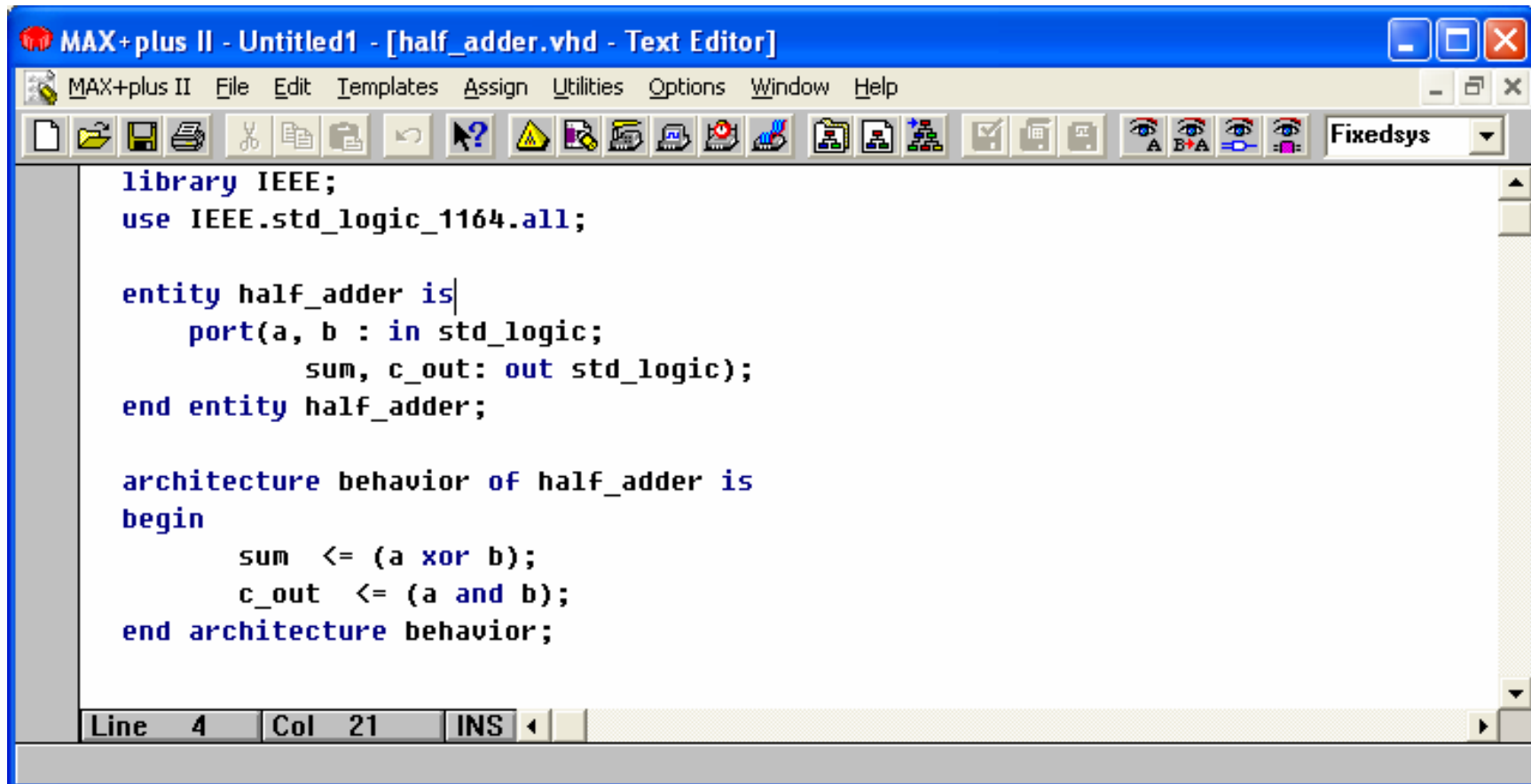

```
MAX+plus II - Untitled1 - [half_adder.vhd - Text Editor]
MAX+plus II  File  Edit  Templates  Assign  Utilities  Options  Window  Help
Library IEEE;
use IEEE.std_logic_1164.all;


entity half_adder is
    port(a, b : in std_logic;
         sum, c_out: out std_logic);
end entity half_adder;

architecture behavior of half_adder is
begin
    sum <= (a xor b);
    c_out <= (a and b);
end architecture behavior;
```

Line 4 Col 21 INS


Max+Plus II


Half-Adder, Compiler

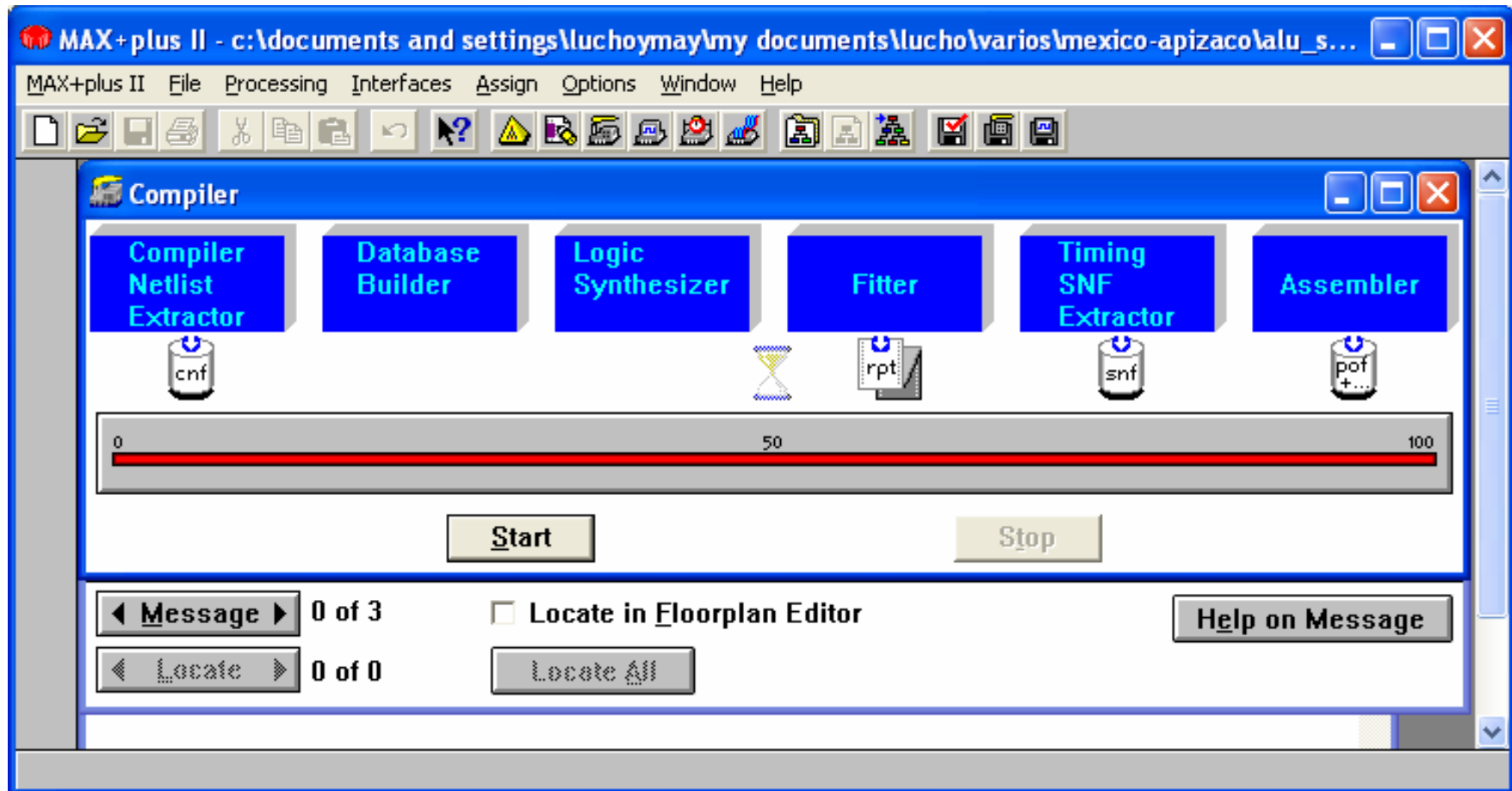

Max+Plus II

Half-Adder, Simulation

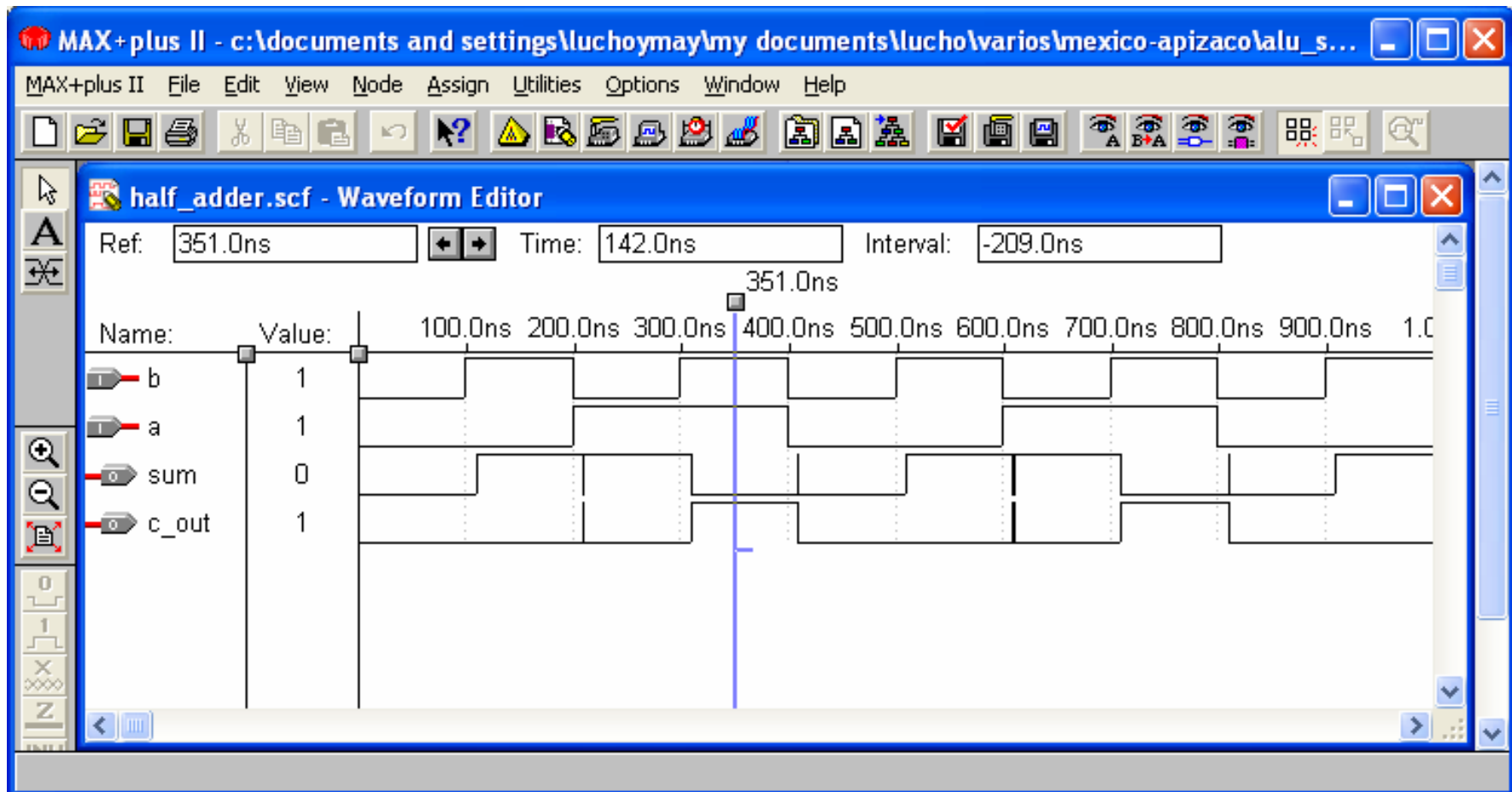

 

Session II

INTRODUCTION TO VHDL – PART II

Dataflow (RTL) Modeling

- The dataflow level of abstraction is often called **R**egister **T**ransfer **L**anguage (**RTL**).
- The dataflow level of abstraction describes how information is passed between registers in the circuit.


Concurrent and Sequential VHDL

- VHDL Allows Both Concurrent and Sequential Statements to Be Entered.
- The Difference Between Concurrent and Sequential Statements Must Be Known for Effective Use of the Language.

Concurrent VHDL

- All Statements in the Concurrent Area Are Executed at the Same Time.
- There Is No Significance to the Order in Which Concurrent Statements Occur.

Concurrent VHDL

 


Example of Concurrent VHDL

Full Adder



Full Adder circuit

 

VHDL code for Full Adder

```
-- Full_Adder  
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity full_adder is  
port (a, b, c_in : in std_logic;  
       sum, c_out : out std_logic);  
end full_adder;
```

VHDL code for Full Adder

```

architecture dataflow of full_adder is
signal s1, s2, s3 : std_logic;
begin
  L1: s1 <= (a xor b);
  L2: s2 <= (c_in and s1);
  L3: s3 <= (a and b);
  L4: sum <= (s1 xor c_in);
  L5: c_out <= (s2 or s3);
end dataflow;
  
```

-- Using Signal Assignment Instructions




Max+Plus II

Full-Adder

- Next we will use MAX+PLUS II to Compile and Simulate our previous Full-Adder model.

Max+Plus II


Full-Adder, Code Entry

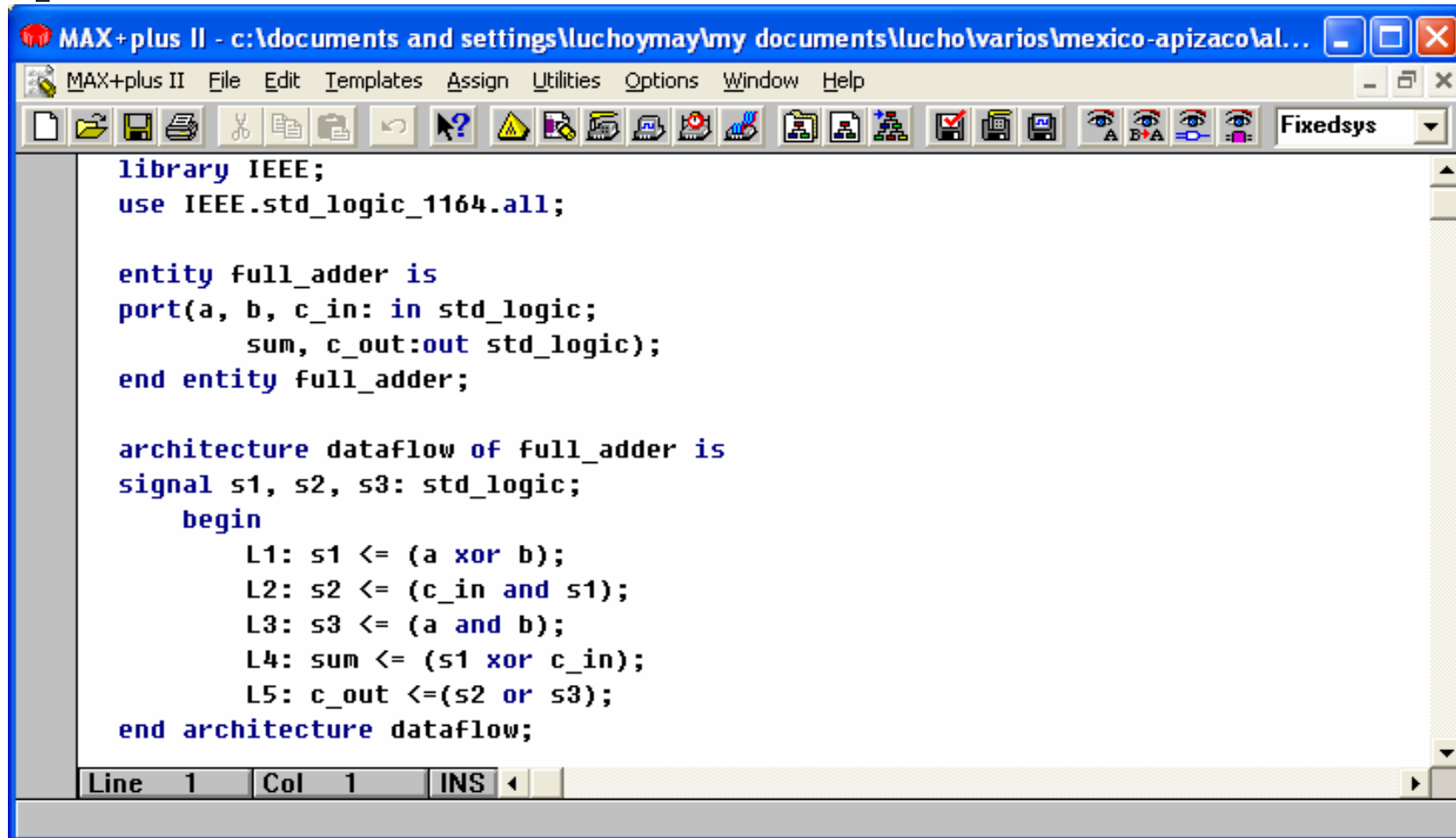

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity full_adder is  
port(a, b, c_in: in std_logic;  
      sum, c_out:out std_logic);  
end entity full_adder;  
  
architecture dataflow of full_adder is  
signal s1, s2, s3: std_logic;  
begin  
    L1: s1 <= (a xor b);  
    L2: s2 <= (c_in and s1);  
    L3: s3 <= (a and b);  
    L4: sum <= (s1 xor c_in);  
    L5: c_out <=(s2 or s3);  
end architecture dataflow;
```


Max+Plus II

Full-Adder, Compiler

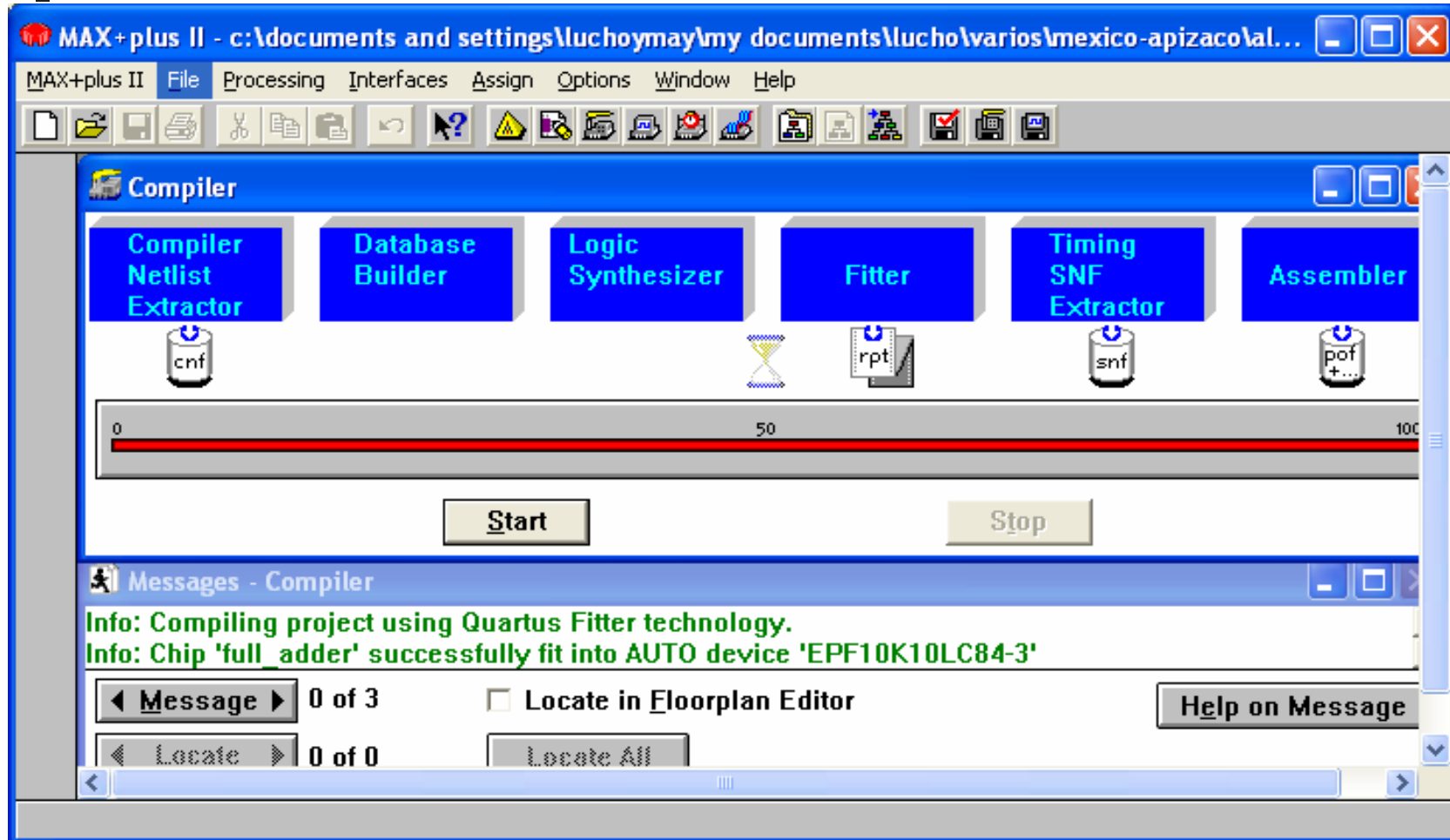

Max+Plus II

Full-Adder, Simulation

 

VHDL code for Full Adder

- The expressions labeled L1-L5 are all concurrent signal assignment statements. All the statements are executed at the same time.

L1: $s1 \leq (a \text{ xor } b);$

L2: $s2 \leq (c_in \text{ and } s1);$

L3: $s3 \leq (a \text{ and } b);$

L4: $sum \leq (s1 \text{ xor } c_in);$


L5: $c_out \leq (s2 \text{ or } s3);$

VHDL code for Full Adder

- The simulator evaluates all the expressions, L1-L5, then applies the results to the signals.
- Once the simulator has applied the results it waits for one of the signal to change and it reevaluates all the expression again.

VHDL code for Full Adder

 - This cycle will continue until the simulation is completed.
- This is called “event driven simulation”.
- It is more computationally efficient than time driven simulation.




Signals

- In the Full_adder VHDL code we came across “signal”.

```
architecture dataflow of full_adder is  
  signal s1, s2, s3: std_logic;  
  begin  
    .....  
end dataflow;
```

- So what are “signals”?

 


Signals

- Signals Are Used to Carry Data From Place to Place in a VHDL Design Description.
- Signals Are Similar to Wires in a Schematic.
- Signals are internal to an entity, so they exist only in the architectures.

Sequential VHDL

- Sequential Statements Are Executed One After the Other in the Order That They Appear.
- Example of Sequential Statement: Process.

Sequential VHDL

 

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE

Process Construct

- The Process construct is the primary means to describe sequential operations.
- Process starts with the keyword *process* and ends with the keyword *end process*.
- The *process* construct itself is treated as a concurrent statement.

Process Statement

- The *process* consists of three parts
 - Sensitivity List
 - Process declaration part
 - Statement Part

Syntax of Process Statement

```
architecture arch_name of ent_name is  
begin
```

```
    process_name: process (sensitivity_list)
```

```
        local_declaration;
```

```
        .....
```

```
        begin
```

```
            sequential statement;
```

```
            sequential statement;
```

```
            .....
```

```
        end process;
```

```
end arch_name;
```

Process Example


```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity nand2 is  
    port (a, b : in std_logic;  
          c : out std_logic);  
end nand2;  
architecture arch1 of nand2 is  
    begin  
        process (a, b)  
            variable temp: std_logic;
```

Process Example

```
begin  
    temp = not (a and b);  
    if (temp = '1') then  
        c <= temp after 5 ns;  
    elseif (temp = '0') then  
        c <= temp after 6 ns;  
    end if;  
end process;  
end arch;
```


Max+Plus II

Nand2, Code Entry

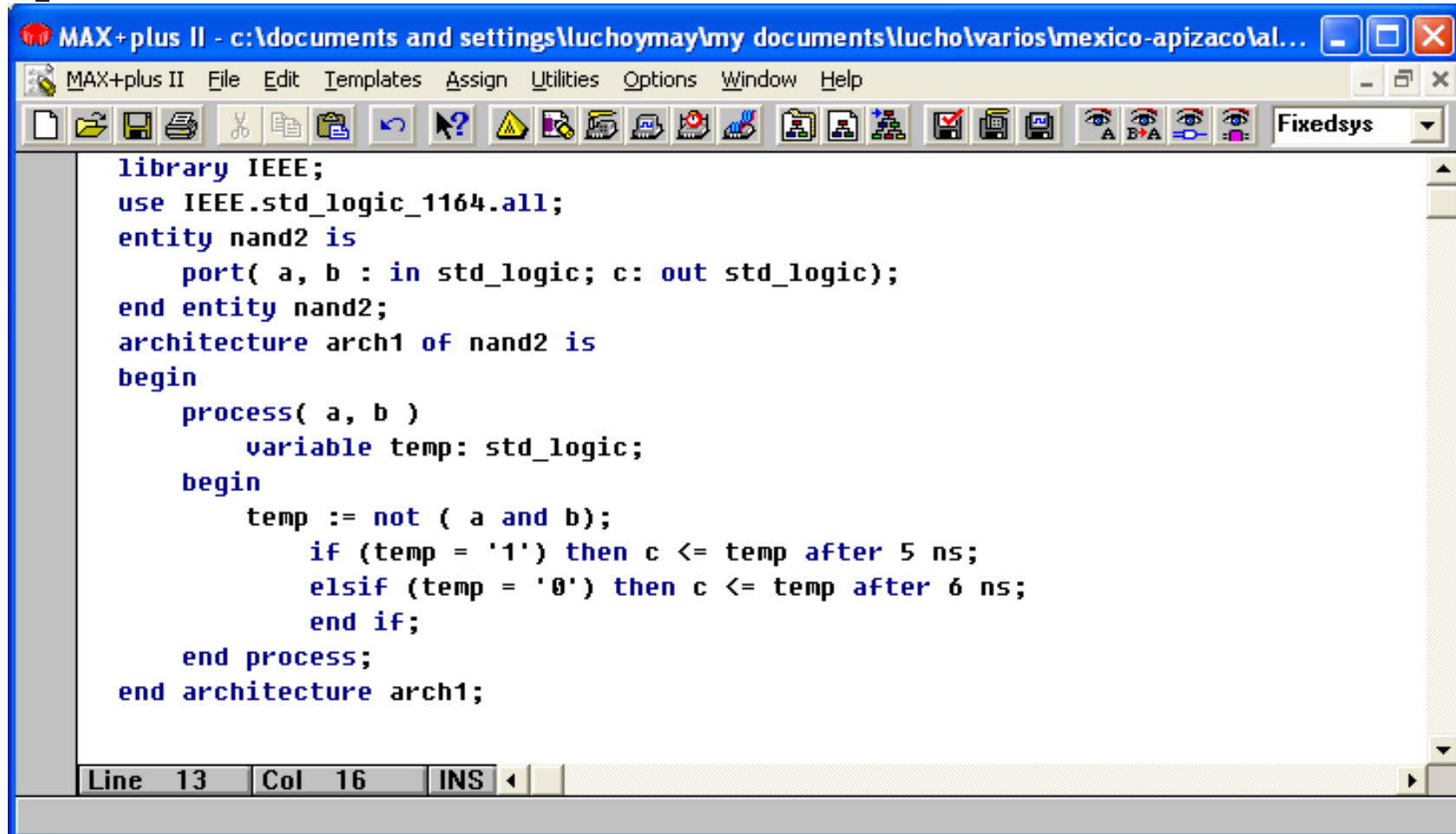


```
library IEEE;
use IEEE.std_logic_1164.all;
entity nand2 is
    port( a, b : in std_logic; c: out std_logic);
end entity nand2;
architecture arch1 of nand2 is
begin
    process( a, b )
        variable temp: std_logic;
    begin
        temp := not ( a and b);
        if (temp = '1') then c <= temp after 5 ns;
        elsif (temp = '0') then c <= temp after 6 ns;
        end if;
    end process;
end architecture arch1;
```

Line 13 Col 16 INS


Max+Plus II

Nand2, Compiler

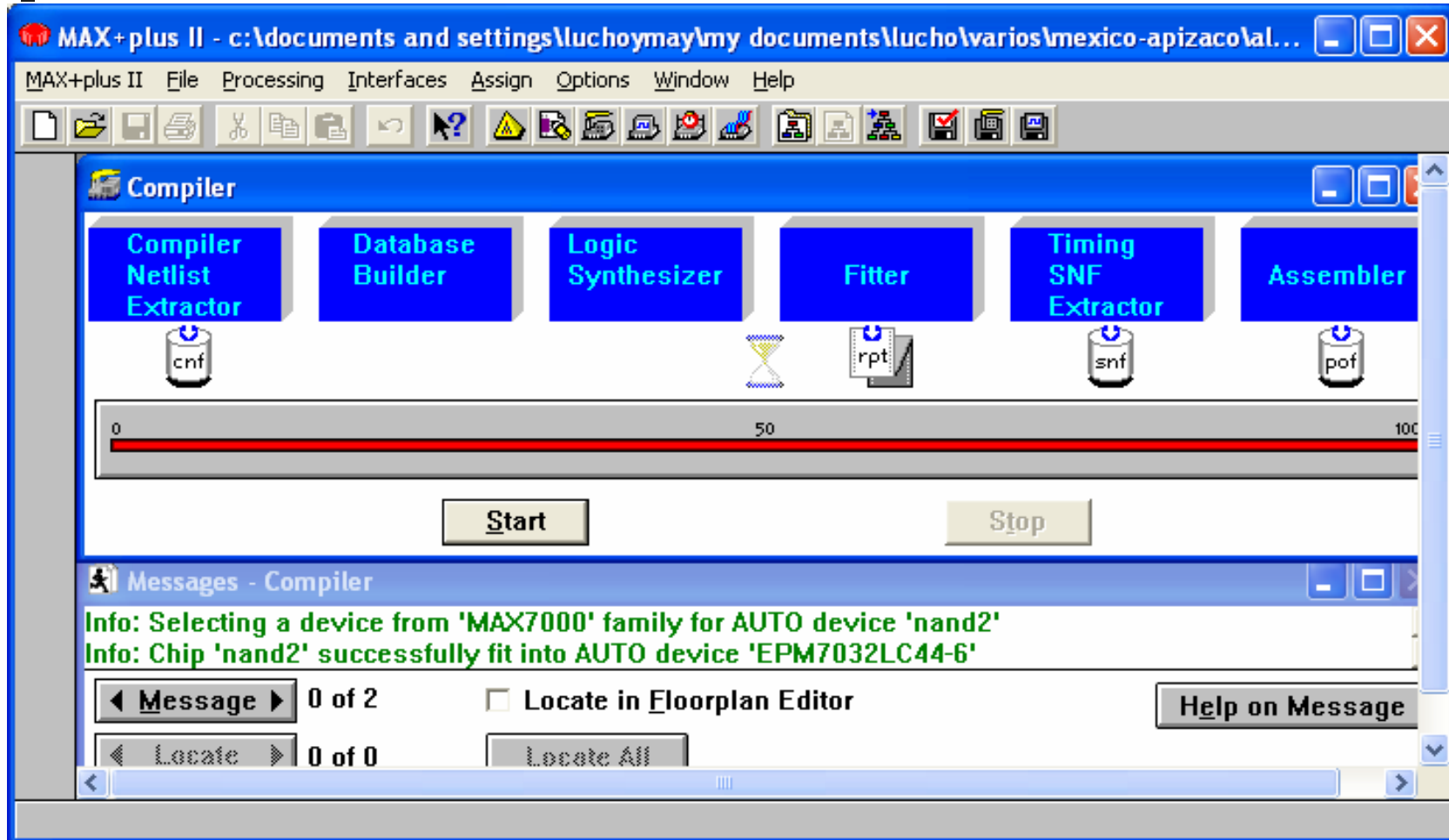

Max+Plus II

Nand2, Simulation

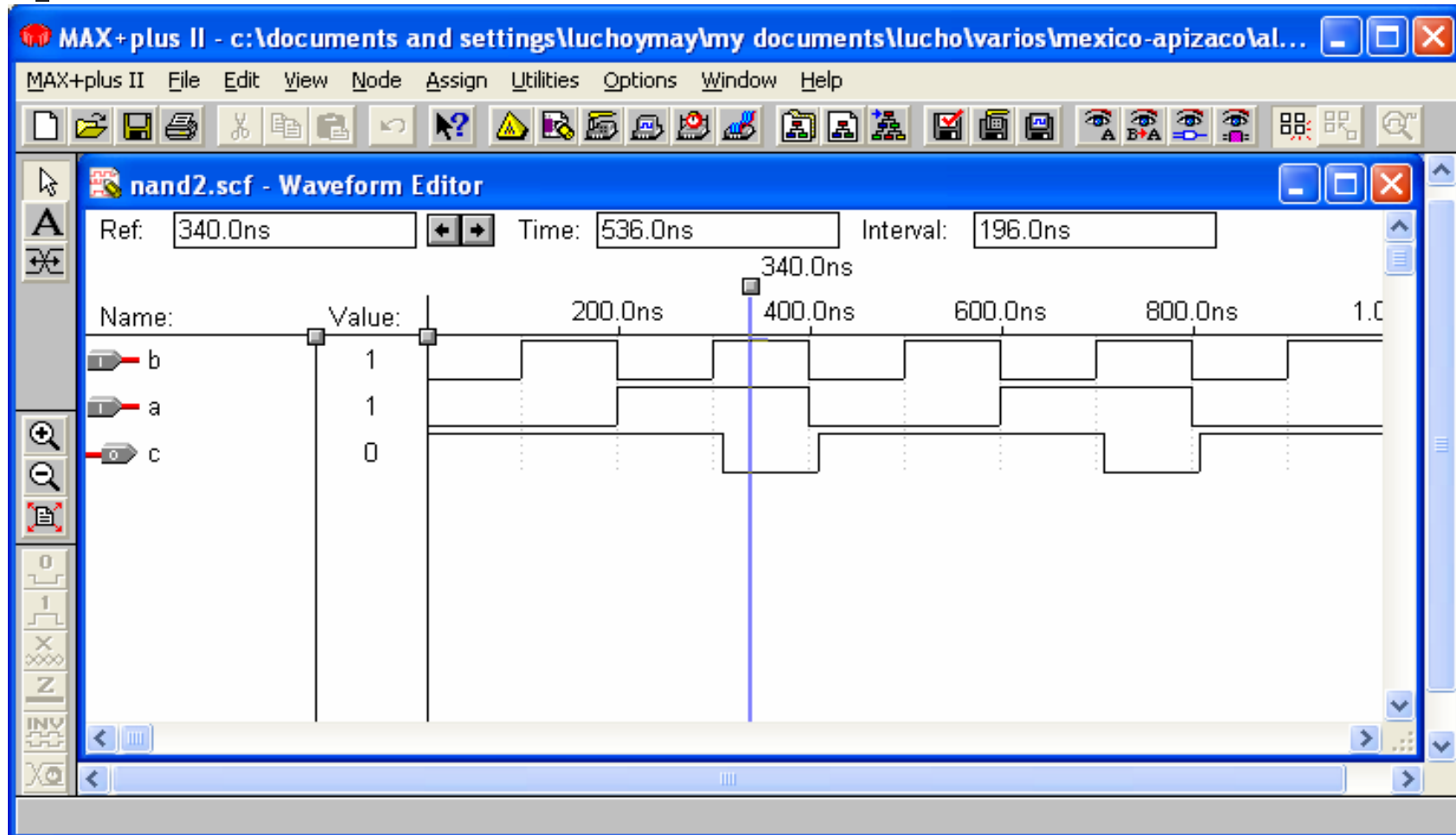

Example Description

- **library** and **use** statements allowing to use the IEEE 1164 standard logic data types.

```
library IEEE;  
use IEEE.std_logic.all
```

Example Description

- An **entity** declaration defining the interface to the circuit.

```
entity nand2 is  
port (a, b : in std_logic;  
        c : out std_logic);  
end nand2;
```

Example Description

- The **process** sensitivity list enumerates exactly which signals causes the process execution.

process (a, b)

Example Description

- The process declarative part is used to declare local variables or constants that can be used in the process.

```
variable temp: std_logic
```

Example Description

- Variables are temporary storage areas similar to variables in software programming languages.

```
variable temp: std_logic
```


Use of Sequential Statements

- Sequential Statements Exist Inside the Process Statements As Well As in Sub Programs.
- The Sequential Statements Are:
 - if
 - case
 - loop
 - assert
 - wait

IF Statements

- The IF statement starts with the keyword *if* and ends with the keyword *end if*.

```
If (x < 10) then  
    a := b;  
end if;
```

IF Statements

- There are also two optional clauses

- Elsif clause
- Else clause

```
if (day = Sunday) then  
    weekend := true;  
elsif (day = Saturday) then  
    weekend := true;  
else  
    weekday := true;  
end if;
```

IF Statements

- The **if** statement can have multiple **elsif** statement parts but only one **else** statement part.

Case statement

- The Case statement is used whenever a single expression value can be used to select between a number of actions.
- A Case statement consists of the keyword ***case*** followed by an expression and the keyword ***is***.

Case statement

- The expression will either return a value that matches one of the *choices* in a *when* statement part or match an *others* clause.

Case Statement Example 2

```
type vectype is array(0 to 1) of bit;
variable bit_vec: vectype;
.....
case bit_vec is
  when "00" =>
    return 0;
  when "01" =>
    return 1;
  when "10" =>
    return 2;
  when "11" =>
    return 3;
end case;
```

Loop Statements

- The loop statement is used whenever an operation needs to be repeated.
- Loop statements are implemented in two ways
 - *while* condition loop statement
 - *for* condition loop statement

Loop Statements (*while*)

- The *while* condition Loop statement will loop as long as the condition expression is TRUE.

```
while (day = weekday) loop  
    day := get_next_day (day);  
end loop;
```

Loop Statements (*for loop*)

```
for i in 1 to 10 loop  
    i_squared(i) := i*i;  
end loop;
```

- This loop will execute 10 times whenever execution begins and its function is to calculate squares from 1 to 10 and insert them into i_squared signal array.

Next statement

- The *next* statement allows us to stop execution of a particular iteration and go on to the next iteration.

```

for i in 0 to max_limit loop
  if (done (i) = true ) then
    next;
  else
    done(i) := true;
  end if;
  q(i) <= a(i) and b(i);
end loop;
  
```

Exit statement

- The VHDL exit statement allows the designer to exit or jump out of the loop statement currently in execution.

```

for i in 0 to max_limit loop
  if (int_a <= 0) then
    exit;
  else
    int_a := int_a-1;
    q(i) <= 3.14 / real(int_a * i);
  end if;
end loop;
  
```

Assert Statement

- Assert Statements Are Very Useful for Reporting Textual Strings to the Designer.
- The Assert Statement Checks the Value of a Boolean Expression. If the Condition Is Not True, a Report (Message) Is Generated During the Simulation.

Assert Statement

- An assert statement includes two options, either or both of which may be used. The first Option
 - **Report:** displays a user defined message if the condition is false

Assert Statement

- An assert statement includes two options, either or both of which may be used. The second Option:
 - **Severity:** allows the user to choose a severity level if the condition is false. The four levels of severity are
 - Note,
 - Warning,
 - Error
 - Failure

Wait Statements

- The *wait* statement allows to suspend the sequential execution of a process or subprogram.
- The condition for resuming execution of the suspended process or subprogram can be specified by three different means.

Wait Statements

- *wait on* signal changes.

```
wait on signal [signal]
```

- *wait until* an expression is true.

```
wait until Boolean_expression
```

Wait Statements

- *wait for* a specific amount time.

```
wait for time_expression
```

Wait on Statement

- The *wait on* signal clause specifies a list of one or more signals upon which the *wait* statement will wait for the events.

```

process
begin
  if (reset = '1' ) then
    q <= '0' ;
  elsif clock 'event and clock = '1' then
    q <= d;
  end if;
  wait on reset, clock;
end process;
  
```

Wait Until Statement

- The *wait until* Boolean_expression clause will suspend execution of the process until the expression returns a true value.

```

process
begin
    wait until clock = '1' and clock' event;
    q <= d ;
end process;
  
```

Wait for Statement

- The *wait for* time_expression clause will suspend execution of the process for the time specified by the time expression.

```
wait for 10 ns;
```

- The wait statement will suspend for 10 ns and after 10 ns the execution will continue.

Structural VHDL

- Structural-level design methods can be useful for managing the complexity of a large design description.
- Structure level of abstraction is used to combine multiple components to form a larger circuit.

Structural VHDL

- Structural VHDL Descriptions Are Quite Similar in Format to Schematic Netlists.


- Larger Circuits Can Be Constructed From Smaller Building Blocks.

Example of Structural VHDL


Let us consider an ALU with

- An OR gate
- An XOR gate
- A Half Adder
- A Full Adder
- A Multiplexer

Example of Structural VHDL

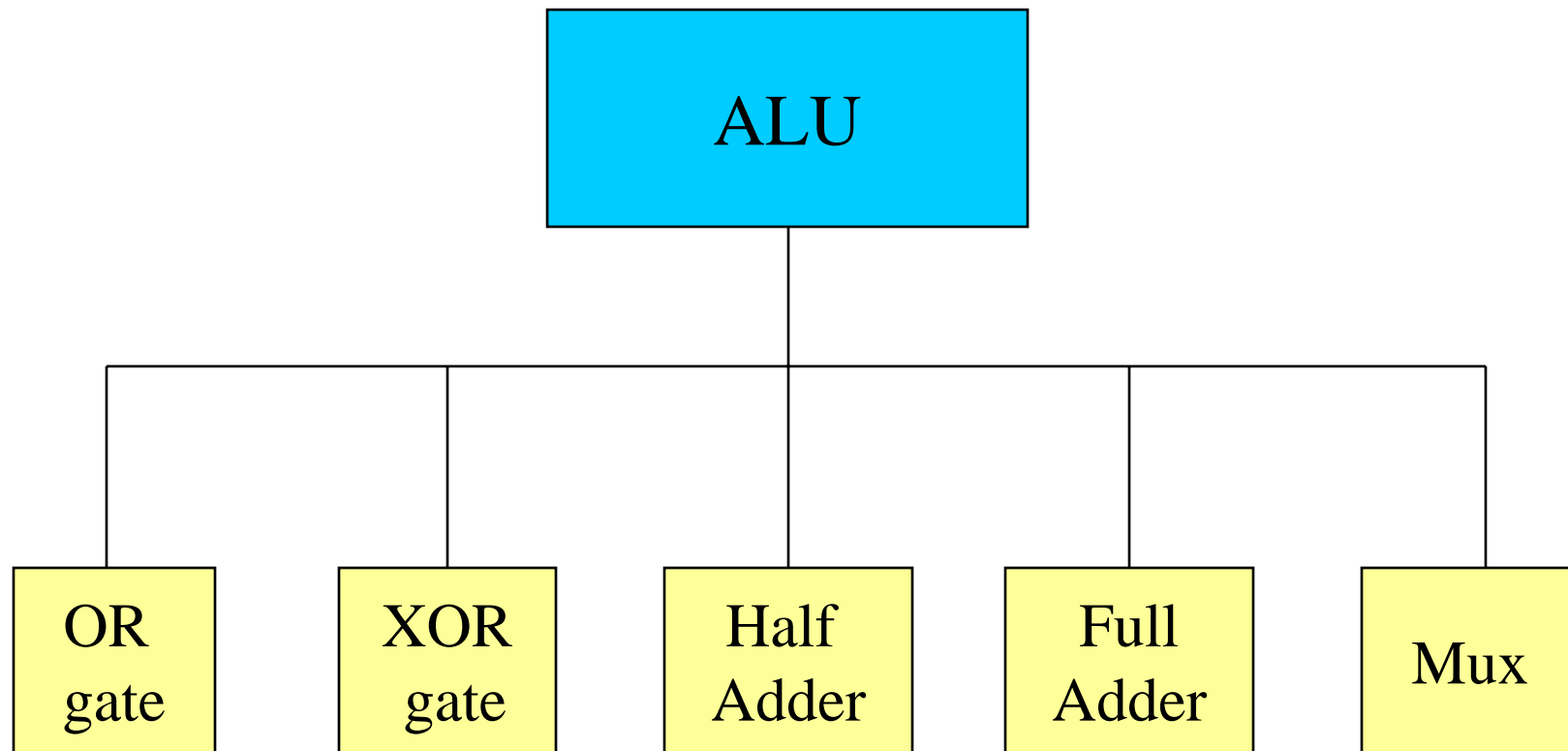


ALU – Block Diagram

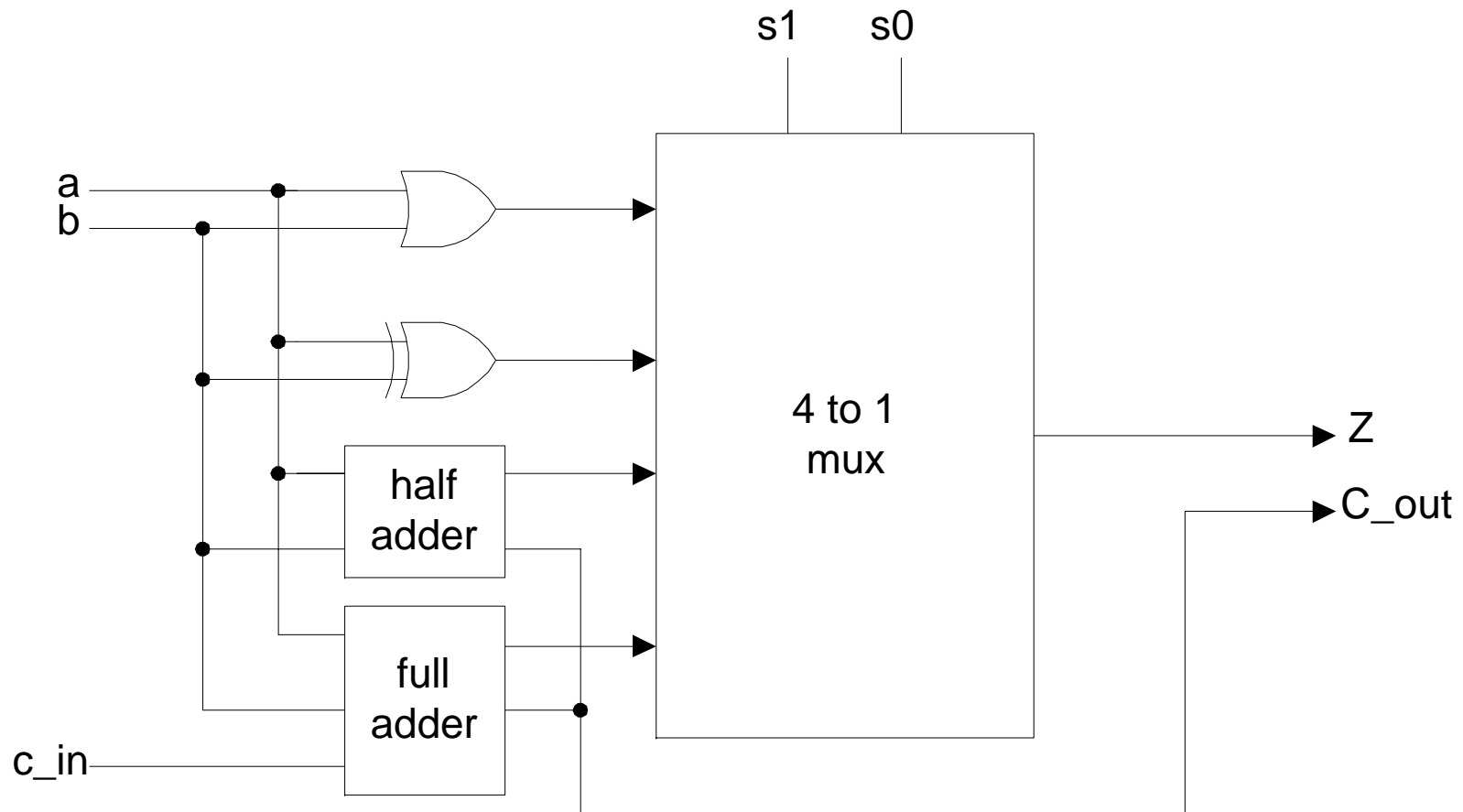

ALU – Function Table

S1	S0	Z	C_out
0	0	a or b	0
0	1	a xor b	0
1	0	ha_sum	ha_c_out
1	1	fa_sum	fa_c_out

 

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL


UNIVERSIDAD DEL NORTE

VHDL code for OR gate

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity t_or is  
    port (a, b : in std_logic;  
          ored : out std_logic);  
end t_or;  
architecture concurrent_behavior of t_or is  
begin  
    ored <= (a or b);  
end concurrent_behavior;
```

Max+Plus II

T_OR, Code Entry

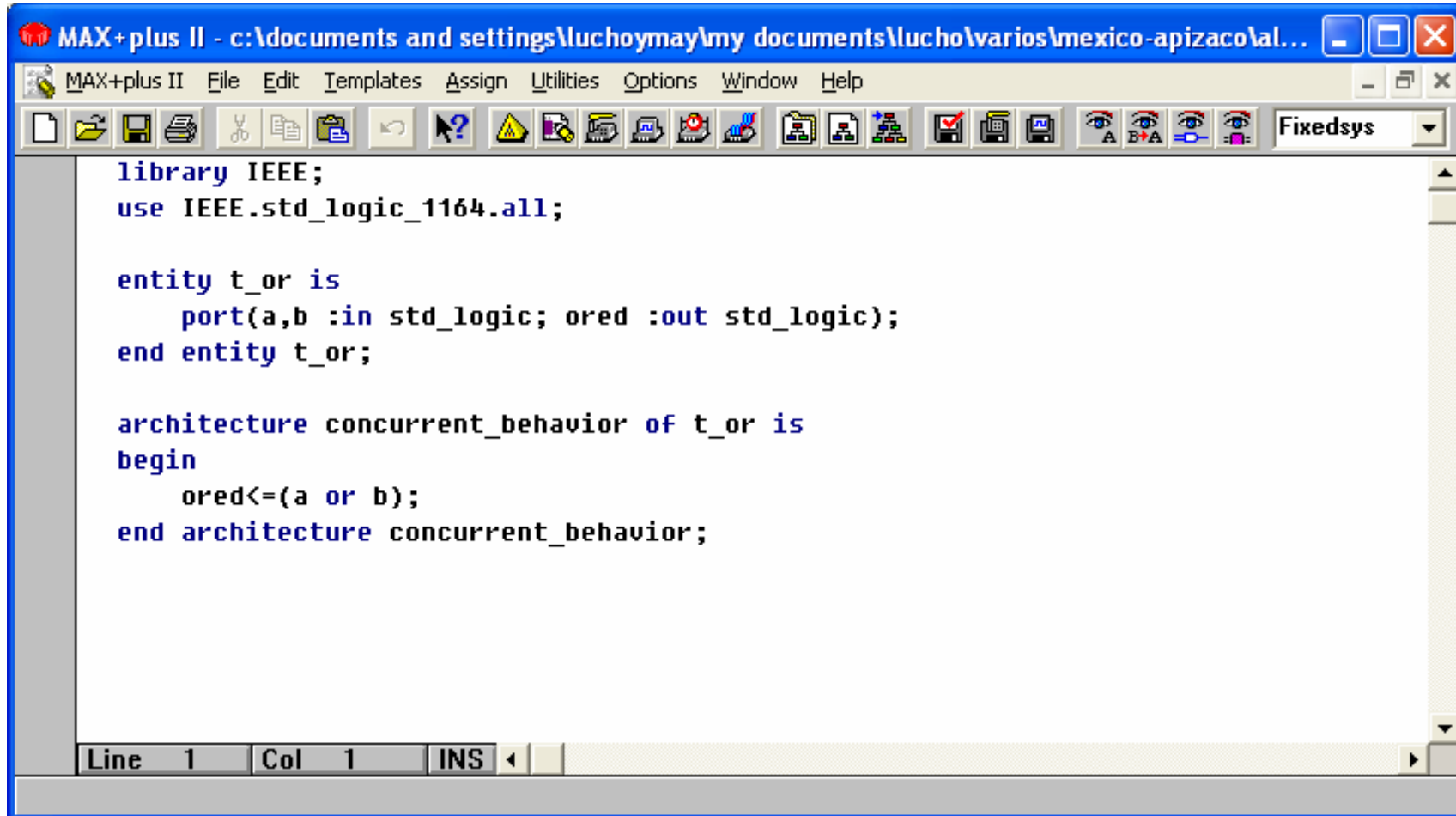


```
library IEEE;
use IEEE.std_logic_1164.all;

entity t_or is
    port(a,b :in std_logic; ored :out std_logic);
end entity t_or;

architecture concurrent_behavior of t_or is
begin
    ored<=(a or b);
end architecture concurrent_behavior;
```


Max+Plus II T_OR, Compiler

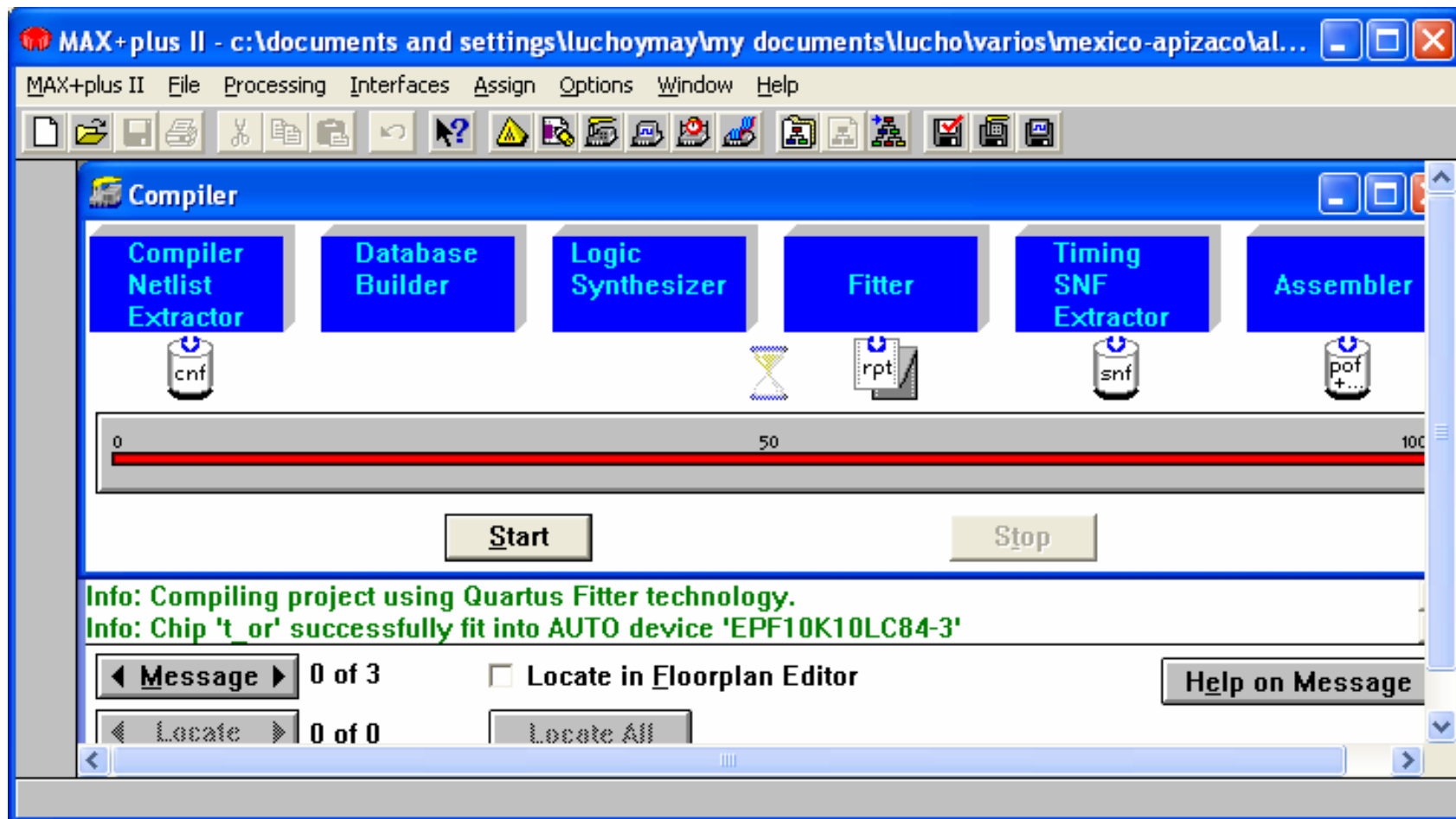

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Max+Plus II

T_OR, Simulation

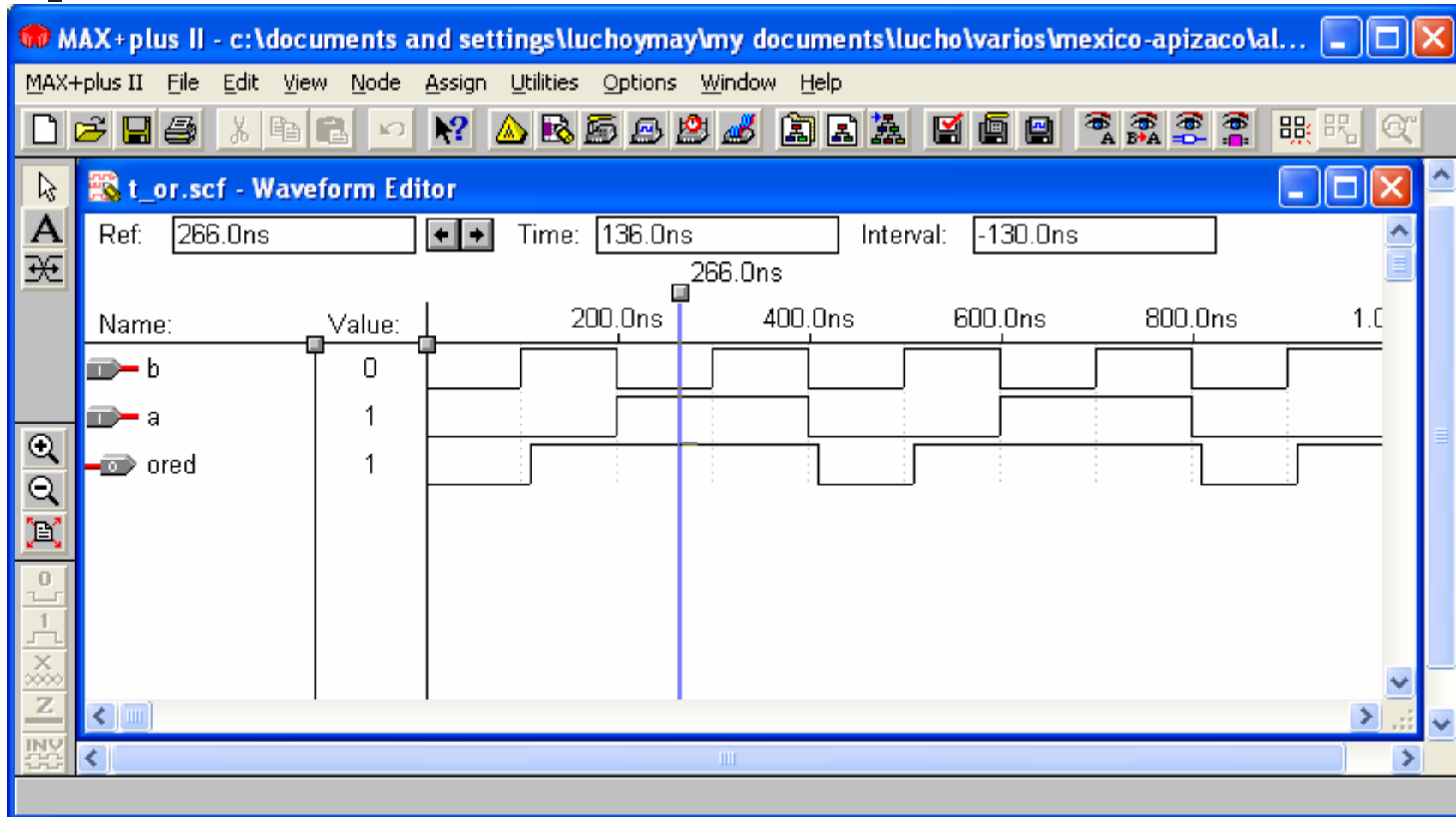


VHDL code for XOR

```
library IEEE;  
use IEEE.std_logic_1164.all;  
entity t_xor is  
    port (a,b : in std_logic;  
          xored : out std_logic);  
end t_xor;  
architecture concurrent_behavior of t_xor is  
begin  
    xored <= (a xor b);  
end concurrent_behavior;
```


Max+Plus II

T_XOR, Code Entry

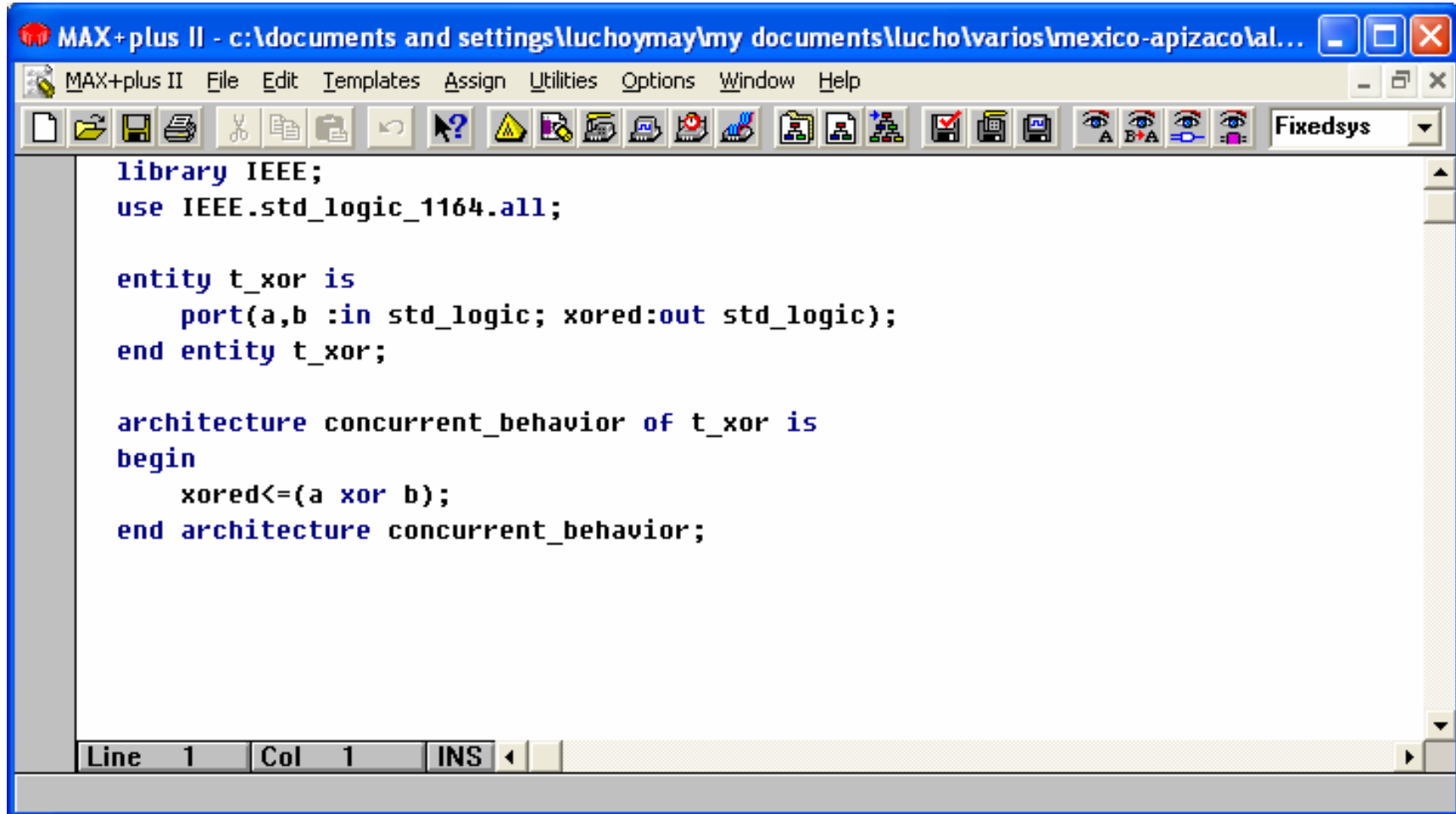


```
library IEEE;
use IEEE.std_logic_1164.all;

entity t_xor is
    port(a,b :in std_logic; xored:out std_logic);
end entity t_xor;


architecture concurrent_behavior of t_xor is
begin
    xored<=(a xor b);
end architecture concurrent_behavior;
```

Max+Plus II T_XOR, Compiler

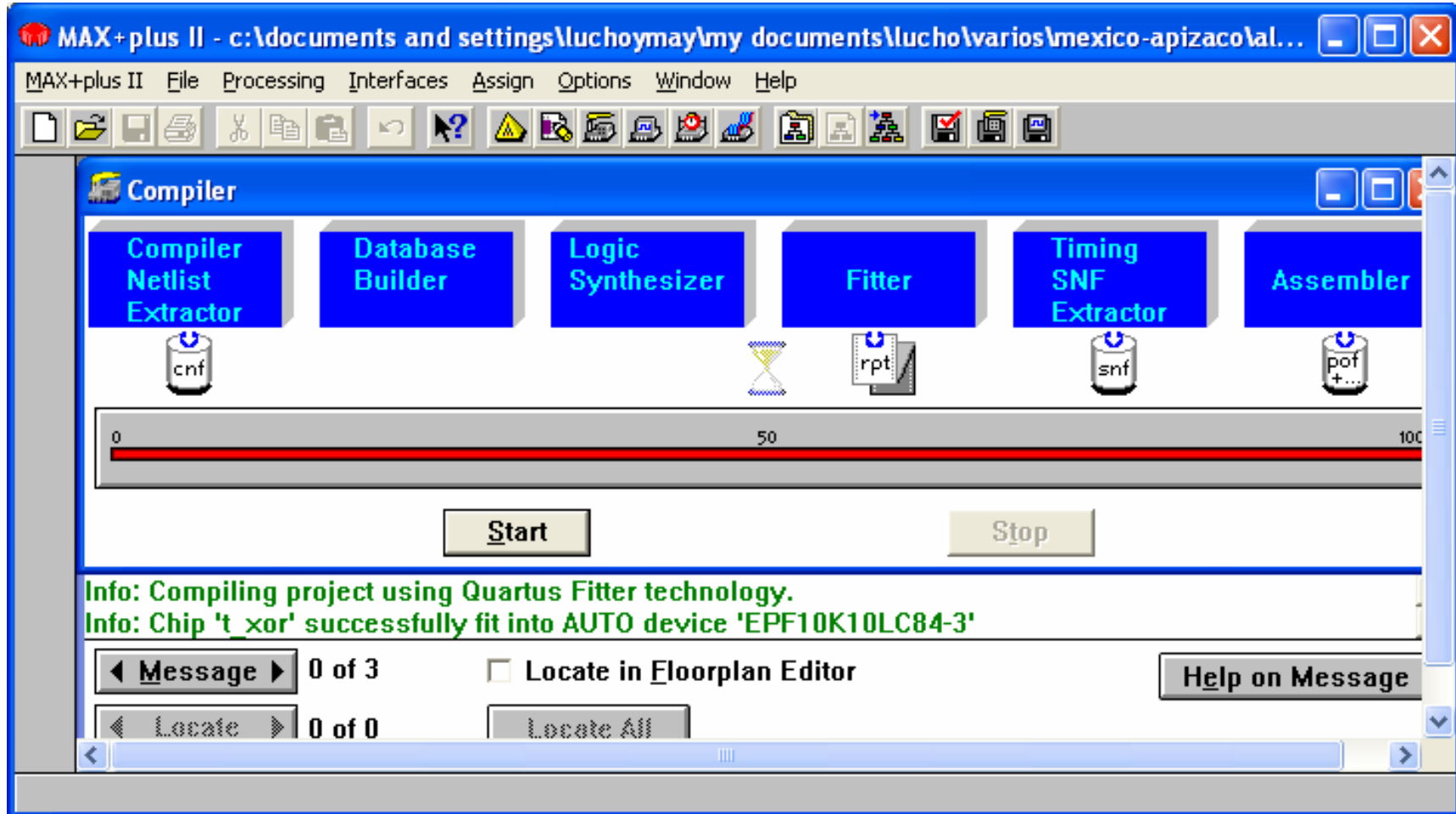

Max+Plus II

T_XOR, Simulation

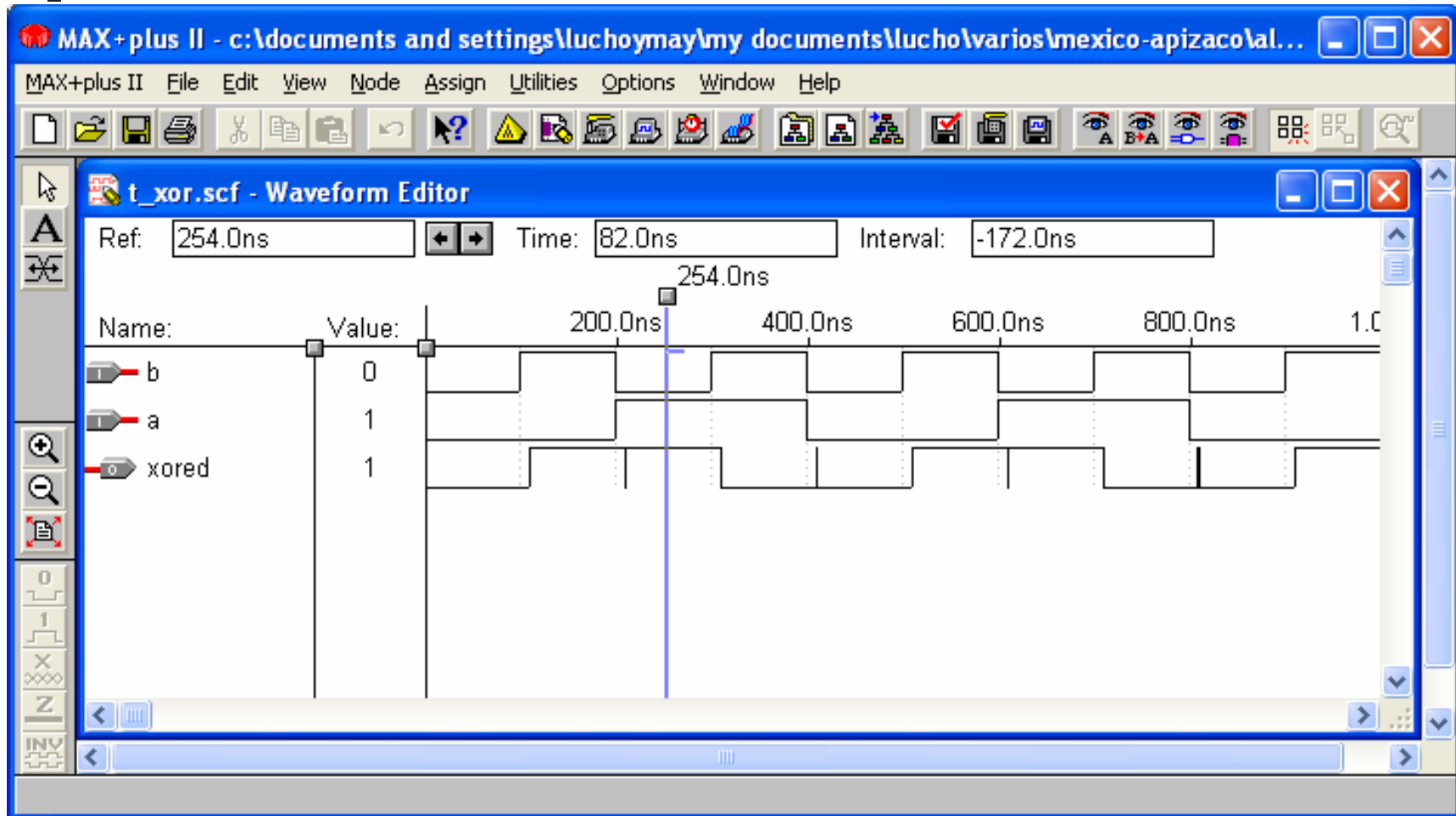

VHDL Code for Half_adder

-- Half Adder

library IEEE;

--refer IEEE library.

use IEEE.std_logic_1164.**all**;

entity half_adder **is**

port (a, b : **in** std_logic; **--declaring I/O ports**

sum, c_out : **out** std_logic);

end half_adder;

Half_Adder code (cont...)

architecture behavior of
half_adder is

begin

sum <= (a xor b);

c_out <= (a and b);

end behavior;


 


Figure 1-1 Half adder circuit

Max+Plus II

Half-Adder, Code Entry

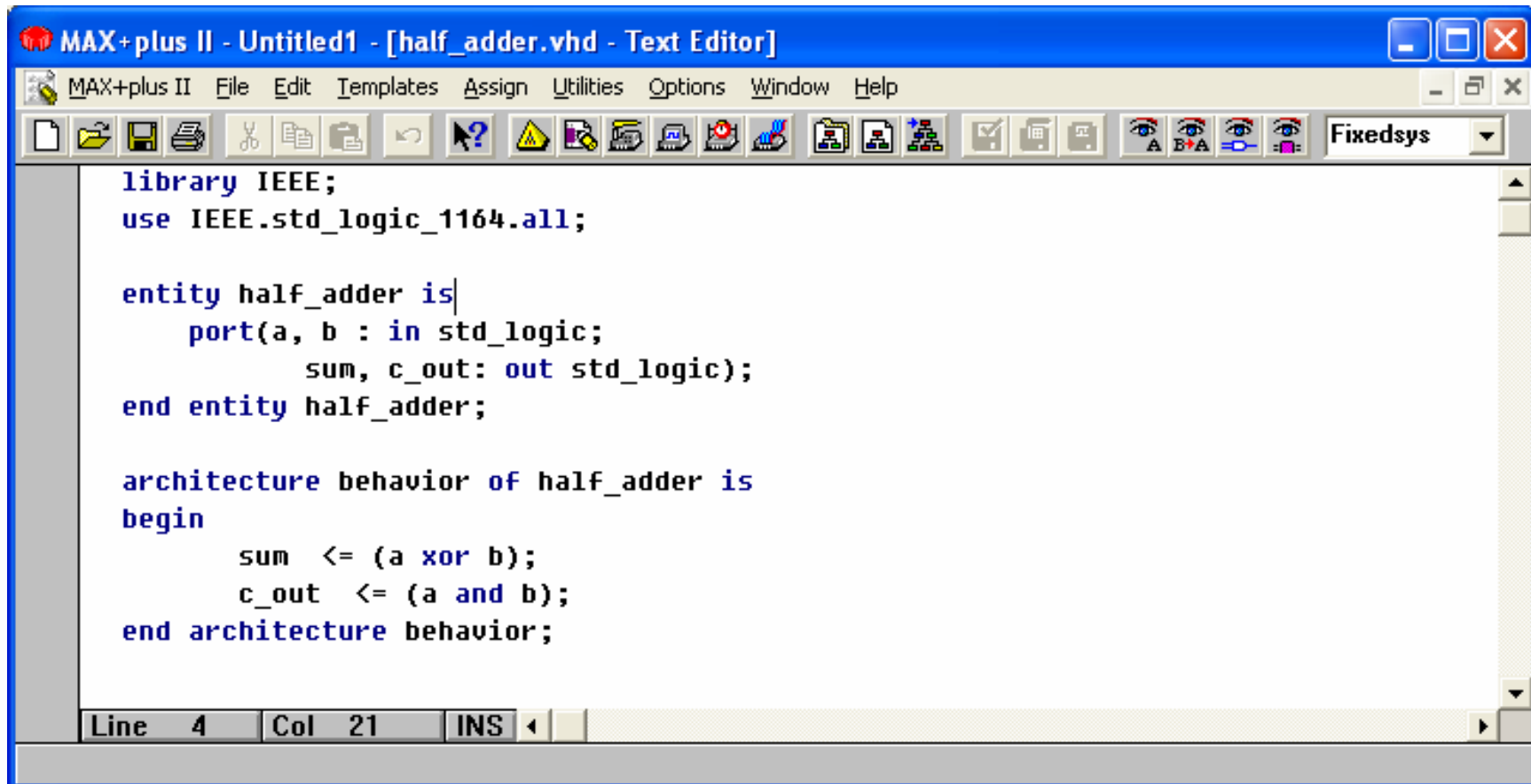

```
MAX+plus II - Untitled1 - [half_adder.vhd - Text Editor]
MAX+plus II  File  Edit  Templates  Assign  Utilities  Options  Window  Help
Library IEEE;
use IEEE.std_logic_1164.all;


entity half_adder is
    port(a, b : in std_logic;
         sum, c_out: out std_logic);
end entity half_adder;

architecture behavior of half_adder is
begin
    sum <= (a xor b);
    c_out <= (a and b);
end architecture behavior;
```

Line 4 Col 21 INS


Max+Plus II

Half-Adder, Compiler

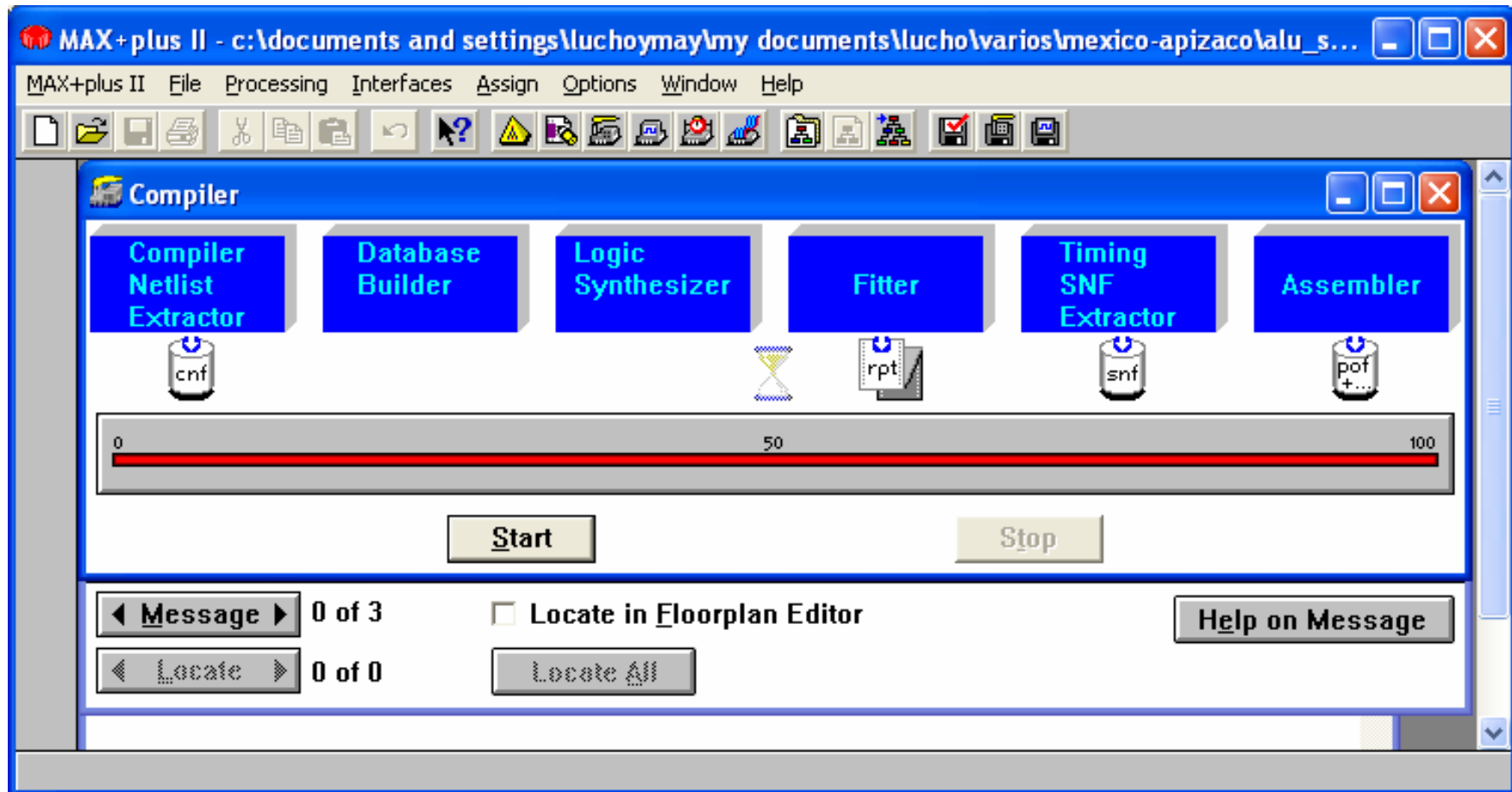


Max+Plus II

Half-Adder, Simulation

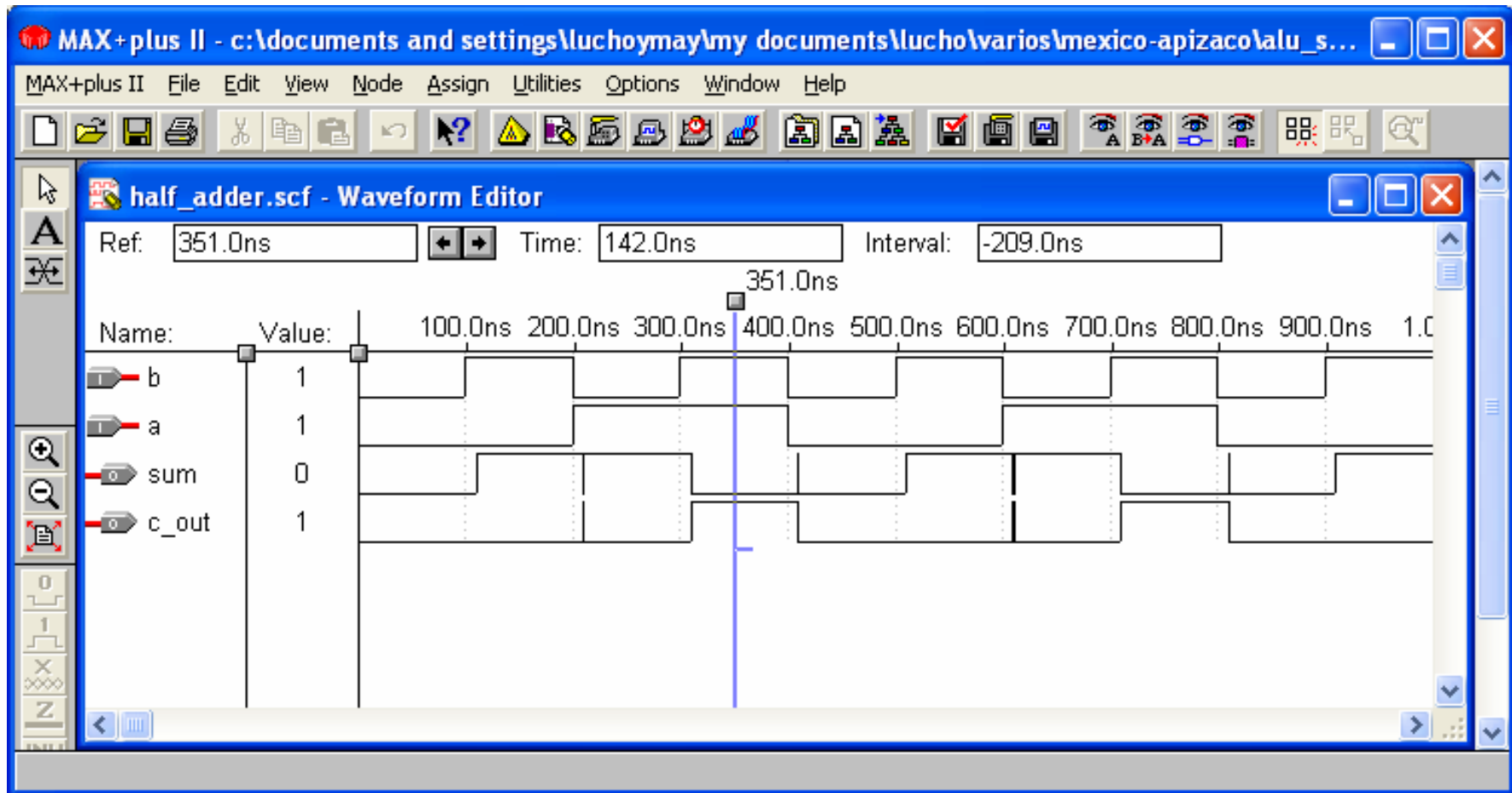

Full Adder circuit

 

VHDL code for Full Adder

```
--Full_Adder  
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity full_adder is  
port (a, b, c_in : in std_logic;  
       sum, c_out : out std_logic);  
end full_adder;
```

VHDL code for Full Adder


```

architecture dataflow of full_adder is
signal s1, s2, s3 : std_logic;
begin
  L1: s1 <= (a xor b);
  L2: s2 <= (c_in and s1);
  L3: s3 <= (a and b);
  L4: sum <= (s1 xor c_in);
  L5: c_out <= (s2 or s3);
end dataflow;
  
```

-- Using Signal Assignment Instructions

Max+Plus II

Full-Adder, Code Entry

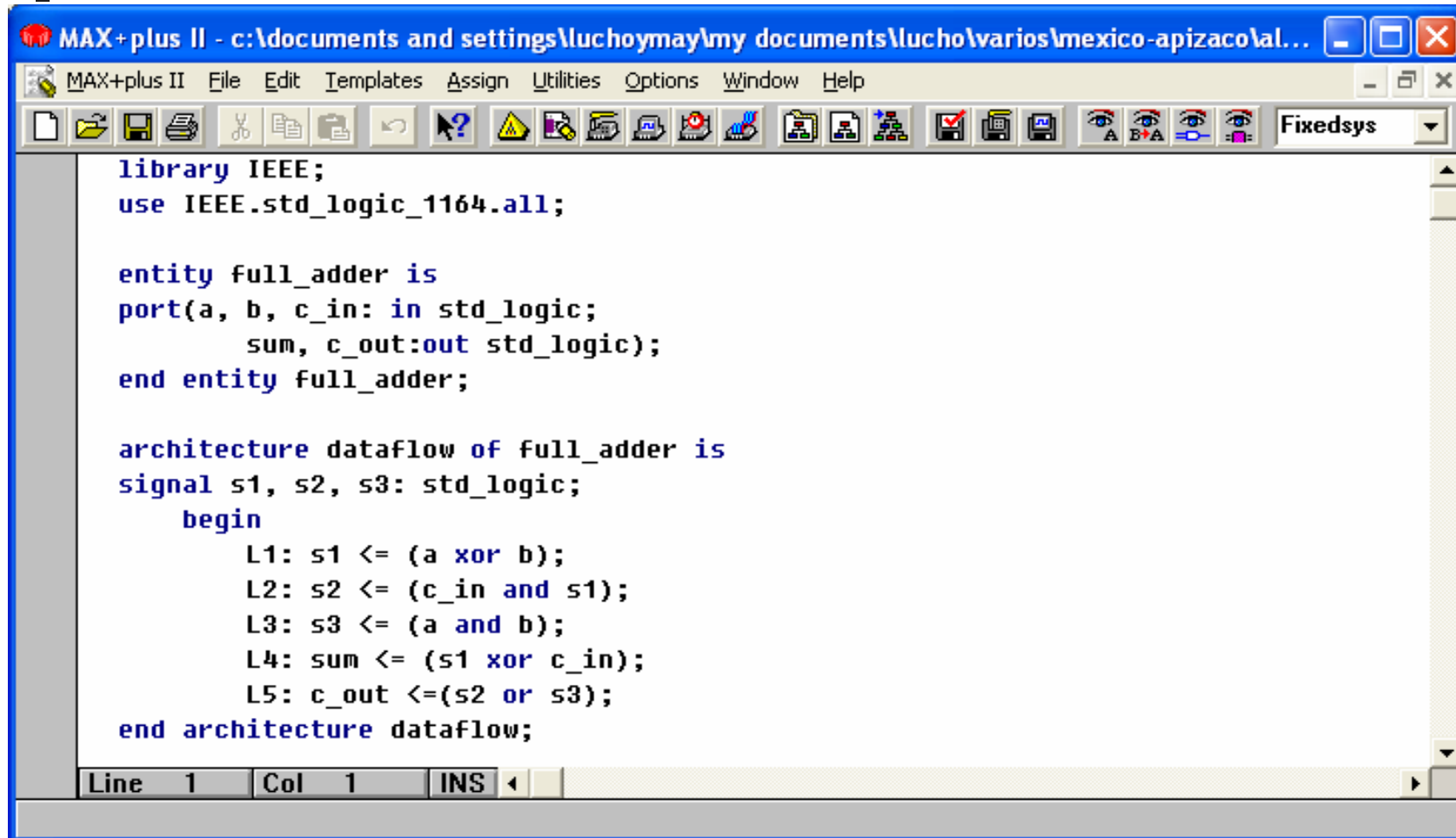


```
MAX+plus II - c:\documents and settings\luchoymay\my documents\lucho\varios\mexico-apizaco\al...
MAX+plus II File Edit Templates Assign Utilities Options Window Help
Library IEEE;
use IEEE.std_logic_1164.all;

entity full_adder is
port(a, b, c_in: in std_logic;
      sum, c_out:out std_logic);
end entity full_adder;

architecture dataflow of full_adder is
signal s1, s2, s3: std_logic;
begin
    L1: s1 <= (a xor b);
    L2: s2 <= (c_in and s1);
    L3: s3 <= (a and b);
    L4: sum <= (s1 xor c_in);
    L5: c_out <=(s2 or s3);
end architecture dataflow;
Line 1 Col 1 INS
```


Max+Plus II

Full-Adder, Compiler

 

Max+Plus II

Full-Adder, Simulation

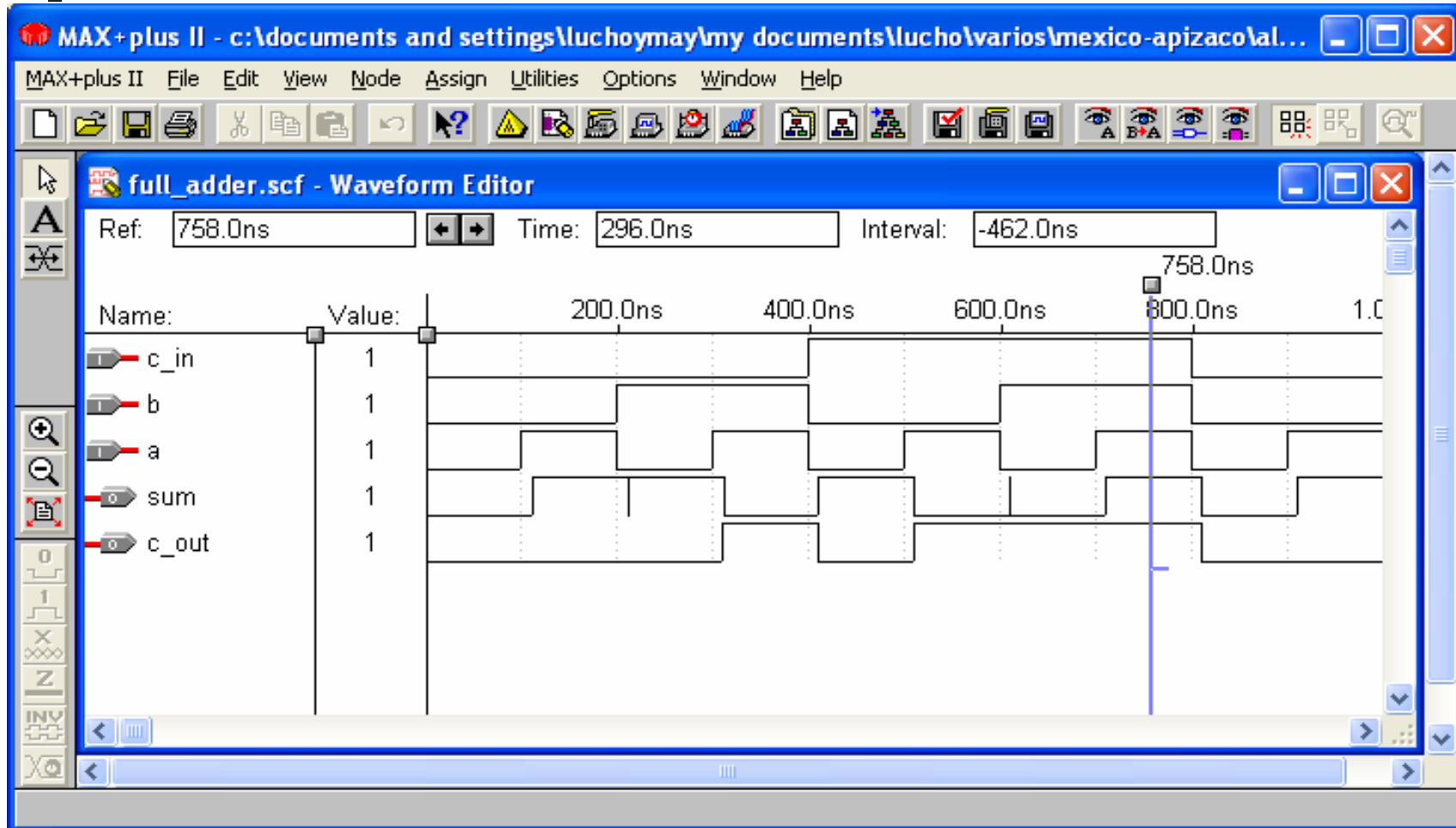

Declaration of ALU Package

```
library IEEE;  
use IEEE.std_logic_1164.all;  
package alu_pack is  
    component t_or  
        port (a, b : in std_logic;  
              ored : out std_logic);  
    end component;  
    component t_xor  
        port (a ,b : in std_logic;  
              xored : out std_logic);  
    end component;
```


Declaration of ALU Package

```
component half_adder
    port (a, b : in std_logic;
          ha_sum, c_out : out std_logic);
end component;
component full_adder
    port (a, b, c_in : in std_logic;
          sum, c_out : out std_logic);
end component;

end alu_pack;
```


Max+Plus II

alu_pack, Code Entry

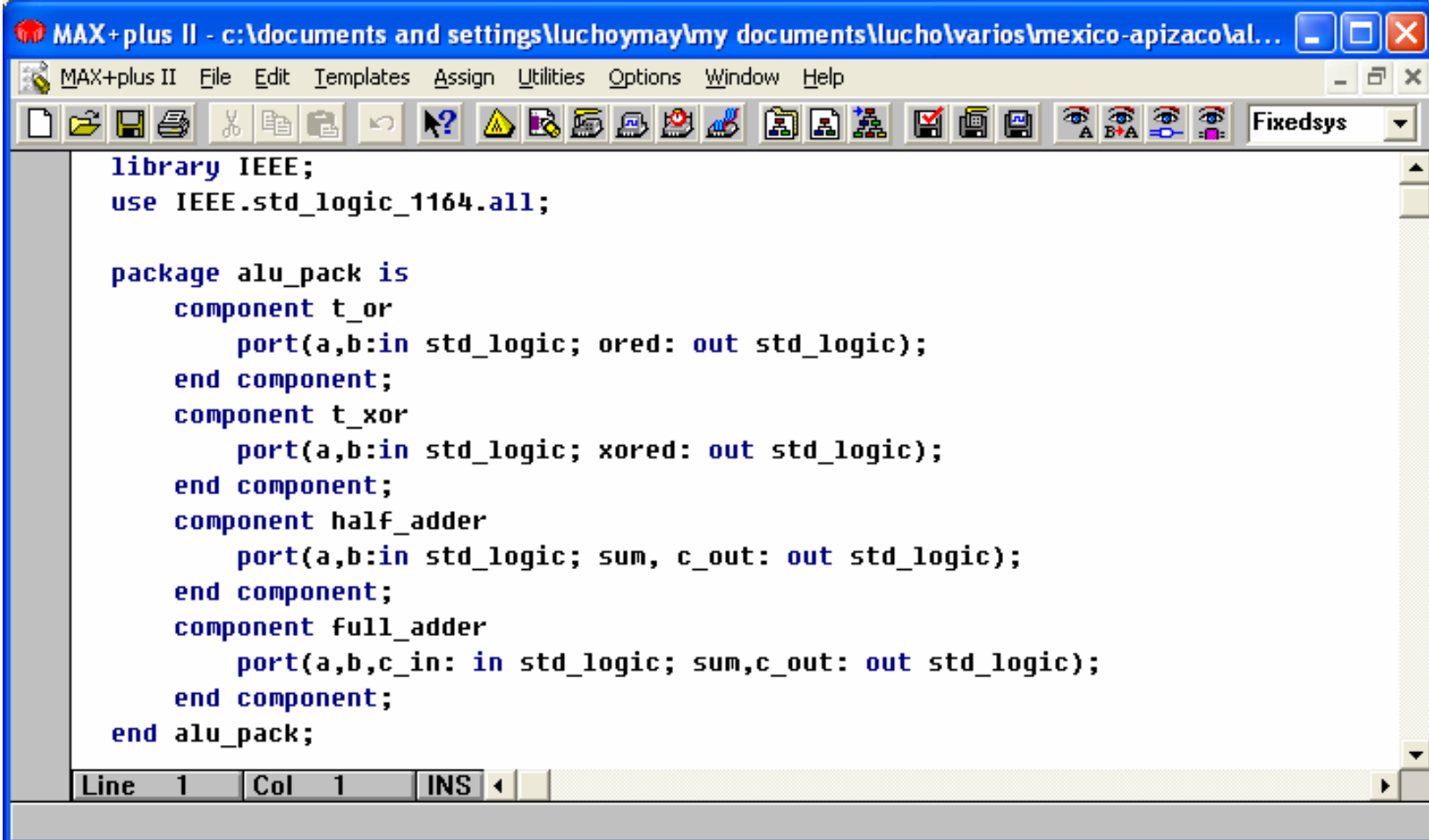


```
library IEEE;
use IEEE.std_logic_1164.all;

package alu_pack is
  component t_or
    port(a,b:in std_logic; ored: out std_logic);
  end component;
  component t_xor
    port(a,b:in std_logic; xored: out std_logic);
  end component;
  component half_adder
    port(a,b:in std_logic; sum, c_out: out std_logic);
  end component;
  component full_adder
    port(a,b,c_in: in std_logic; sum,c_out: out std_logic);
  end component;
end alu_pack;
```

Max+Plus II

alu_pack, Compiler

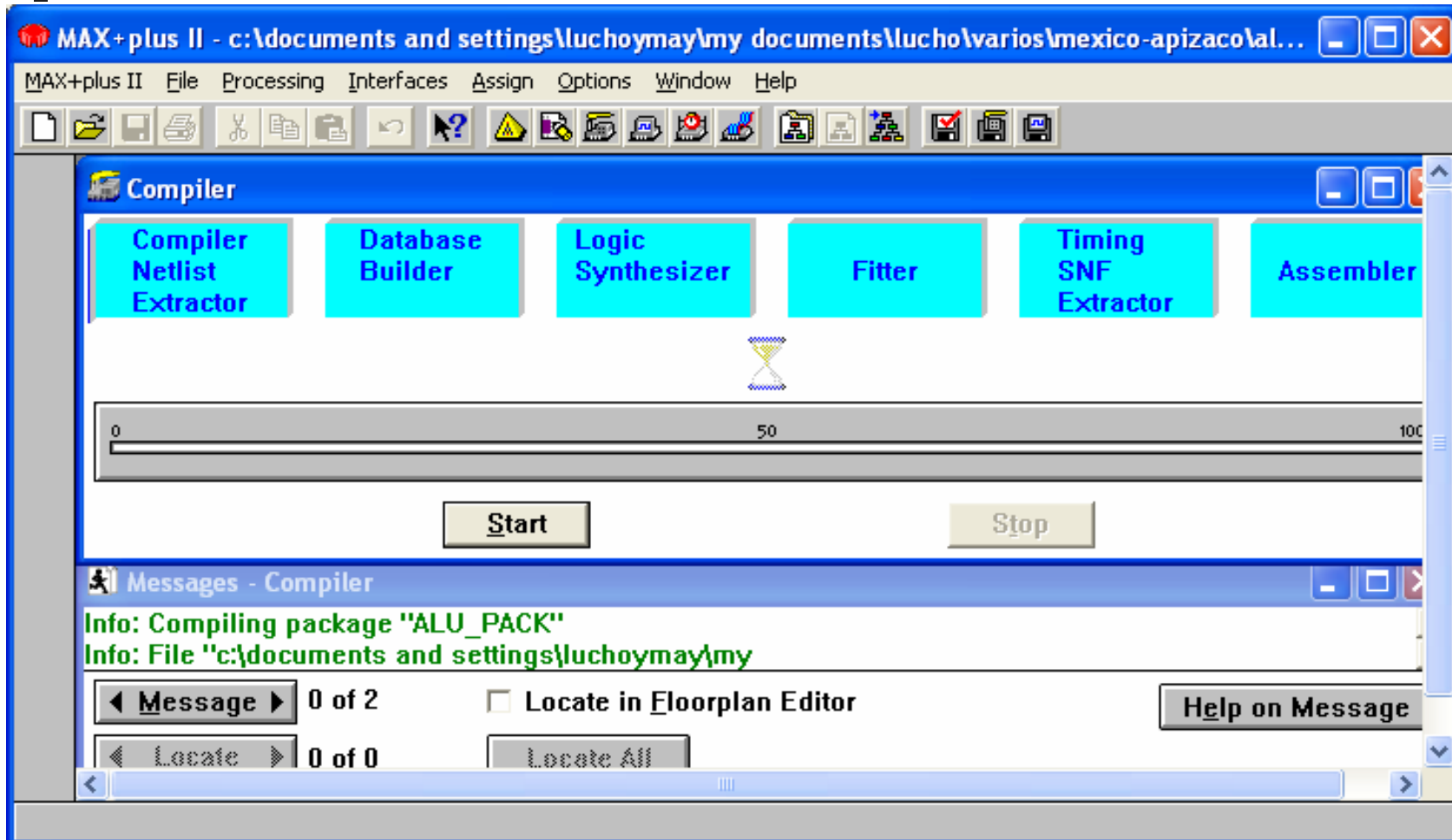



Max+Plus II

alu_pack, Simulation

- The ALU_PACK design can not be simulated since it is a Package.
- Its operation will be verified together with the designs that will use it. In this case this will be the ALU main design.

Main Code for ALU

```
library IEEE;  
use IEEE.std_logic_1164.all;  
library work;  
use work.alu_pack.all;  
  
entity alu is  
    port (a, b, c_in, s0, s1 : in std_logic;  
          z, c_out : out std_logic);  
end alu;
```

Main Code for ALU Cont...

architecture structural **of** alu **is**

signal ored, xored, ha_sum, ha_c_out, fa_sum,
 fa_c_out : std_logic;

begin

```

a1: t_or port map (a => a, b => b, ored => ored);
x1: t_xor port map (a => a, b => b, xored => xored);
h1: half_adder port map (a => a, b => b,
    sum => ha_sum, c_out => ha_c_out);
f1: full_adder port map (a => a, b => b,
    c_in => c_in, sum => fa_sum,
    c_out => fa_c_out);
  
```

Main Code for ALU Cont....

```
alu_process: process (a, b, c_in, s0, s1)
begin
    if (s1 = '0' and s0 = '0') then
        z <= ored;
        c_out <= '0';
    end if;
    if (s1 = '0' and s0 = '1') then
        z <= xored;
        c_out <= '0';
    end if;
```

Main Code for ALU Cont....

```
if (s1 = '1' and s0 = '0') then  
    z <= ha_sum;  
    c_out <= ha_c_out;
```

```
end if;
```

```
if (s1 = '1' and s0 = '1') then  
    z <= fa_sum;  
    c_out <= fa_c_out;
```


```
end if;
```

```
end process alu_process;
```

```
end architecture structural;
```

Max+Plus II

ALU, Code Entry

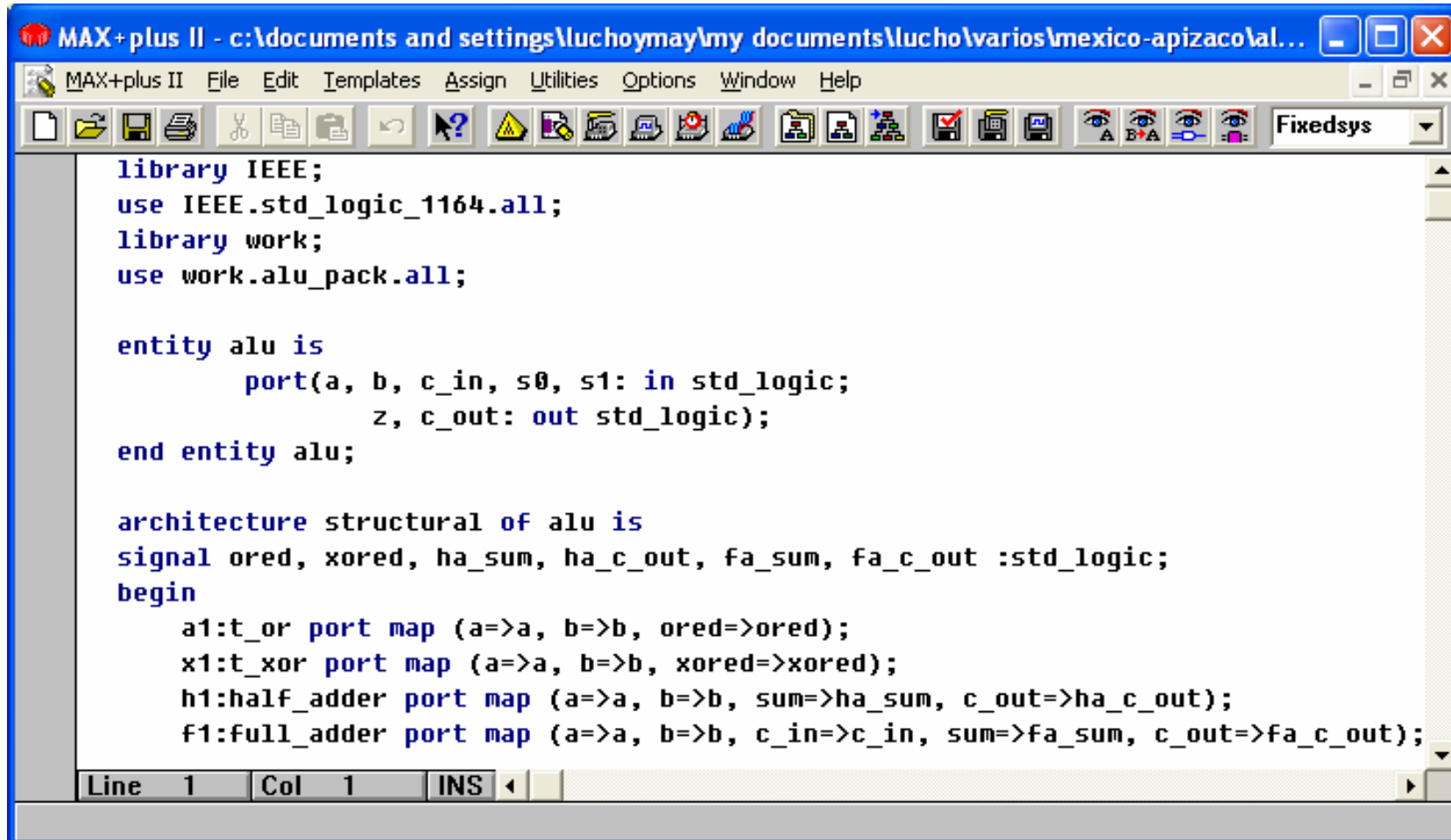


```
library IEEE;
use IEEE.std_logic_1164.all;
library work;
use work.alu_pack.all;

entity alu is
    port(a, b, c_in, s0, s1: in std_logic;
         z, c_out: out std_logic);
end entity alu;

architecture structural of alu is
    signal ored, xored, ha_sum, ha_c_out, fa_sum, fa_c_out :std_logic;
begin
    a1:t_or port map (a=>a, b=>b, ored=>ored);
    x1:t_xor port map (a=>a, b=>b, xored=>xored);
    h1:half_adder port map (a=>a, b=>b, sum=>ha_sum, c_out=>ha_c_out);
    f1:full_adder port map (a=>a, b=>b, c_in=>c_in, sum=>fa_sum, c_out=>fa_c_out);
```



Max+Plus II


ALU, Compiler

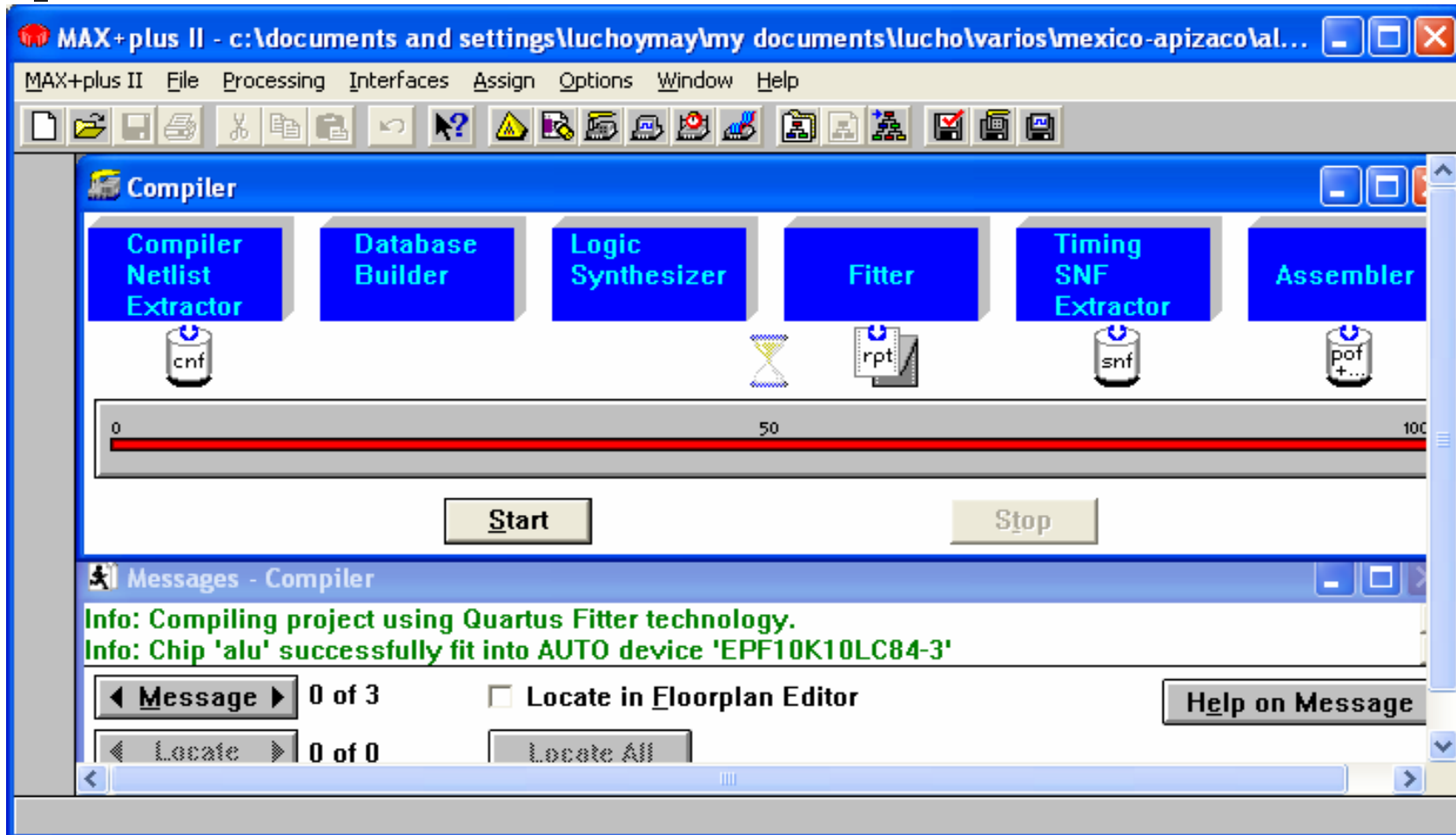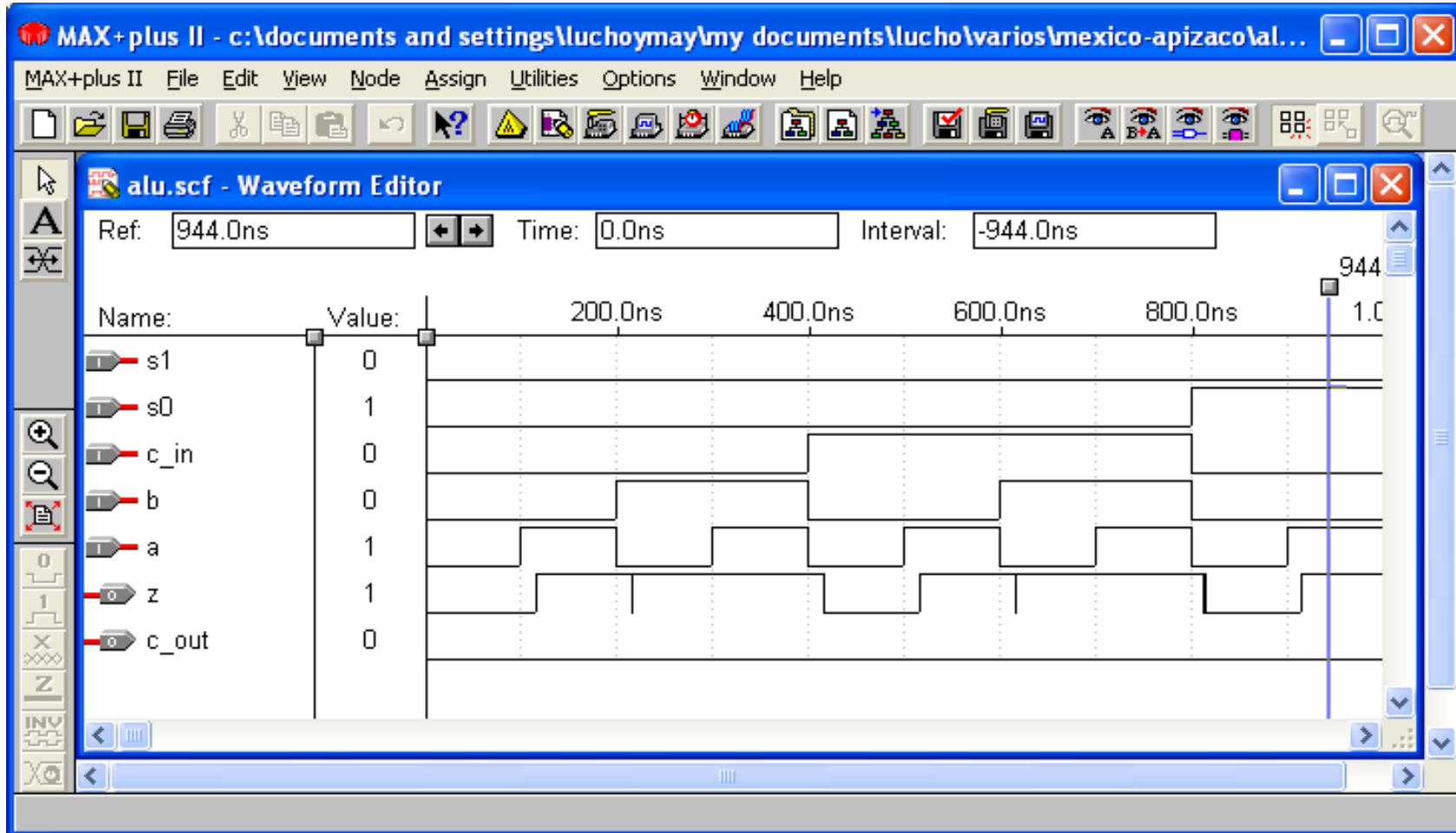

Max+Plus II

ALU, Simulation



 


Session III

CONTROL AND DATA PATH ORGANIZATION

Control and Data Path Organization

- Most complex digital circuits can be broken up into two parts:
 - Control
 - Data Path

Control and Data Path Organization

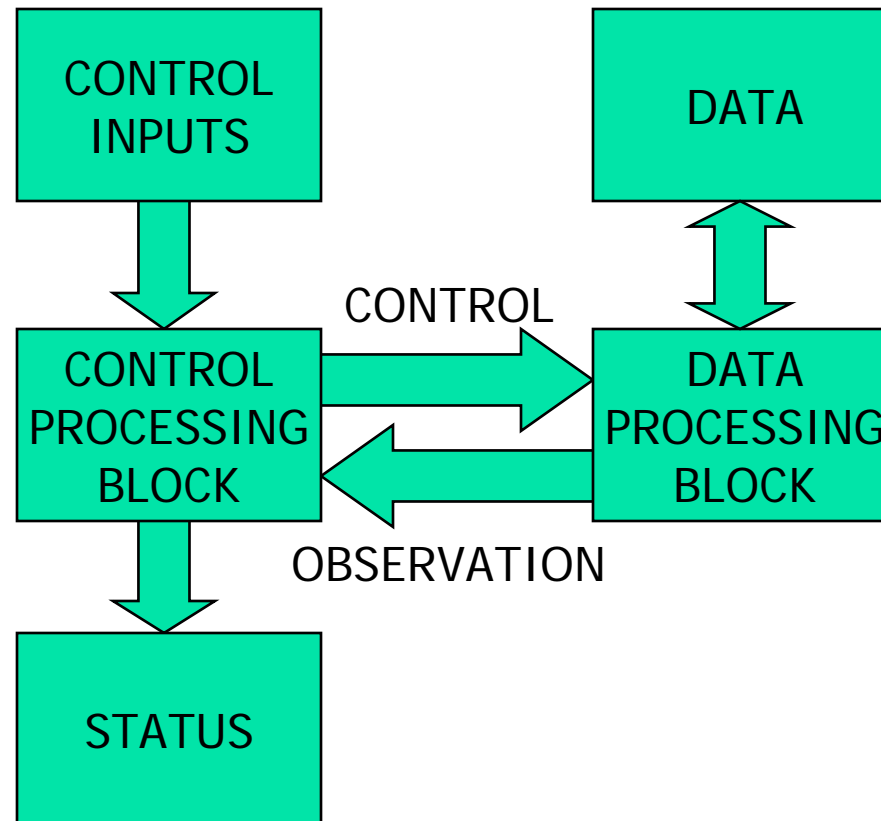


Finite State Machines

- Two Classes of Finite State Machines (FSMs):
 - Moore Machines
 - Mealy Machines


Moore Finite State Machines

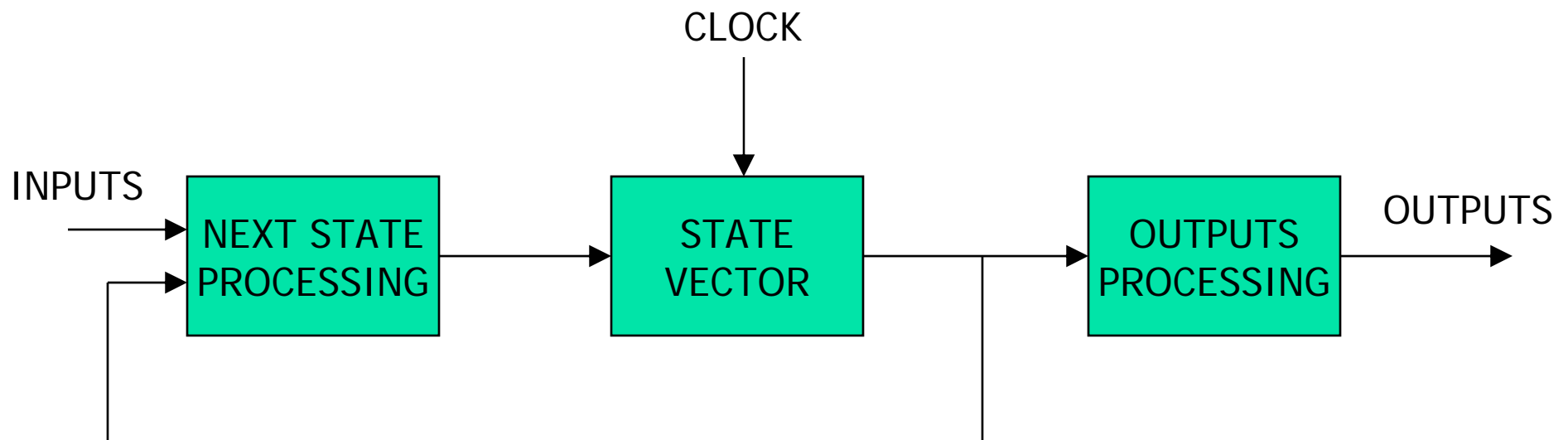
- **Outputs depend only on the state**
- State and Outputs Processing are combinational elements
- State Vector is Sequential Elements



Mealy Finite State Machines

- Outputs depend on the state and the inputs

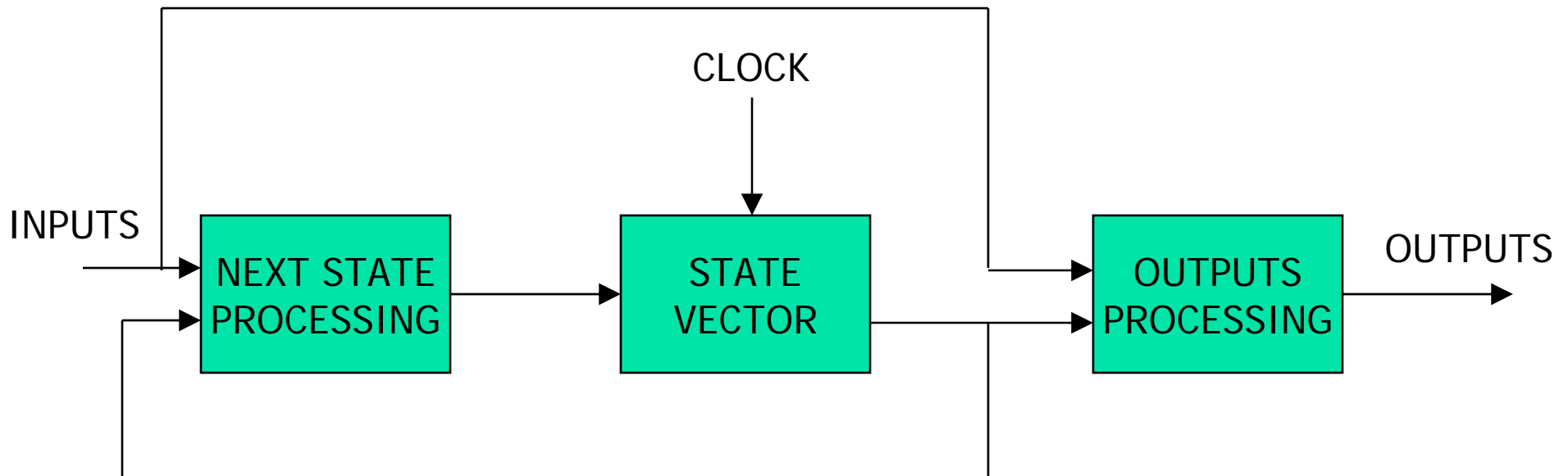

 


Session IV

VHDL IMPLEMENTATION EXAMPLES


– A Decimation Filter for a Sigma-Delta Analog to Digital Converter

2-Ch Σ - Δ Analog to Digital Converter

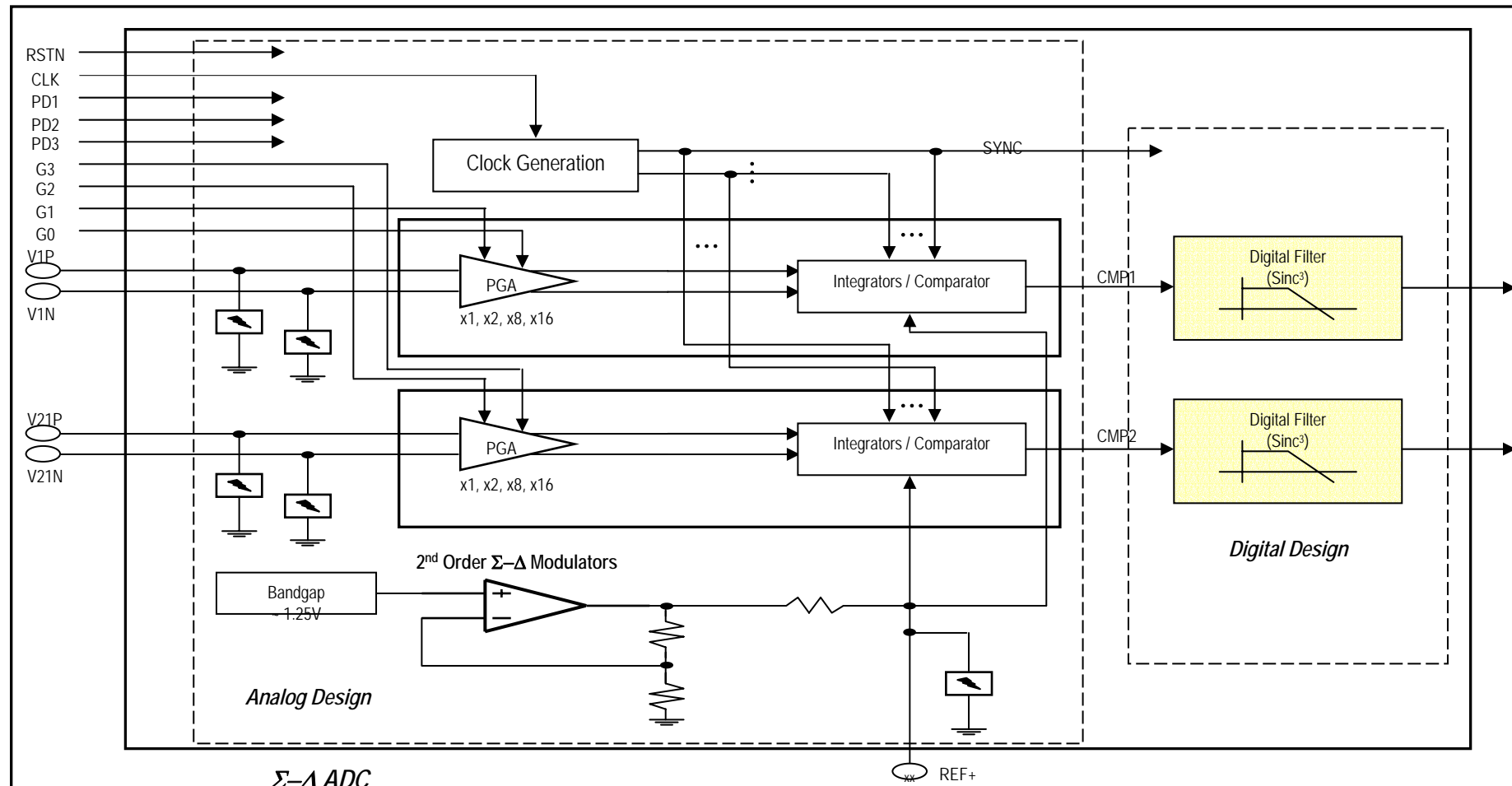




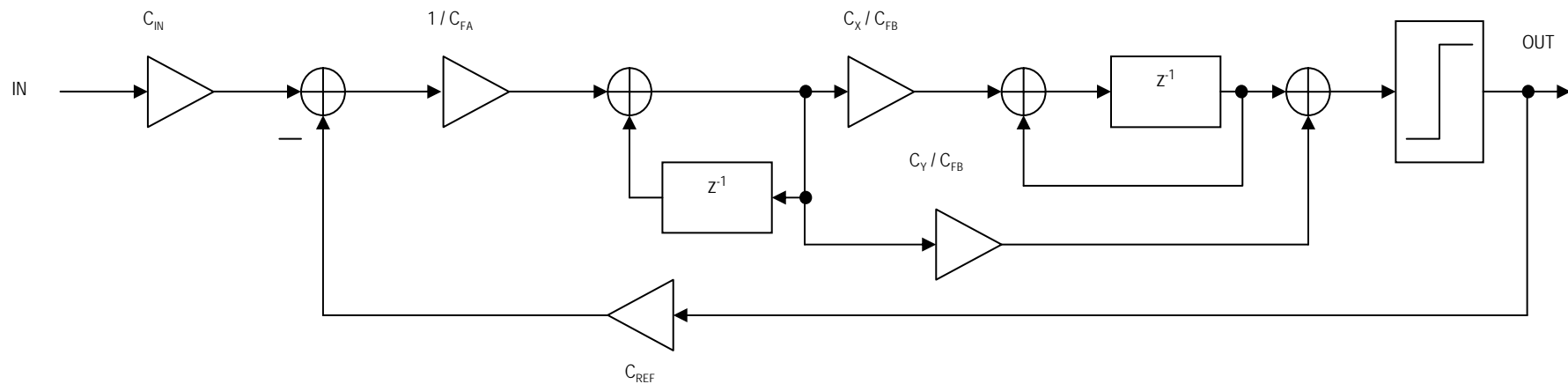2nd Order Σ - Δ Modulator (block/algorithmic)



- This can be modeled in Behavioral VHDL


2nd Order Σ - Δ Modulator (circuit)

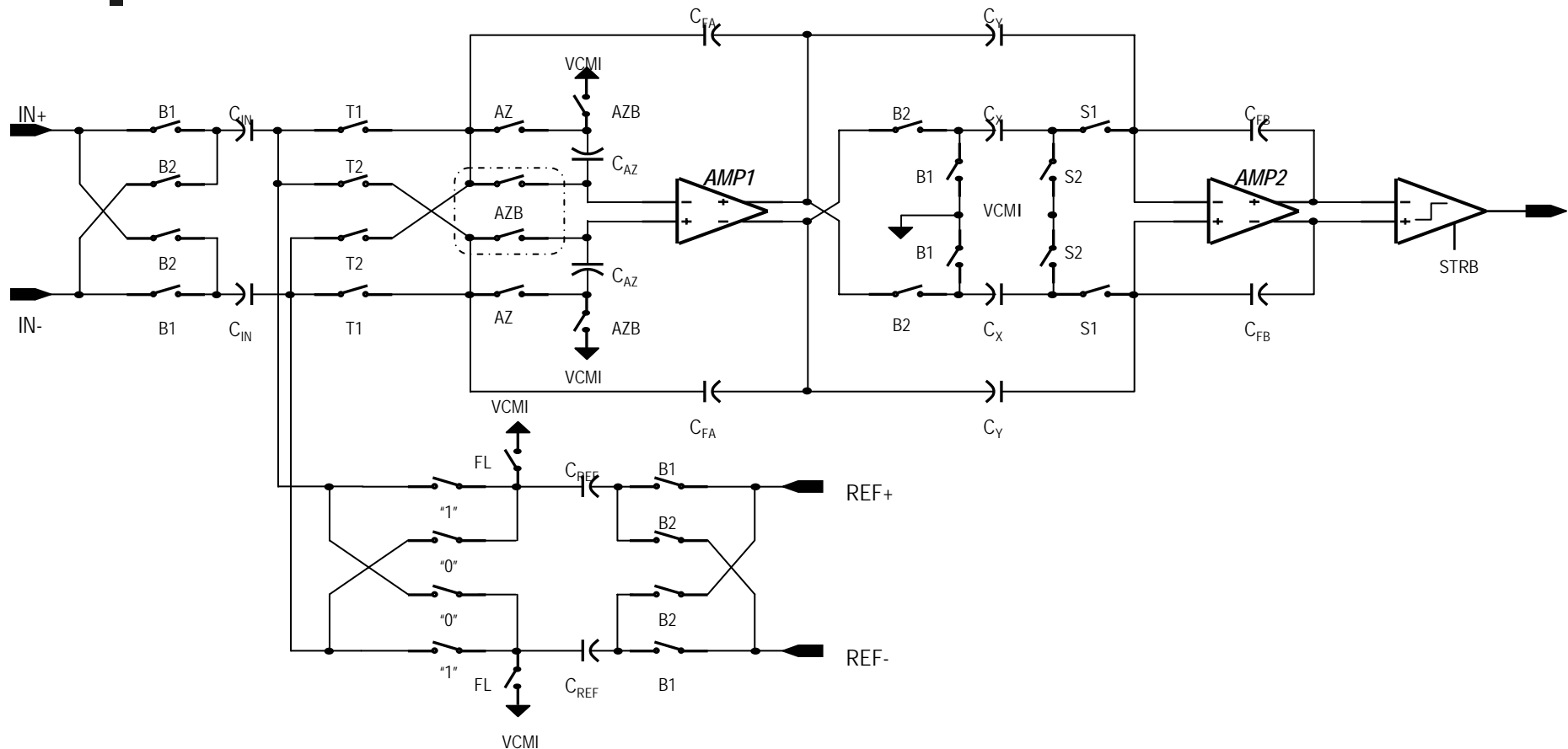

- This can also be modeled in Behavioral VHDL

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

Decimation Digital Filter

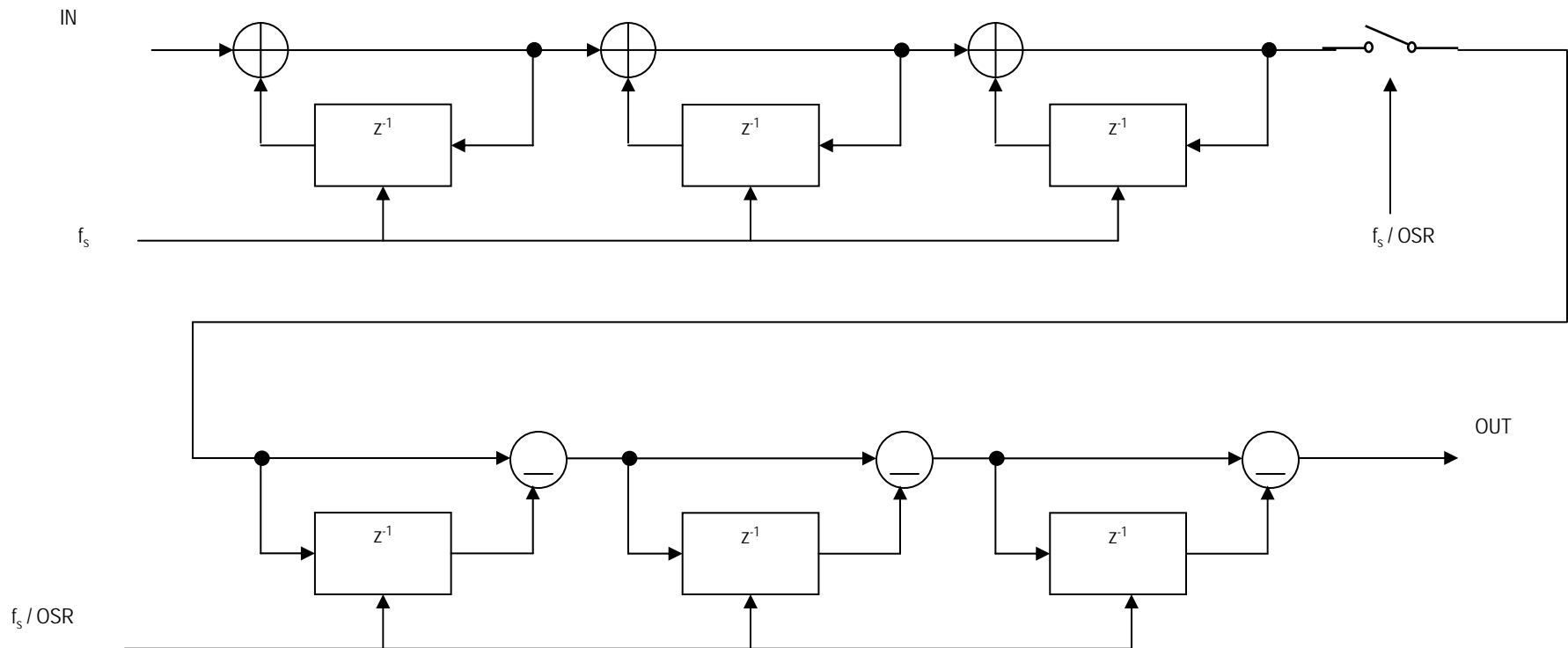

Decimation Digital Filter

- Cubic sinc
- Bits of noise free accuracy for delta-sigma ADC's:
 - $\text{BITS} = 3 * \text{LOG}(\text{OSR}) / \text{LOG}(2) + 2$
 - Assume $\text{OSR}=32$, then $\text{BITS}=17$, and set $\text{BITS}=16$

Decimation Digital Filter

- First Filter Equations
 - $H_1(z) = Y_1(z)/X(z) = 1/(1 - 3z^{-1} + 3z^{-2} - z^{-3})$
 - $y_1(n) = x(n) + 3y_1(n-1) - 3y_1(n-2) + y_1(n-3)$
- Second Filter Equations
 - $H_2(z) = Y(z)/X_1(z) = 1 - 3z^{-1} + 3z^{-2} - z^{-3}$
 - $y(n) = x_1(n) - 3x_1(n-1) + 3x_1(n-2) - x_1(n-3)$
- Decimation (Retiming)
 - $x_1(n) = y_1(n/OSR)$
 - $x_1(n) = y_1(n/32)$


What do we need for our design?

- $y_1(n) = x(n) + 3 y_1(n-1) - 3 y_1(n-2) + y_1(n-3)$
- $y(n) = x_1(n) - 3 x_1(n-1) + 3 x_1(n-2) - x_1(n-3)$
- $x_1(n) = y_1(n/32)$

- Control
 - On every $x(n)$
 - S02: Store $x(n)$ in accumulator, count $x(n) \bmod 32$
 - S03: Accumulate $2 y_1(n-1)$
 - S04: Accumulate $y_1(n-1)$
 - S05: Accumulate 1's complement of $2 y_1(n-2)$
 - S06: Accumulate 1's complement of $y_1(n-2)$
 - S07: Accumulate 2
 - S08: Accumulate $y_1(n-3)$
 - S09: Update y registers
 - On every $x_1(n)$ (every 32nd $y_1(n)$)
 - S10: Accumulate 1's complement of $2 x_1(n-1)$
 - S11: Accumulate 1's complement of $x_1(n-1)$
 - S12: Accumulate $2 x_1(n-2)$
 - S13: Accumulate $x_1(n-2)$
 - S14: Accumulate 1's complement of $x_1(n-3)$
 - S15: Accumulate 3, output result
 - S16: Store $y_1(n-1)$ in accumulator
 - S17: Update x registers

- Data Path
 - 16 bits
 - Adder-Accumulator
 - 1's complement
 - Shift left by one ($\times 2$)
 - Store $y_1(n-1)$, $y_1(n-2)$, $y_1(n-3)$
 - Store $x_1(n-1)$, $x_1(n-2)$, $x_1(n-3)$
 - Constants: 2 & 3

Decimation Digital Filter Architecture

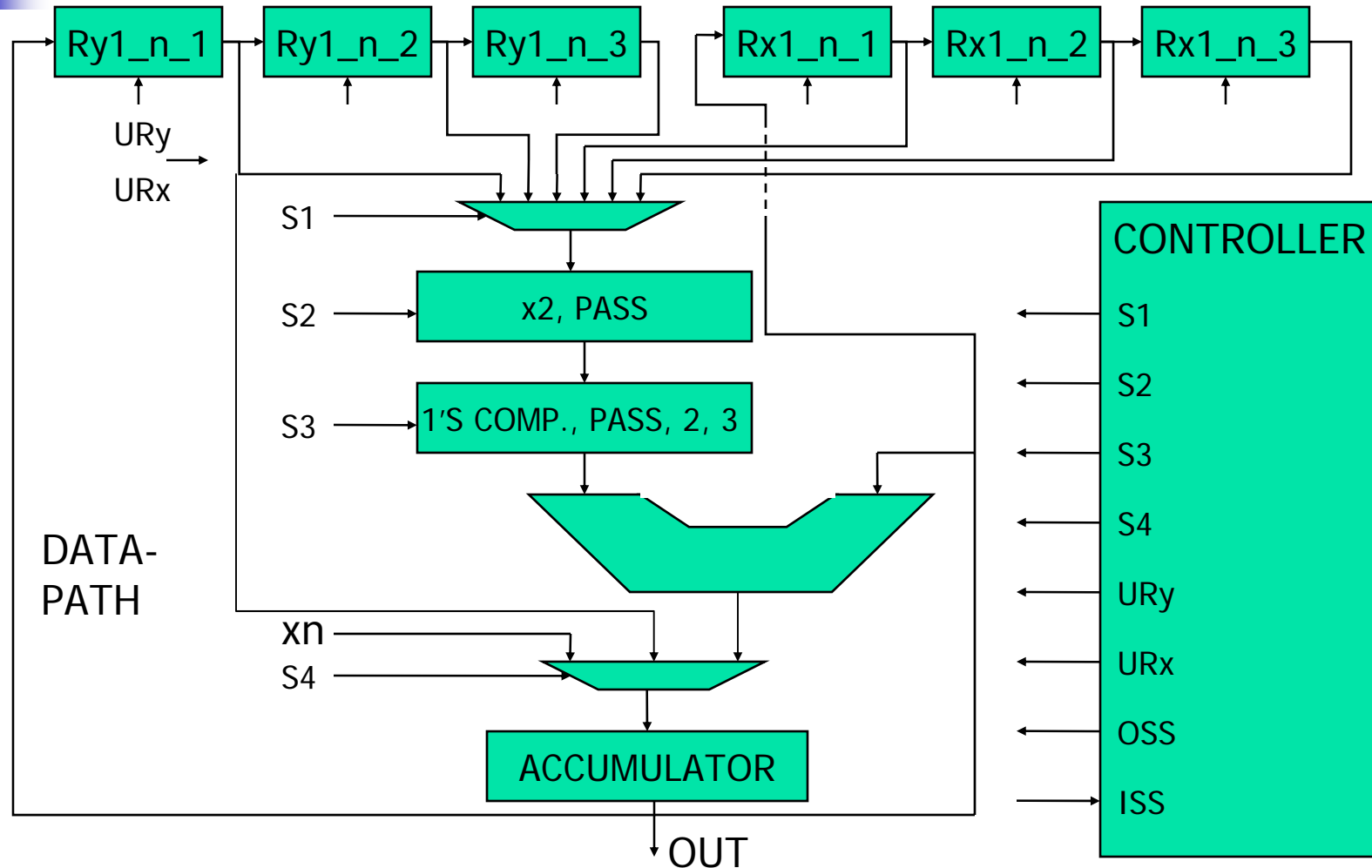

VHDL code for Data_Path

```
--Data_Path
```

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
entity Data_Path is
```

```
port (CLK, reset, xn, URy, URx, S2 : in std_logic;
```

```
      S3, S4 : in std_logic_vector(1 downto 0);
```

```
      S1 : in std_logic_vector(2 downto 0);
```

```
      OUTPUT : out std_logic_vector(15 downto 0));
```

```
end Data_Path;
```

VHDL code for Data_Path

```

architecture behave of Data_Path is
  signal Ry1_n_1, Ry1_n_2, Ry1_n_3 :
    std_logic_vector(15 downto 0);
  signal Rx1_n_1, Rx1_n_2, Rx1_n_3 :
    std_logic_vector(15 downto 0);
  signal ACCUMULATOR : std_logic_vector(15 downto 0);
begin
  OUTPUT <= ACCUMULATOR;
process (CLK, reset) begin
  constant my_zero : std_logic_vector(15 downto 0) :=
    "0000000000000000";
  variable T1, T2, T3, T4, T5 : std_logic_vector(15 downto 0);
  variable my_msb : std_logic;
  if reset = '1' then
    Ry1_n_1 <= my_zero; Ry1_n_2 <= my_zero; Ry1_n_3 <= my_zero;
    Rx1_n_1 <= my_zero; Rx1_n_2 <= my_zero; Rx1_n_3 <= my_zero;
    ACCUMULATOR <= my_zero;
  elseif CLK'EVENT and CLK = '1' then
    if URy = '1' then
      Ry1_n_3 <= Ry1_n_2; Ry1_n_2 <= Ry1_n_1;
      Ry1_n_1 <= ACCUMULATOR;
    end if;
    if URx = '1' then
      Rx1_n_3 <= Rx1_n_2; Rx1_n_2 <= Rx1_n_1;
      Rx1_n_1 <= ACCUMULATOR;
    end if;
    case S1 is
      when "000" => T1 <= Ry1_n_1;
      when "001" => T1 <= Ry1_n_2;
      when "010" => T1 <= Ry1_n_3;
      when "011" => T1 <= Rx1_n_1;
      when "100" => T1 <= Rx1_n_2;
      when "101" => T1 <= Rx1_n_3;
    end case;
    case S2 is
      when '0' =>
        my_msb <= T1(15);
        T2 <= T1 sll 1;
        T3 <= T2 and "0111111111111111";
        T4 <= T3 or (my_msb & "0000000000000000");
        when '1' => T4 <= T1;
    end case;
    case S3 is
      when "00" => T5 <= not T4;
      when "01" => T5 <= T4;
      when "10" => T5 <= "0000000000000010";
      when "11" => T5 <= "0000000000000011";
    end case;
    case S4 is
      when "00" =>
        ACCUMULATOR <= "0000000000000000" & xn;
      when "01" => ACCUMULATOR <= Ry1_n_1;
      when "10" =>
        ACCUMULATOR <= ACCUMULATOR + T5;
    end case;
  end if;
end process;
end behave;

```

VHDL code for Controller

```

--Controller
library IEEE;
use IEEE.std_logic_1164.all;

entity Controller is
generic (TPD : TIME := 1 nS);
port (CLK, reset, ISS : in std_logic;
       URy, URx, S2, OSS : out std_logic;
       S3, S4 : out std_logic_vector(1 downto 0);
       S1 : out std_logic_vector(2 downto 0));
end Controller;
  
```

VHDL code for Controller

```

architecture Moore of Controller is
  type STATETYPE is (S00, S01, S02, S03, S04, S05,
    S06, S07, S08, S09, S10, S11, S12, S13, S14, S15,
    S16, S17);
  signal State : STATETYPE;
  signal Counter : std_logic_vector(4 downto 0);
begin
  URy <= '1' after TPD when State = S09
    else '0' after TPD;
  URx <= '1' after TPD when State = S17
    else '0' after TPD;
  with State select
    S1 <= "000" after TPD when S03 | S04 | S16,
    "001" after TPD when S05 | S06,
    "010" after TPD when S08,
    "011" after TPD when S10 | S11,
    "100" after TPD when S12 | S13,
    "101" after TPD when S14;
  
```

```

    S2 <= '0' after TPD when State = S03 or
      State = S05 or State = S10 or State = S12
      else '1' after TPD;
  with State select
    S3 <= "00" after TPD when S05 | S06 | S10 |
      S11 | S14,
    "01" after TPD when S03 | S04 | S08 | S12 |
      S13 | S16,
    "10" after TPD when S07,
    "11" after TPD when S15;
  with State select
    S4 <= "00" after TPD when S02,
    "01" after TPD when S16,
    "10" after TPD when S03 | S04 | S05 | S06 |
      S07 | S08 | S10 | S11 | S12 | S13 | S14 | S15;
  OSS <= '1' after TPD when State = S15
    else '0' after TPD;
  
```

VHDL code for Controller

```

process (CLK, reset) begin
  if reset = '1' then State <= S00;
  elseif CLK'EVENT and CLK = '1' then
    case State is
      when S00 =>
        if ISS = '1' then State <= S02;
        end if;
      when S01 =>
        if ISS = '1' then State <= S02;
        end if;
      when S02 =>
        if Counter = "11111" then
          Counter <= "00000";
        else
          Counter <= Counter + "00001";
        end if;
        State <= S03;
      when S03 => State <= S04;
      when S04 => State <= S05;
      when S05 => State <= S06;
      when S06 => State <= S07;
      when S07 => State <= S08;
      when S08 => State <= S09;
      when S09 =>
        if Counter = "00000" then
          State <= S10;
        else
          State <= S01;
        end if;
      when S10 => State <= S11;
      when S11 => State <= S12;
      when S12 => State <= S13;
      when S13 => State <= S14;
      when S14 => State <= S15;
      when S15 => State <= S16;
      when S16 => State <= S17;
      when S17 => State <= S01;
    end case;
  end if;
end process;
end Moore;
  
```

Main Code for FILTER

```
library IEEE;  
use IEEE.std_logic_1164.all;  
  
entity FILTER is  
    port (reset, CLK, ISS, xn : in std_logic;  
          OSS : out std_logic;  
          OUTPUT : out  
            std_logic_vector(15 downto 0));  
end entity FILTER;
```

Main Code for FILTER Cont...

architecture structural **of** FILTER **is**

```

signal URy, URx, S2 : std_logic;
signal S3, S4 : std_logic_vector(1 downto 0);
signal S1 : std_logic_vector(2 downto 0);
  
```

begin


```

c: Controller port map (CLK => CLK, reset => reset,
  ISS => ISS, URy => URy, URx => URx, S2 => S2,
  OSS => OSS, S3 => S3, S4 => S4, S1 => S1);
dp: Data_Path port map (CLK => CLK, reset => reset,
  xn => xn, URy => URy, URx => URx, S2 => S2,
  S3 => S3, S4 => S4, S1 => S1, OUTPUT => OUTPUT);
  
```


end architecture structural;

Conclusions

From Gates to Large IP

 

Conclusions

 


Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL


UNIVERSIDAD DEL NORTE

May 21 - 23, 2003

202

 

Thanks.....

 

lenavarr@eng.usf.edu
hernande@a-wit.com

Tecnologías de la Información: Telecomunicaciones, Aplicaciones en
Procesamiento Digital de Señales y Diseño Digital con VHDL

UNIVERSIDAD DEL NORTE